

D

# Topic: TRANSISTOR BIASING

U.G. - III

Consider an npn transistor circuit shown in fig (1a). During the positive half-cycle of the signal, base is +ve w.r.t emitter and hence base-emitter junction is forward biased. This will cause a base current and much larger collector current to flow in the circuit. The result is that positive half-cycle of the signal is amplified in the collector as shown. However, during the negative half-cycle of the signal, base-emitter junction is reverse-biased and hence no current flows in the circuit. The result is that there is no output due to the negative half-cycle of the signal. Thus we shall get an amplified output of the signal with its negative half-cycles completely cut off which is unfaithful amplification.

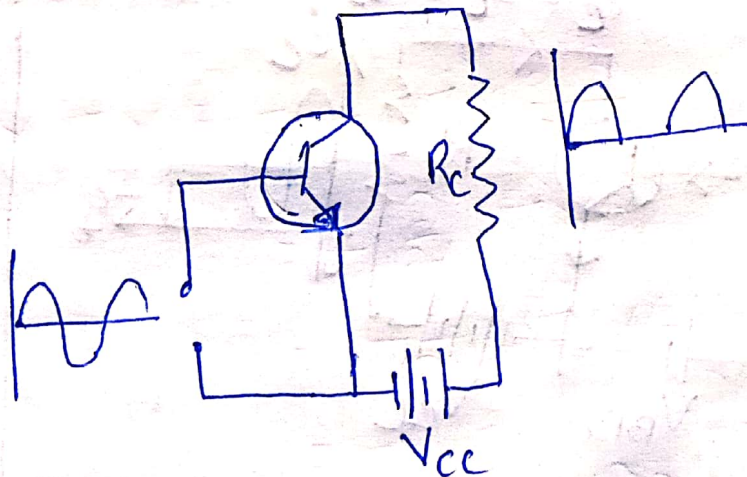


Fig (1a)

Now, a battery source  $V_{BB}$  in the base circuit is introduced as shown in fig (1b). The magnitude of this voltage should be such that it keeps the input circuit forward biased even during the peak of negative half cycle of the signal, when no signal is applied, a d.c. current  $I_c$  will flow in the collector circuit due to  $V_{BB}$  as shown. This is known as "zero signal collector current" ( $I_c$ ). During the positive half-cycle of the signal, input circuit is more forward biased and hence collector current increases. However, during the negative half cycle of the signal, the input circuit is less forward biased and collector current decreases. In this way, negative half-cycle of the signal also appears in the output and hence faithful amplification results. It follows that for faithful amplification, proper zero signal collector current must flow.

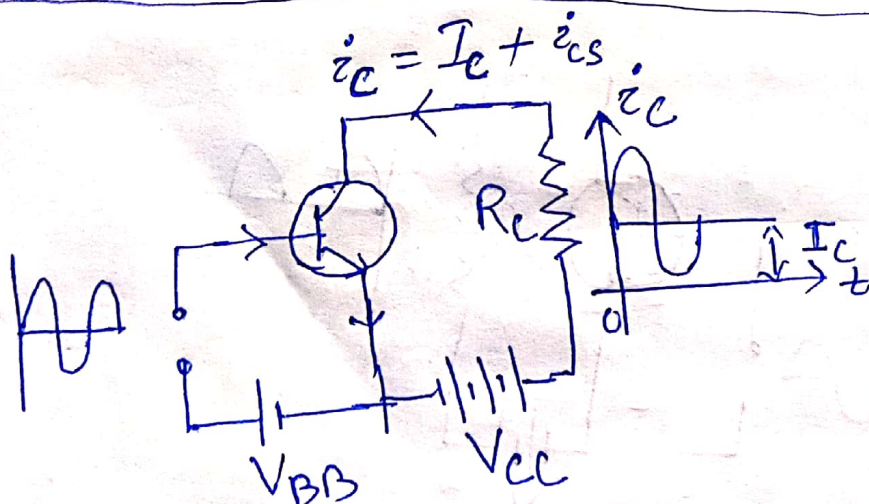


Fig. (1b)

Total  
 $i_c$  = Collector current  
 $I_c$  = Zero signal current  
 $i_{cs}$  = Current due to signal.

(3)

Thus transistor biasing is the process of flow of zero signal collector current and the maintenance of proper collector-emitter voltage during the passage of signal. The basic purpose of transistor biasing is to keep the base-emitter junction properly forward biased and collector-base junction properly reverse biased during the application of the signal.

The following are the most commonly used methods of obtaining transistor biasing from one source of supply  $V_{CC}$ :

- (i) Base resistor method
- (ii) Emitter bias method
- (iii) Biasing with collector-feedback resistor
- (iv) voltage-divider bias

### (i) Base Resistor Method


In this method, a high resistance  $R_B$  of several hundred  $k\Omega$  is connected between the base and +ve end of supply for npn transistor as shown in fig (2) and between base and -ve end of supply for pnp transistor. Here, the required zero signal base current is provided by  $V_{CC}$  and it flows through  $R_B$  because base is +ve w.r.t emitter i.e. base-emitter junction is forward biased. The required value of zero

(4) Signal base current  $I_B$  and hence  $I_C = \beta I_B$  can be made to flow by selecting the proper value of base resistor  $R_B$ .

Circuit Analysis:-

We have to find the value of  $R_B$  so that required collector current flows in the zero signal condition. Let  $I_C$  be the required zero signal collector current.

$$\therefore I_B = \frac{I_C}{\beta}$$

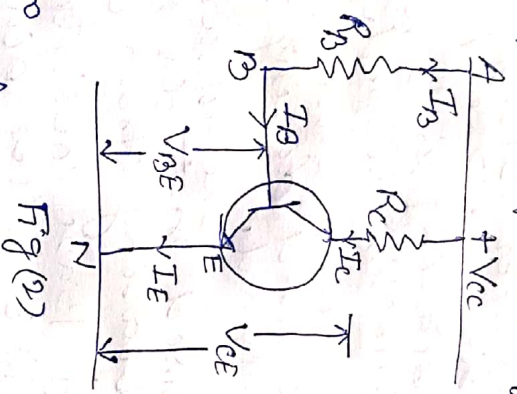

Considering the closed circuit ABENA and applying Kirchhoff's voltage law, we get,

$$V_{CC} = I_B R_B + V_{BE}$$

$$\text{or, } I_B R_B = V_{CC} - V_{BE}$$

$$\therefore R_B = \frac{V_{CC} - V_{BE}}{I_B} \quad \text{--- (1)}$$

As  $V_{CC}$  and  $I_B$  are known and  $V_{BE}$  can be seen from the transistor manual, therefore, value of  $R_B$  can be readily found from eqn (1).

(5) Since  $V_{BE}$  is generally quite small compared to  $V_{CC}$ , the former can be neglected with little error. It then follows from eqn (1) that

$$R_B = \frac{V_{CC}}{I_B}$$

It may be noted that  $V_{CC}$  is a fixed known quantity and  $I_B$  is chosen at some suitable value, hence  $R_B$  can always be found directly and for this reason, this method is sometimes called fixed bias method.

(To be continue)