

**Paper 1, TDC Part-1**  
**Chapter– 4, Circuit Theorems**  
**Lecture - 9**

**By:**

**Mayank Mausam**

**Assistant Professor (Guest Faculty)**

**Department of Electronics**

**L.S. College, BRA Bihar University,**

**Muzaffarpur, Bihar**

# Circuit Theorem

In this lecture we will discuss about 'Reciprocity' Theorem.

Like other theorems, this theorem is also very useful for those network which has independent source, is made of resistive element and the network is linear or bilateral.

So If we wish to apply reciprocity theorem in any network then following condition must be satisfied-

- a) The network consist of independent source.
- b) The network is made up of resistive elements only, that means n/w should be time invariant.
- c) The network is linear and bilateral.

## Circuit Theorem

It means that reciprocity theorem is not applicable:-

- 1) Network with of dependent source.
- 2) In time variant network.
- 3) In a non linear network.

A network or circuit in which reciprocity theorem is applicable is called reciprocal network/ circuit.

# Circuit Theorem

Explanation of Reciprocity Theorem

Let us consider a <sup>passive</sup> n/w of linear elements.

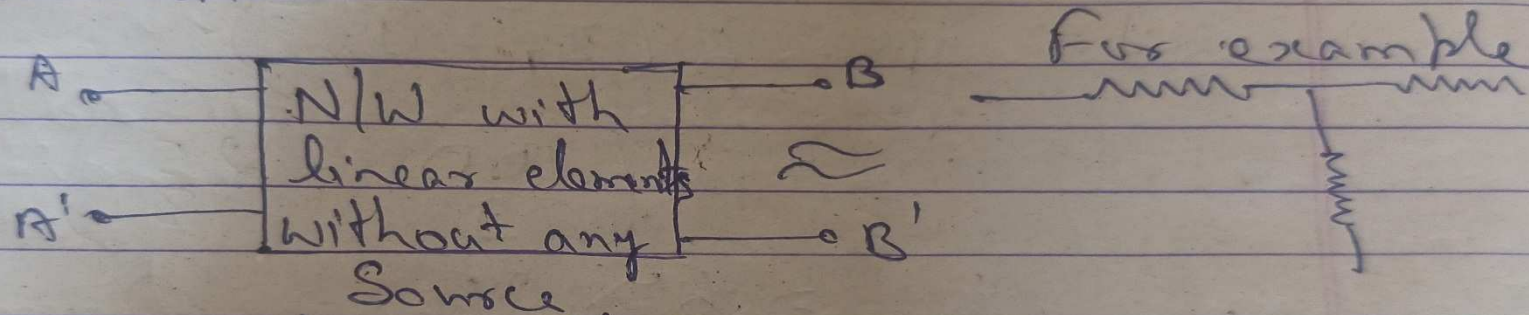


Figure 1(a)

Let the above n/w be excited by a voltage ~~and~~ source which is independent at terminal AA'. Due to this voltage source the current  $I$  flows through the short circuit terminal BB' as shown in figure 1(b)

# Circuit Theorem

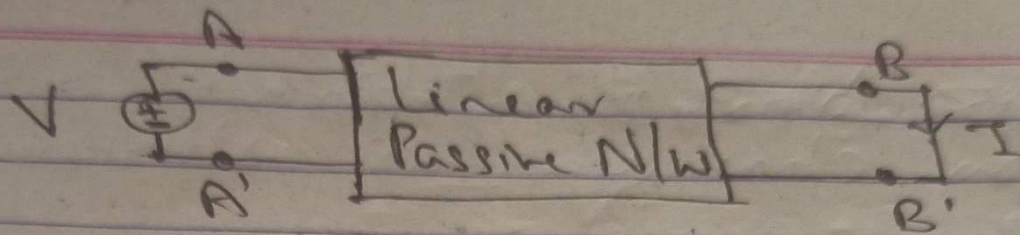


Figure 1 (b)

Here 'V' is the supply voltage and 'I' is the output current, are mutually transferable and the ratio of V and I is called the transfer resistance.

Now as per the Reciprocity theorem if this supply voltage 'V' is connected between terminal 'BB'', then the current response in the short circuited terminal 'AA' will be 'I' as shown in figure below

# Circuit Theorem

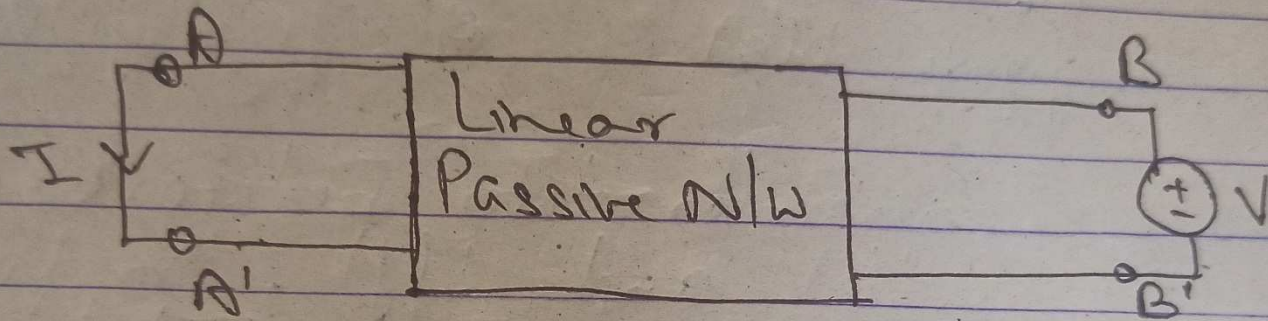


Figure 2(c)

Here we should also note that <sup>if</sup> the direction of supplying voltage ~~should~~ is ~~be~~ same then the direction of response current will be also same.

If the direction of voltage is change the

# Circuit Theorem

The direction of response current will be also changed as shown in figure 1(d)


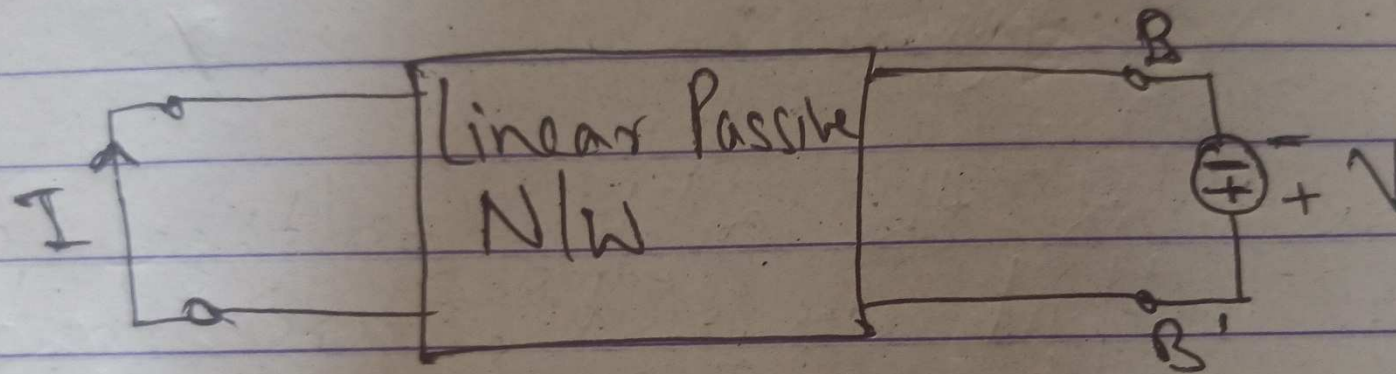
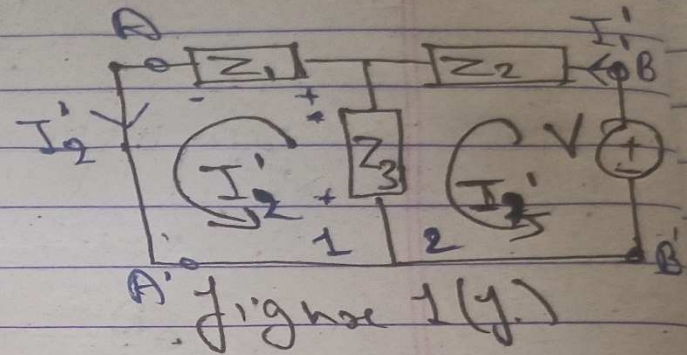


Figure 1(d)

Proof of Reciprocity Theorem :-

# Circuit Theorem

Proof of Reciprocity Theorem :-

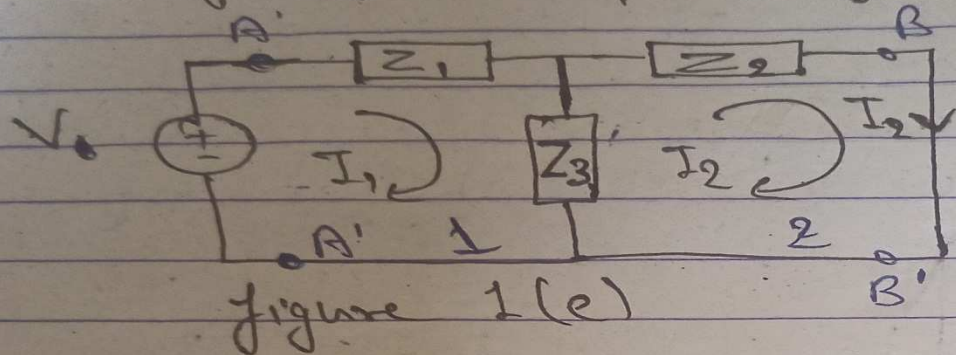

Let us consider two network as shown in figure 1(e) and 1(f). In figure 1(e) the voltage source is connected between terminal  $AA'$  and response current is  $I_2$  flowing in short circuit terminal  $BB'$ .

While in figure 1(f) the n/w is just as in the figure 1(e), but here the voltage source is connected between terminal  $BB'$  and response current  $I_2'$  is between short circuit terminal  $AA'$ .

# Circuit Theorem

So As per reciprocity theorem,

$$\frac{I_2}{V} = \frac{I_2'}{V} \quad \text{or,} \quad \frac{V}{I_2} = \frac{V}{I_2'}$$

This is possible only when  $I_2' = I_2$

Let us find the current  $I_2$  in terminal BB' of figure 1(c)

Applying KVL in loop 1,

$$I_1 Z_1 + I_1 Z_3 - I_2 Z_3 = V$$

$$\text{or, } I_1 (Z_1 + Z_3) - I_2 Z_3 = V \quad \text{--- (i)}$$

# Circuit Theorem

$$\text{or, } I_1 (Z_1 + Z_3) - I_2 Z_3 = V \quad \text{--- (i)}$$

Now applying KVL in loop 2,

$$-I_1 Z_3 + I_2 Z_2 + I_2 Z_3 = 0$$

or,

$$I_1 Z_3 = I_2 (Z_2 + Z_3)$$
$$I_1 = \frac{I_2 (Z_2 + Z_3)}{Z_3}$$

putting value of  $I_1$  in eqn. (i) we get

$$\frac{I_2 (Z_2 + Z_3)(Z_1 + Z_3)}{Z_3} - I_2 Z_3 = V$$

# Circuit Theorem

$$\text{Or, } I_2 (Z_1 Z_2 + Z_1 Z_3 + Z_2 Z_3 + \cancel{Z_2^2}) - \cancel{I_2 Z_3^2} = \sqrt{Z_3}$$

$$\text{Or, } \frac{I_2}{\cancel{\bullet}} = \frac{\sqrt{Z_3}}{Z_1 Z_2 + Z_3 Z_1 + Z_2 Z_3}$$

Now we will find  $I_2'$  for circuit shown in figure 1(f).

Applying KVL in loop 1 of figure 1(f)

$$I_2' (Z_1 + Z_3) - I_1' Z_3 = 0$$

$$I_1' = \frac{I_2' (Z_1 + Z_3)}{Z_3}$$

# Circuit Theorem

KVL in loop 1 of figure 1(f)

$$I_1'(Z_2 + Z_3) - I_2' Z_3 = \text{⊙ } V$$

putting value of  $I_1'$  we get.

$$\frac{I_2'(Z_2 + Z_3)(Z_1 + Z_3)}{Z_3} - I_2' Z_3 = V$$

$$I_2'(Z_1 Z_2 + Z_3 Z_1 + Z_2 Z_3 + \cancel{Z_3^2}) - \cancel{I_2' Z_3^2} = V Z_3$$

$$\text{or, } I_2' = \frac{V Z_3}{Z_1 Z_2 + Z_2 Z_3 + Z_3 Z_1}$$

# Circuit Theorem

As, the value of  $I_2$  and  $I_2'$  are same, so the ratio of response to excitation for both n/w of figure 1(c) & 1(f) are same i.e.


$$\frac{I_2}{V} = \frac{I_2'}{V} \quad \text{or,} \quad \frac{V}{I_2} = \frac{V}{I_2'}$$

This proves the reciprocity theorem.

Similarly if the value of voltage source is multiplied with any number then the response current will be also multiplied with the same number.

# Circuit Theorem

Ex. for network of figure 1(f).

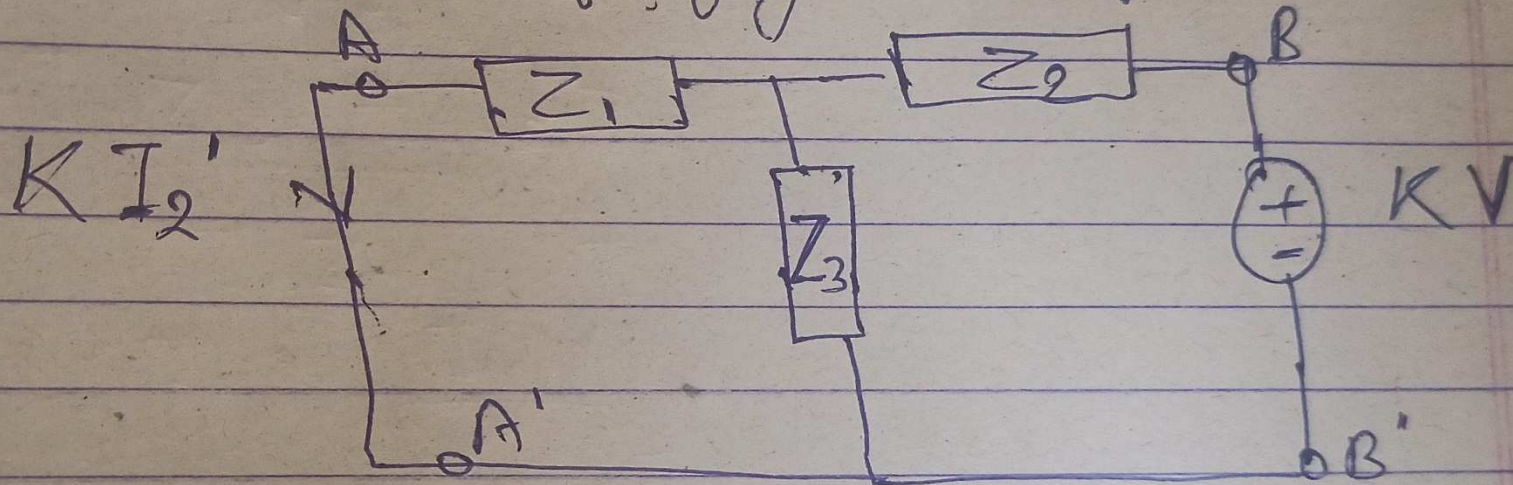

$$\text{So, } \frac{I_2}{V} = \frac{KI_2'}{KV} = \frac{I_2'}{V}$$

This proves the reciprocity theorem

# Circuit Theorem

In next lecture we will discuss problem based on reciprocity theorem.

*THANK YOU*