

Paper 1, TDC Part-1
Chapter– 4, Circuit Theorems
Lecture - 12

By:

Mayank Mausam

Assistant Professor (Guest Faculty)

Department of Electronics

L.S. College, BRA Bihar University,

Muzaffarpur, Bihar

Circuit Theorem

Let us see some problems on Star-delta transformation


Whenever we deal with star or delta connection during analysis of circuit we will must follow the following steps

1.) While analysing any network first we have to solve series & || combination of resistors. Without solving series & || combination we ~~will do~~ should not do any transformation i.e. either "Star to Delta" transformation or "Delta to Star" transformation.

Circuit Theorem

Once we resolve series & parallel combination then we do required transformation.

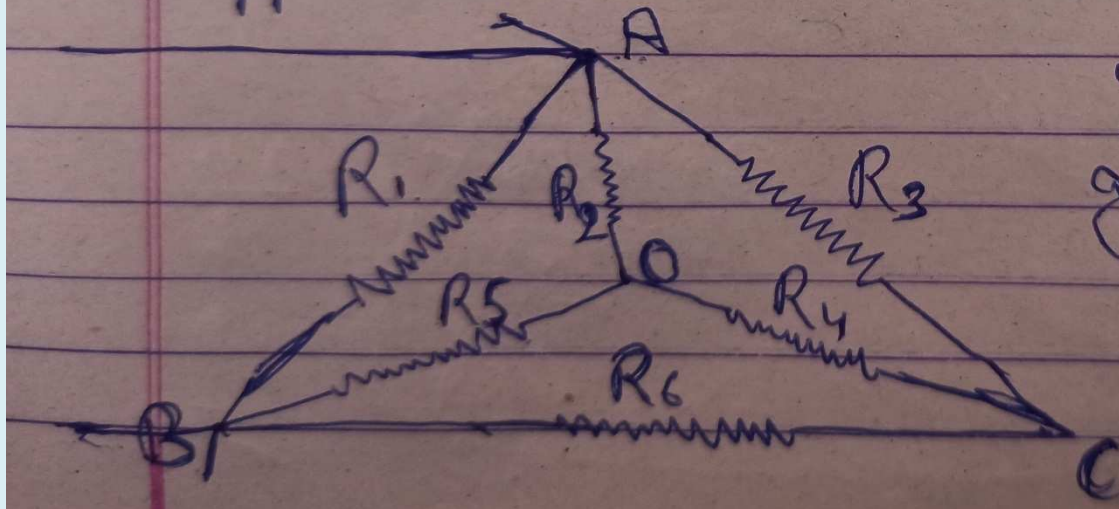
2.) Whenever we deal with 3 delta at a time then we should solve the star i.e. transform the star to delta which appear between the 3 delta.



In figure of the given network we have 3 delta, AOB, AOC, BOC

Circuit Theorem


We can see the star, between the delta

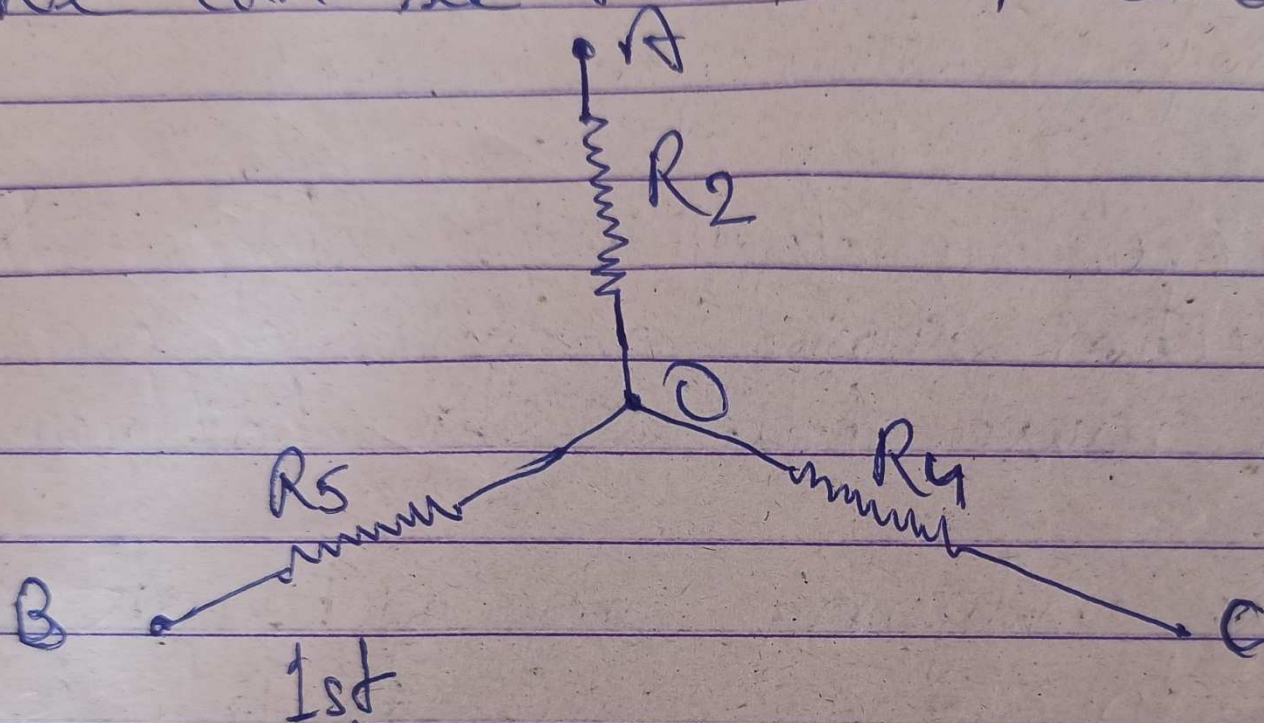

We will transform this star to delta then solve the network.

Circuit Theorem

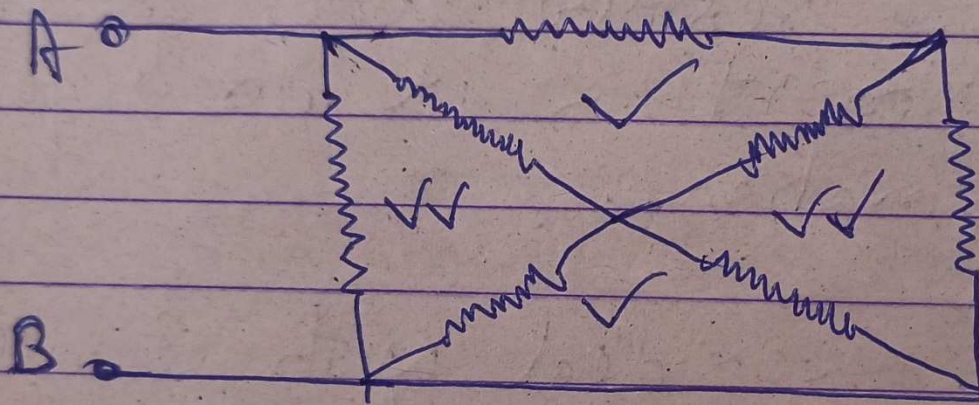
3) If ~~we~~ there are 4 delta at a time in a n/w we will then solve ~~the~~ two opposite delta at a time.



So here we solve either single tick delta at a time or double tick delta at a time.

Circuit Theorem

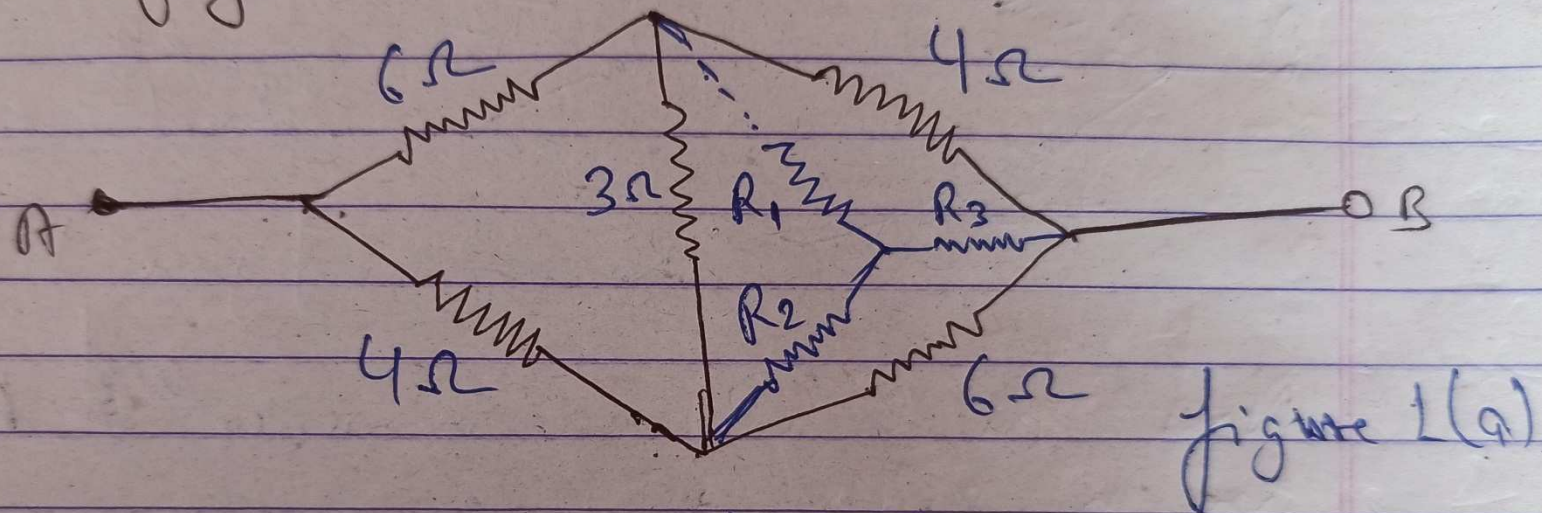Example's Find the equivalent resistor between terminal A & B of the network given in figure 1(a).



Soln. In the given figure we can see that there is no combination of series and parallel resistor. There are 2 delta connection of resistor. So to find equivalent resistance between terminal

Circuit Theorem

connection of resistor. So to find equivalent resistance between terminal A & B we transform any ~~of~~ one of the delta to star connection. Let us transform the delta connection of right side i.e. towards terminal B.


Now using the formula of delta to star transform we find the equivalent resistor R_1 , R_2 & R_3 as,

$$R_1 = \frac{3 \times 4}{3 + 4 + 6} = \frac{12}{13} \Omega ; R_2 = \frac{3 \times 6}{13} = \frac{18}{13}$$


$$R_3 = \frac{4 \times 6}{13} = \frac{24}{13}$$

Circuit Theorem


Now drawing the N/W with star connection

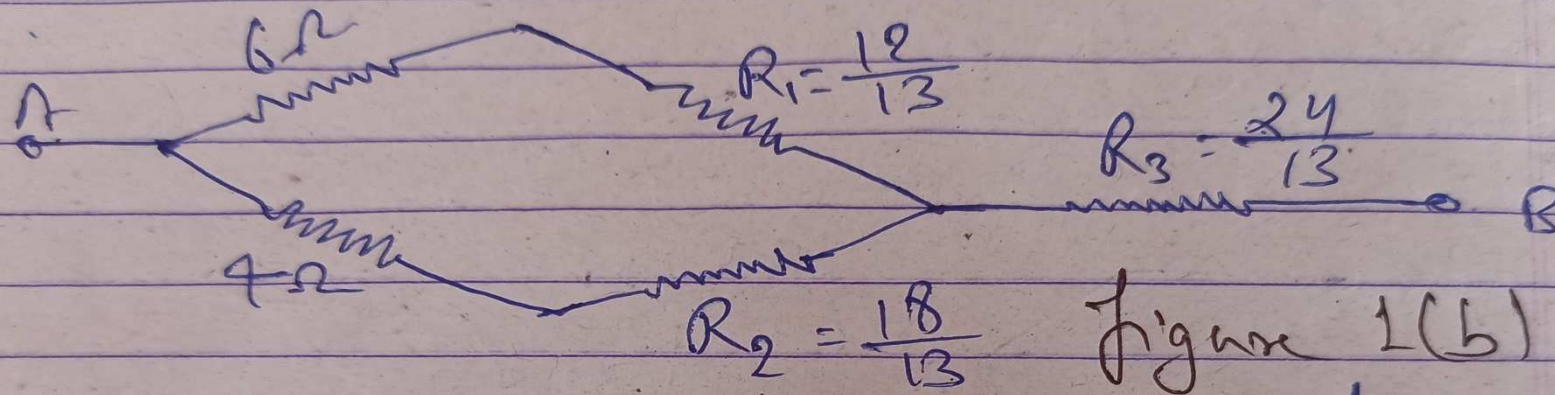

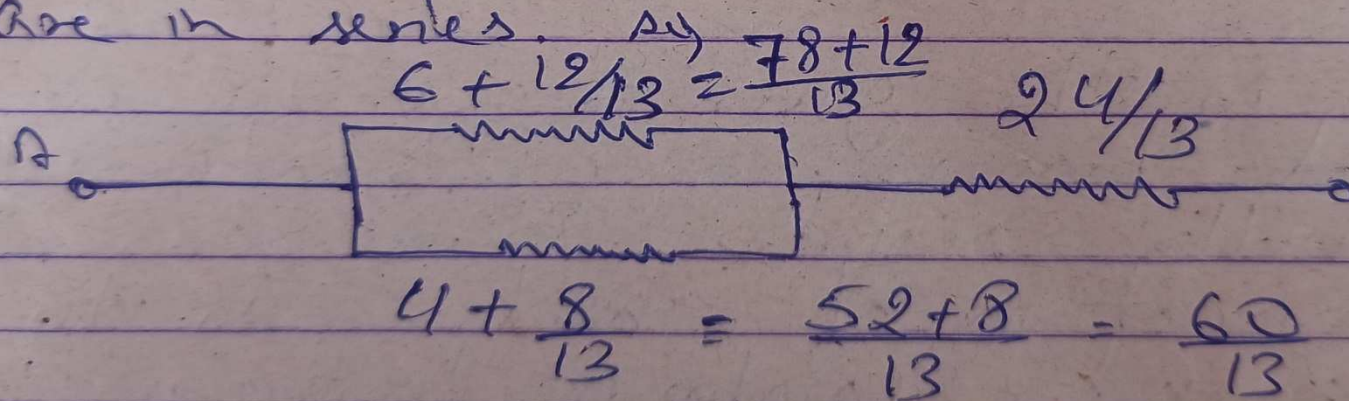Now R_1 & 6Ω are in series and R_2 & 4Ω are in series.



Circuit Theorem

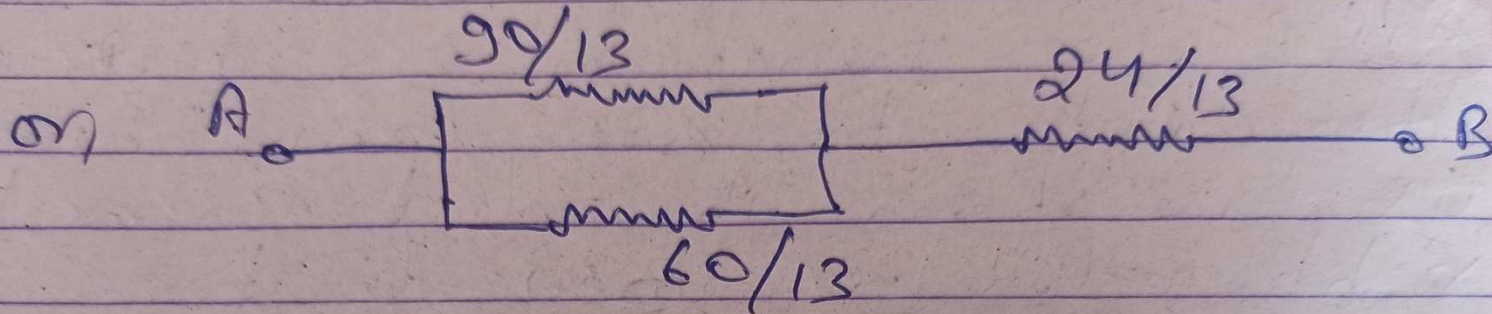


Equivalent resistor between terminal A & B is

$$R_{eq} = \left(\frac{90}{13} \parallel \frac{60}{13} \right) + \frac{24}{13}$$

$$= \frac{\frac{90}{13} \times \frac{60}{13}}{\frac{90+60}{13}} = \frac{18}{13} + \frac{24}{13}$$

$$R_{eq} = \frac{36}{13} + \frac{24}{13} = \frac{60}{13} \Omega$$

Circuit Theorem

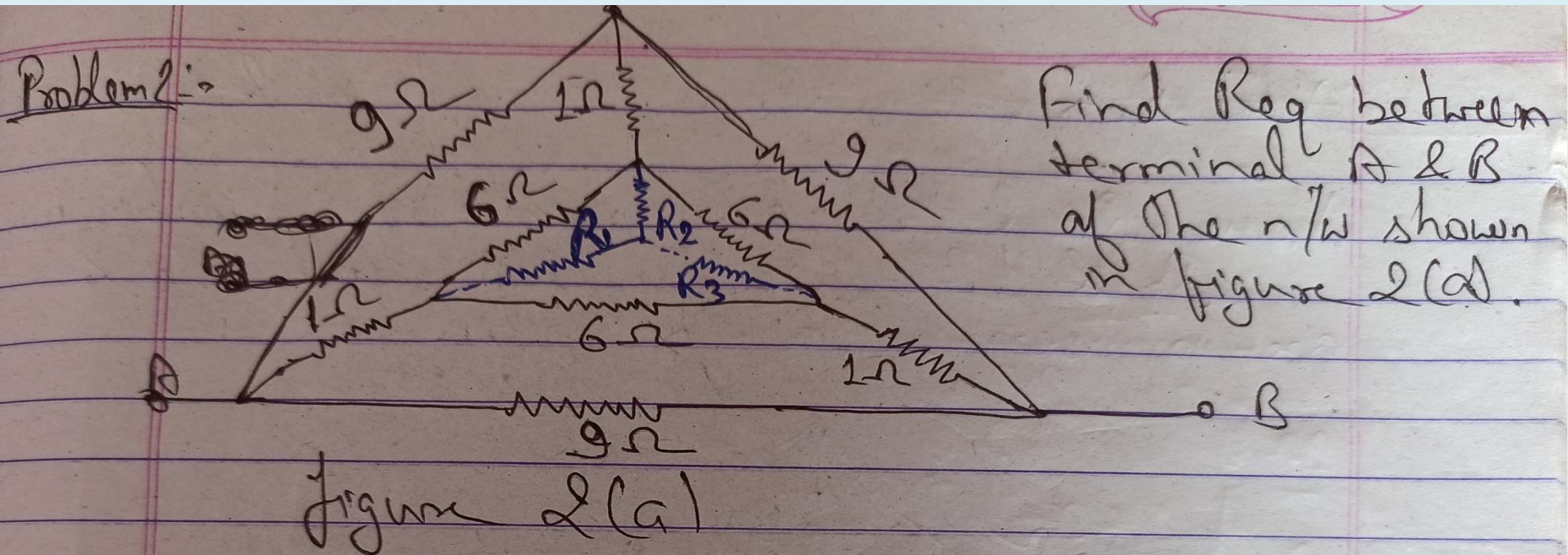


Soln:- In the given n/w of figure 2(a) we have two delta connection one is inside and other is outside. There is no series & || connection of resistors. To find R_{eq} we will transform delta of inside into star connection, so,

Circuit Theorem

$$R_1 = \frac{6 \times 6}{6+6+6} = \frac{36}{18} = 2\Omega = R_2 = R_3$$


As all arm contain resistors of same value so $R_1 = R_2 = R_3 = 2\Omega$.

Now the N/W will be.

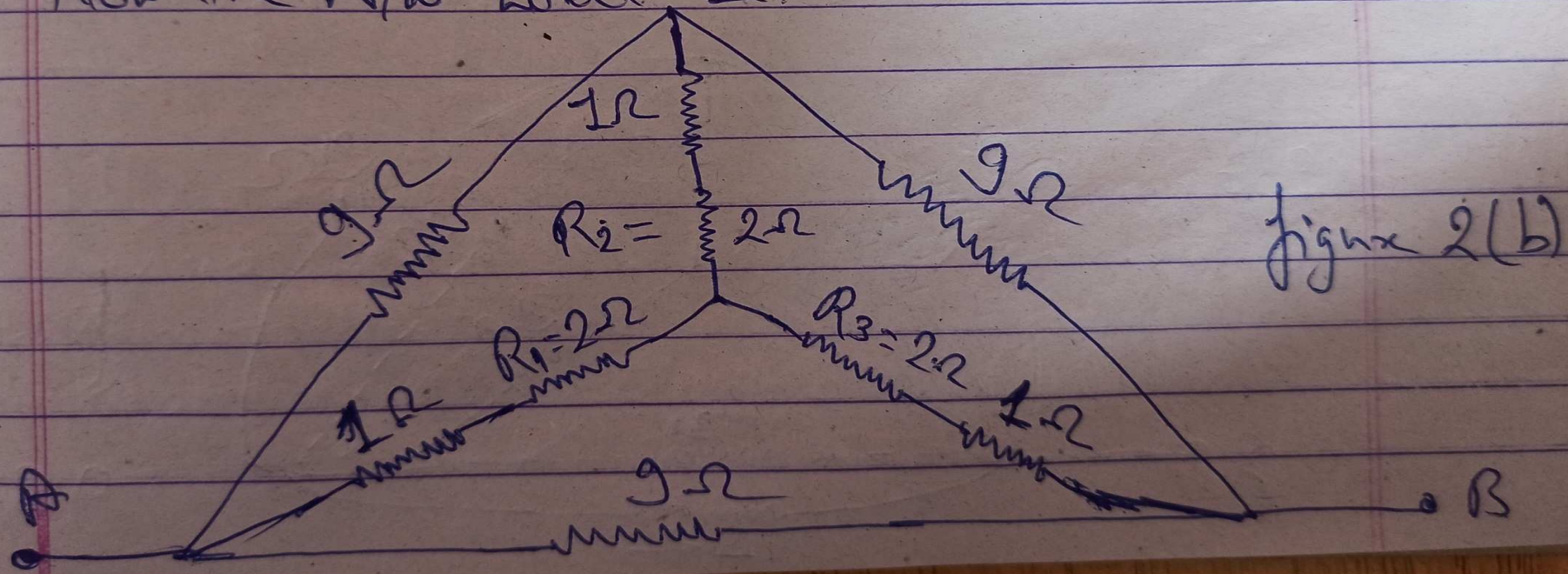

Circuit Theorem

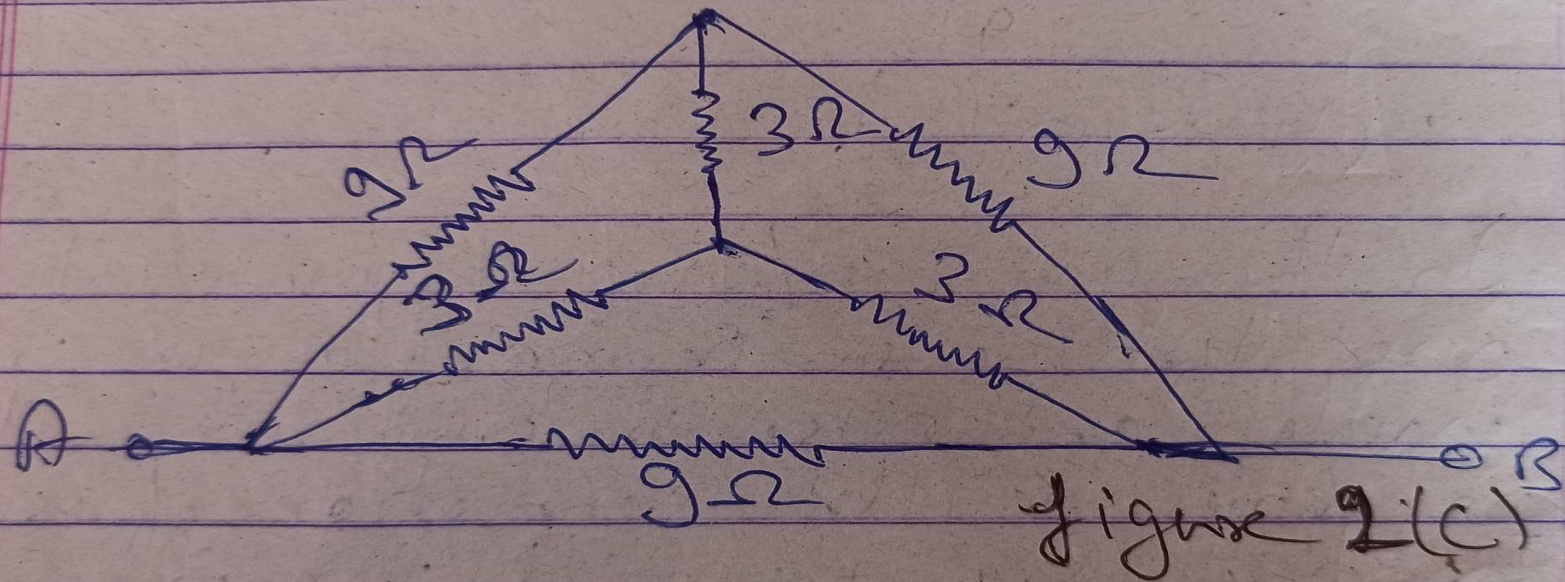Now R_1 & $1R$ are in series, similarly, R_2 & $1R$ " " " and R_3 & $1R$ are in series. so the n/w is.



Now again there is no any series or ||^l connection. Here we can say that these are 3, delta connection or 1 delta

Circuit Theorem

Now again there is no any series or || connection. Here we can say that these are 3 delta connection or 1 delta connection outside and 1 star connection inside delta connection.

Here we will transform inner star connection into delta connection.

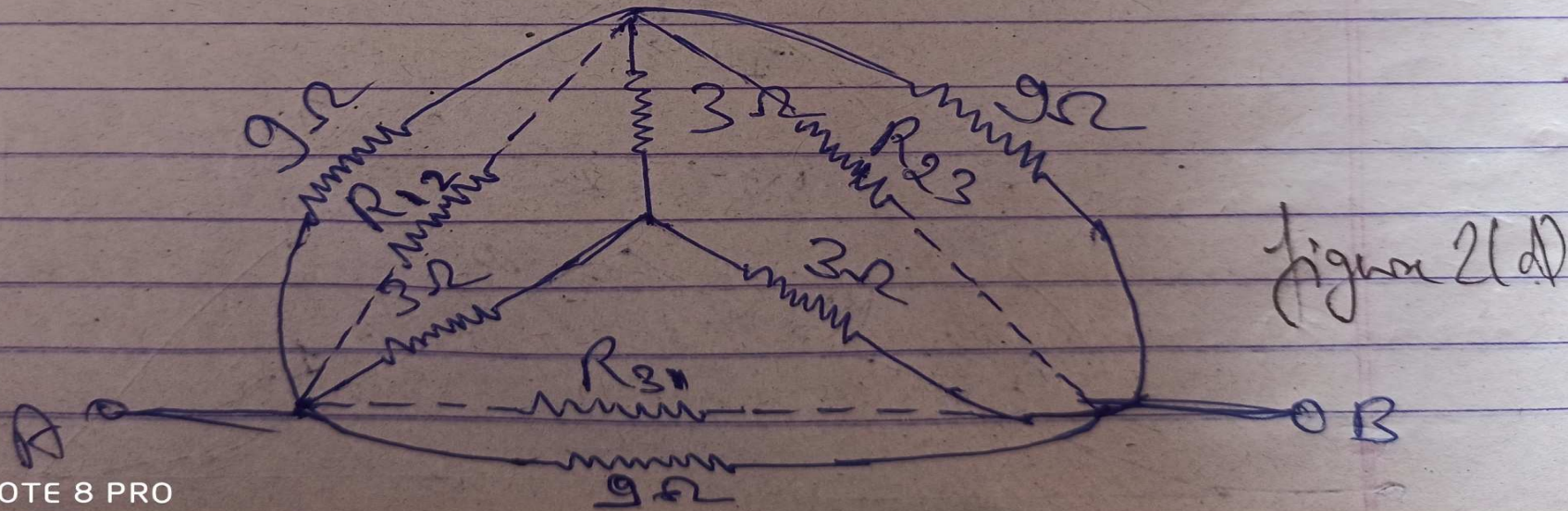


Figure 2(d)

Circuit Theorem

$$R_{12} = \frac{3 \times 3 + 3 \times 3 + 3 \times 3}{3} = \frac{27}{3} \Omega$$

Since all resistors have the resistance of same value so,

$$R_{12} = R_{23} = R_{31} = 9 \Omega$$

Now the n/w can be drawn like.

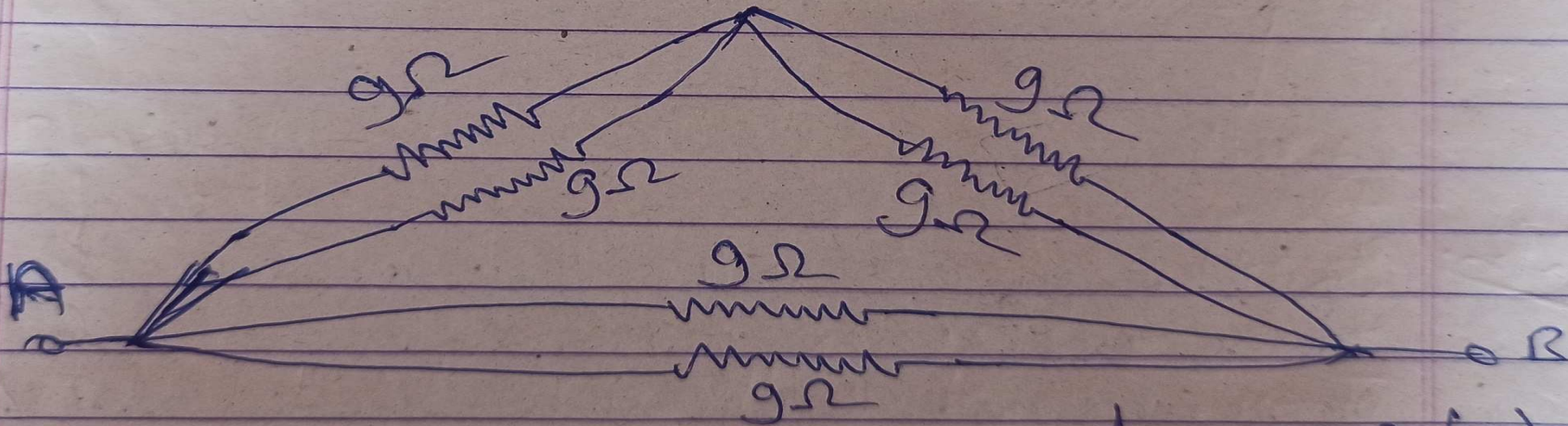



figure 2(e)

Circuit Theorem

Figure 2(e)

Now these are 3 || connection of
 9Ω & 9Ω resistors

$$\text{So } (9 || 9) = \frac{9 \times 9}{18} = 4.5\Omega$$

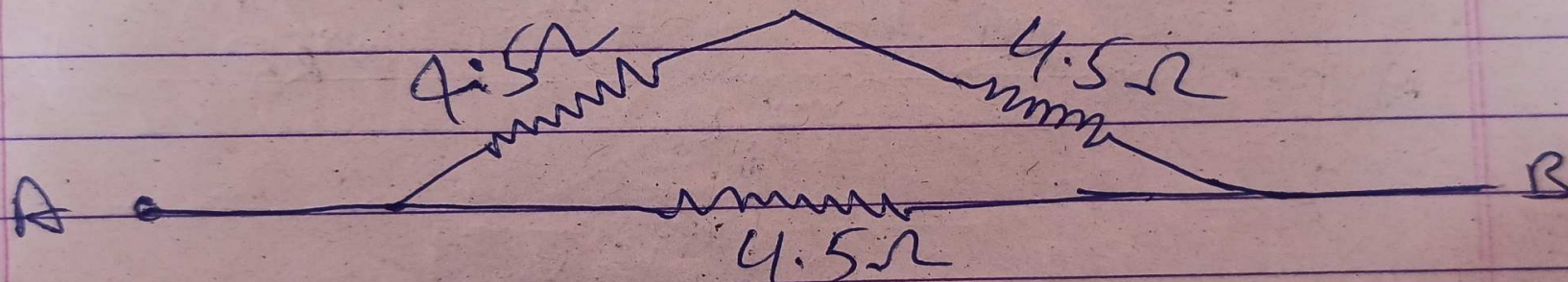


$$R_{eq} = (4.5 + 4.5)\Omega || 4.5\Omega$$

$$R_{eq} = 9\Omega || 4.5\Omega = \frac{9 \times 4.5}{13.5} = 3\Omega$$

Circuit Theorem

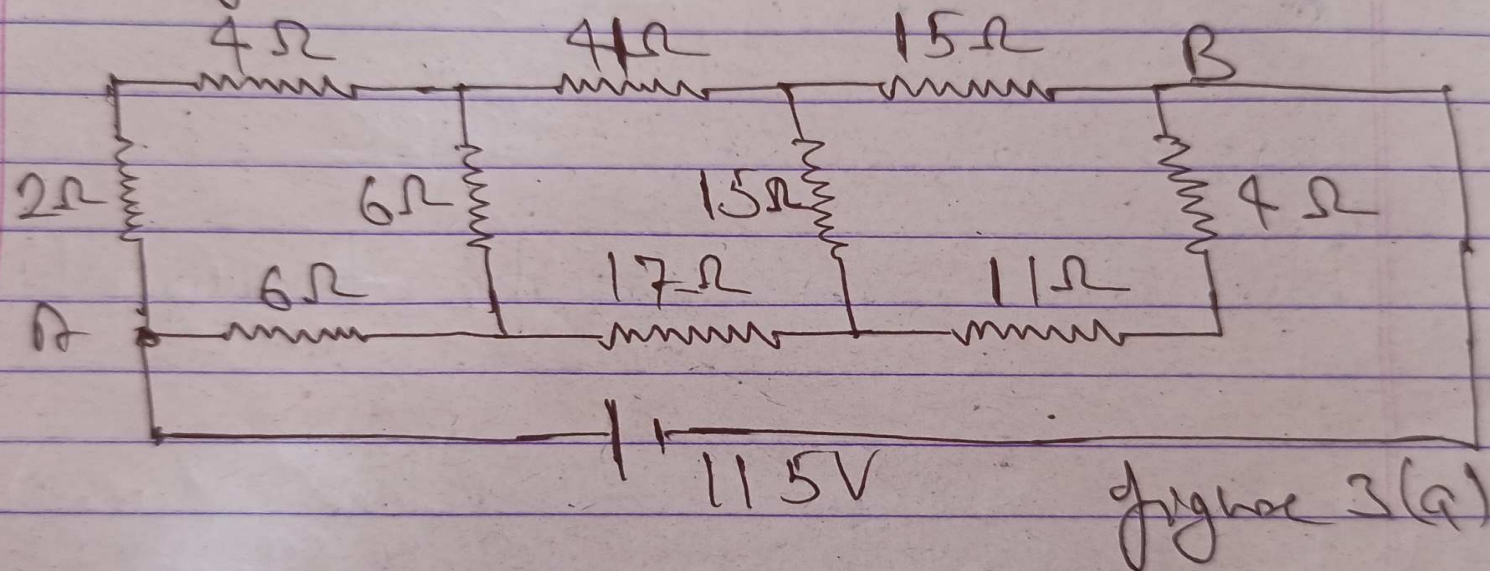
Example 5. Find the current in the $17\text{-}\Omega$ resistor in the network shown in figure 3(a) using star-delta transformation.



Soln. In the given n/w we observe that these ~~are~~ series combination of $2\text{ }\Omega$ & $4\text{ }\Omega$ are in series at left side and $4\text{ }\Omega$ & $11\text{ }\Omega$ are in series at right side so the

Circuit Theorem

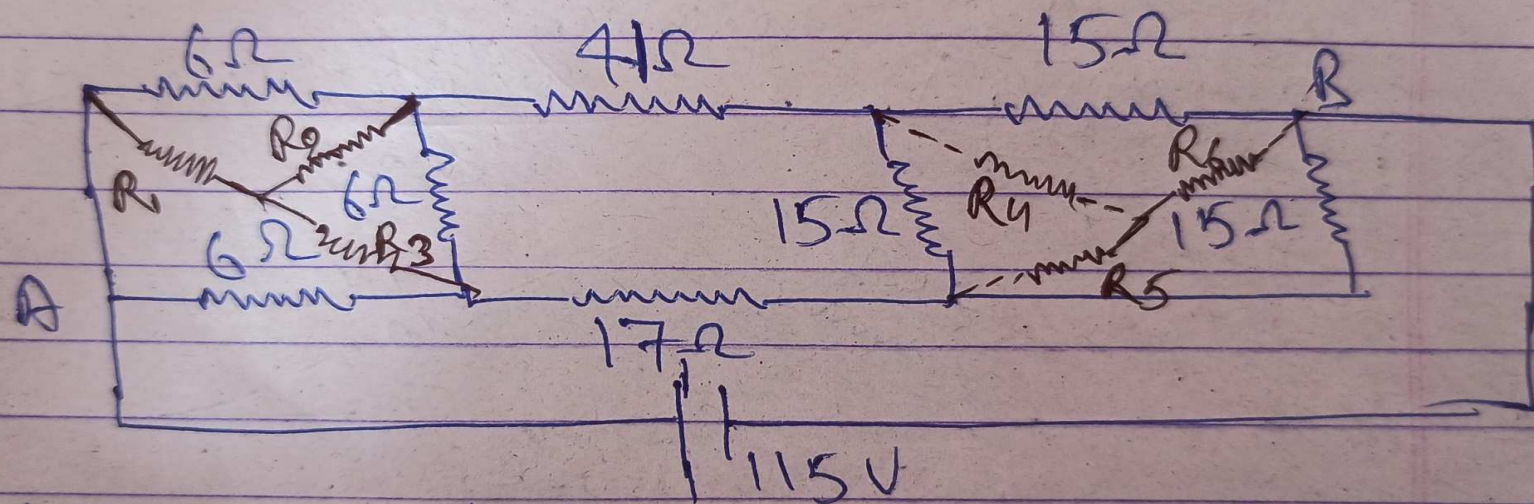these ~~two~~ series combination $2\ \Omega$ & $4\ \Omega$ are in series at left side and $4\ \Omega$ & $11\ \Omega$ are in series at right side so the n/w can be redrawn as,



We have 2 delta connections in the n/w or 4 star connections. Let us consider 2 delta connection and transforming this two delta connection to star connection.

Circuit Theorem

for 1st delta with 6Ω resistor each,
equivalent star connection will have
resistor value as,

$$R_1 = R_2 = R_3 = \frac{6 \times 6}{6 + 6 + 6} = \frac{36\Omega}{18} = 2\Omega$$


Now for 2nd delta with 15Ω resistor each,
equivalent star connection will have

$$R_4 = R_5 = R_6 = \frac{15 \times 15}{15 + 15 + 15} = \frac{15 \times 15}{45} = 5\Omega$$

Now the ckt. is like

Circuit Theorem

Now the ckt. is like.

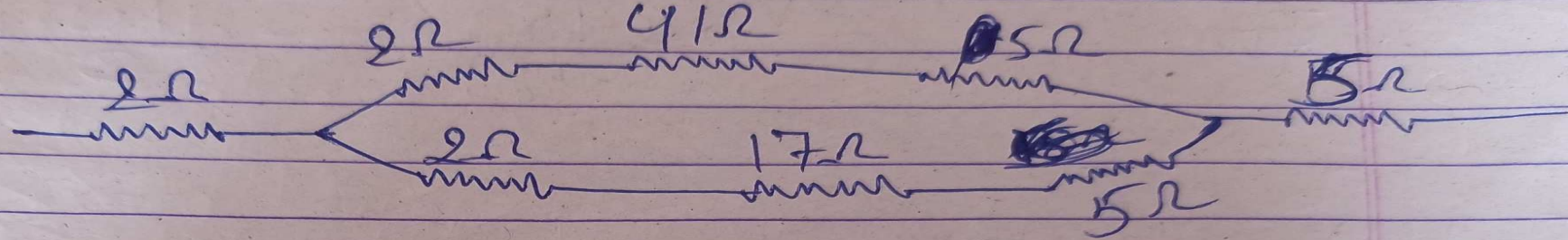


Now, 2Ω , 41Ω & 5Ω are in series so

$$(2 + 41 + 5) = 48\Omega$$

and also, 2Ω , 17Ω & 5Ω are in series so,

$$(2 + 17 + 5)\Omega = 24\Omega$$

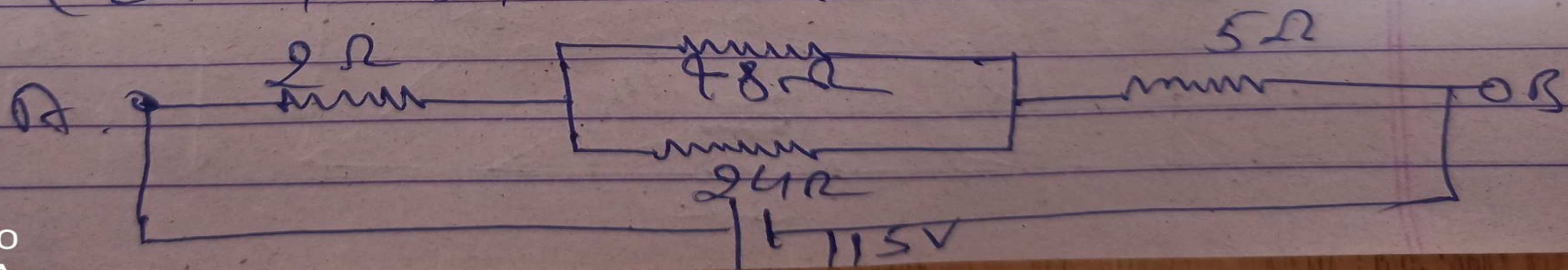

Circuit Theorem

$$R_{eq} = 2 + (24 || 48) + 5 \Omega$$

$$= 2 + \frac{24 \times 48}{(24 + 48)} + 5 \Omega$$

$$R_{eq} = 23 \Omega$$


$$I_{total} = \frac{115 V}{23 \Omega} = 5 A$$

Current through 17Ω resistor is current through the series connection of 2Ω , 17Ω and 5Ω i.e. 24Ω resistor.

$$I_{17} = I_{24} = \frac{5 \times 48}{(24 + 48)} = \frac{10}{3} = 3.33 A$$

Circuit Theorem

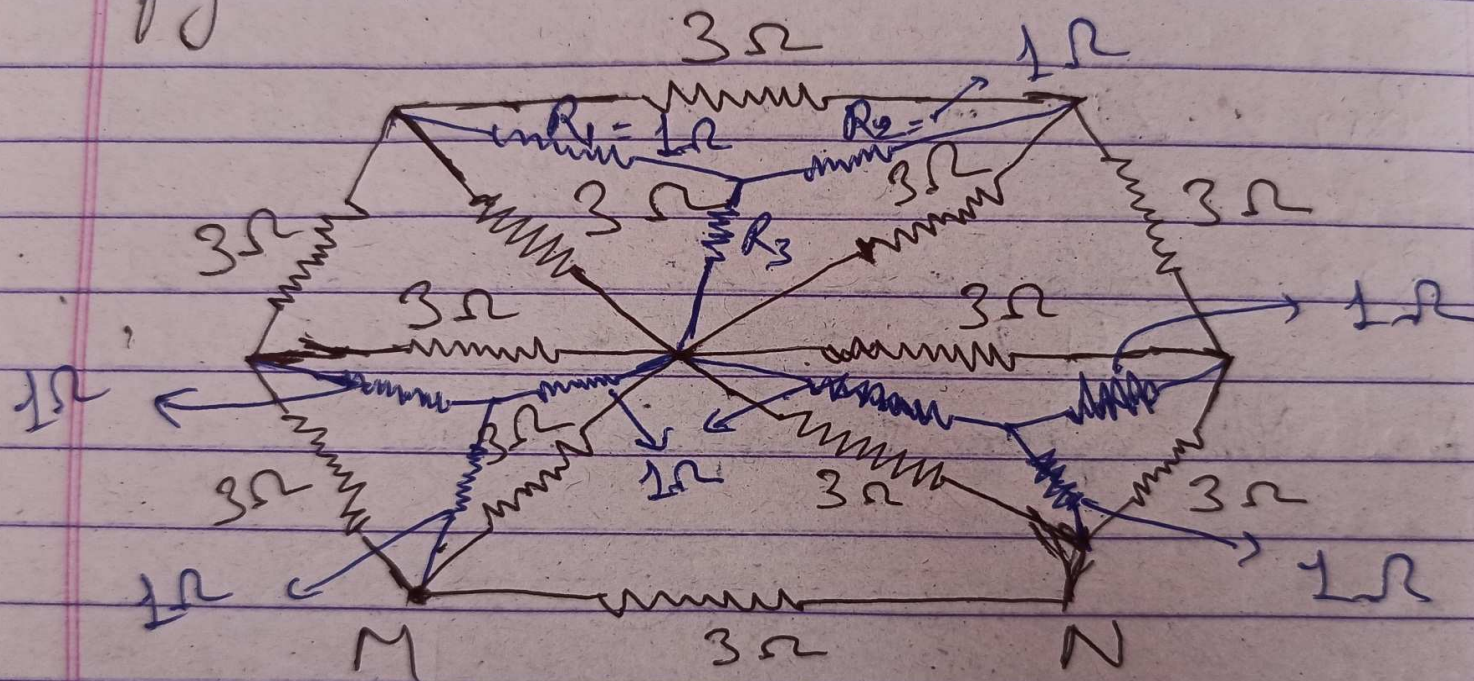Example 4) Find the total resistance between terminal MN of the n/w shown in figure 4(a)



also: Here we can observe that there is no

Circuit Theorem

Soln: Here we can observe that there is no series & || or connection of resistors. There are 6 delta connections of resistors.

To analyse the ckt we will consider ~~any~~ ³ alternate delta, at a time to transform into star connection.

As the value of all resistors are same so in ~~star~~ equivalent star connection the value of all ~~arms~~ resistors will be same for each star connection in each arm.

$$R_1 = R_2 = R_3 = \frac{3 \times 3}{3+3+3} = \frac{9}{3} = 1R$$

Circuit Theorem

connections. We will not consider series combination of the branch ^{MN} across which equivalent series resistor to be find out.

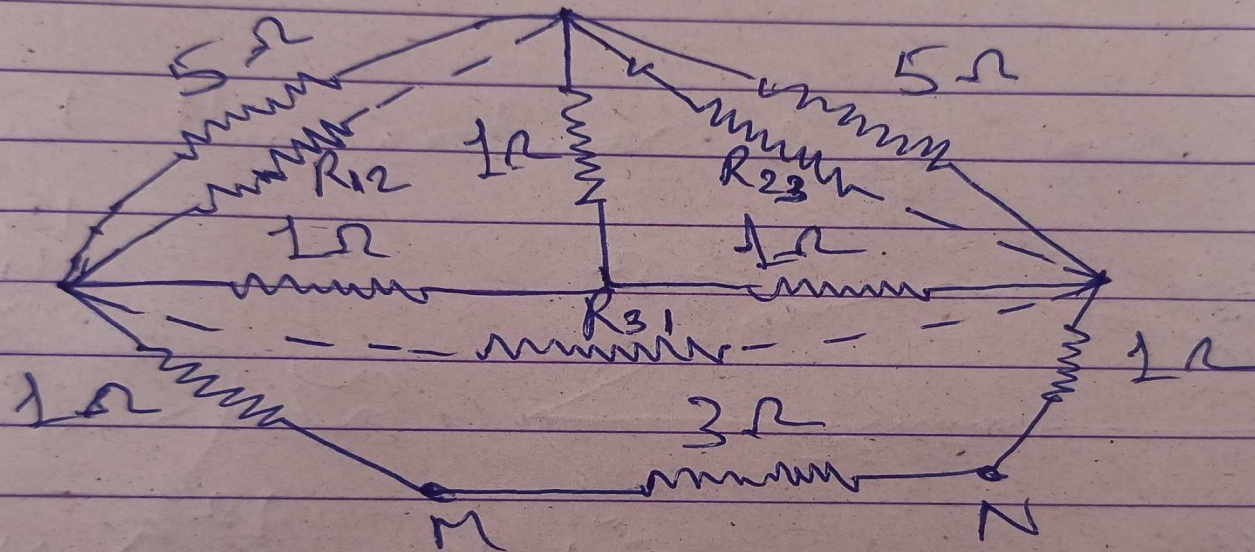


figure 4(c).


Now here we can observe a star ^{connection} inside the n/w. So we convert this star to delta connection. As each branch of star has $1R$ resistor so it's equivalent delta will have

Circuit Theorem

delta connection with all three resistors having same value.

$$R_{12} = R_{23} = R_{31} = \frac{1 \times 1 + 1 \times 1 + 1 \times 1}{1} = 3R$$

Now the n/w can be drawn as below.

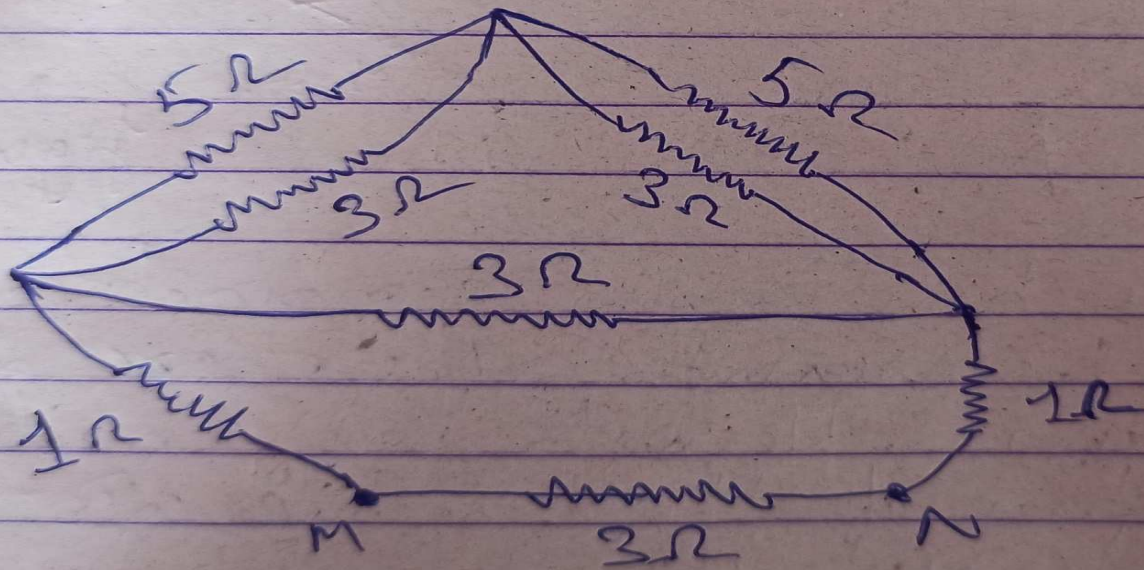

Here 5Ω & 3Ω are in parallel and there are 2 such connections.

$$\text{So } (5 \parallel 3) = \frac{5 \times 3}{8} = \frac{15R}{8}$$

Circuit Theorem

figure 4(d)

These two $\frac{15}{8} \Omega$ resistors will be in series.

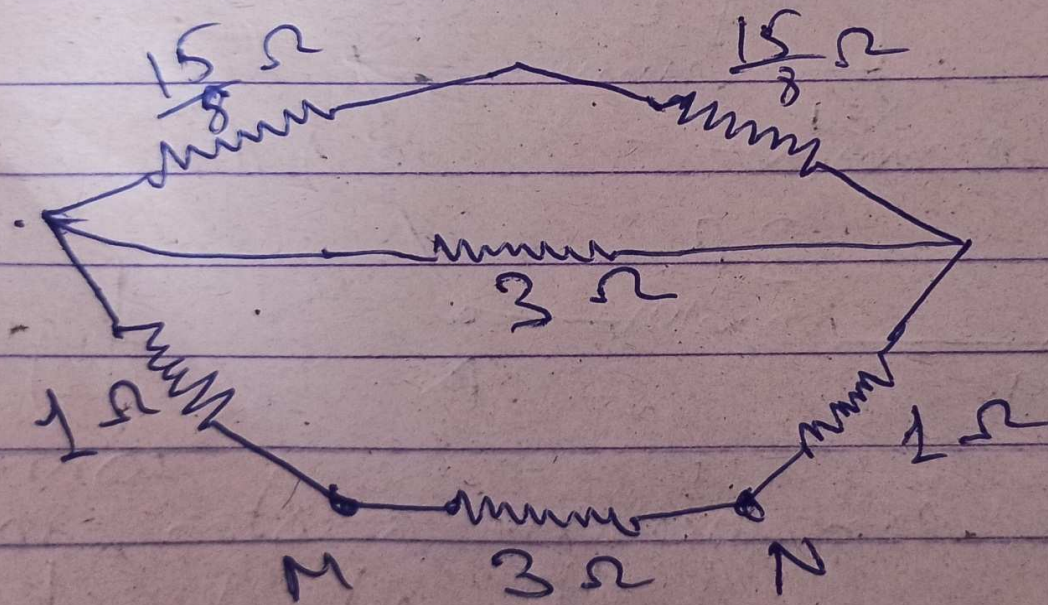


figure 4(e)


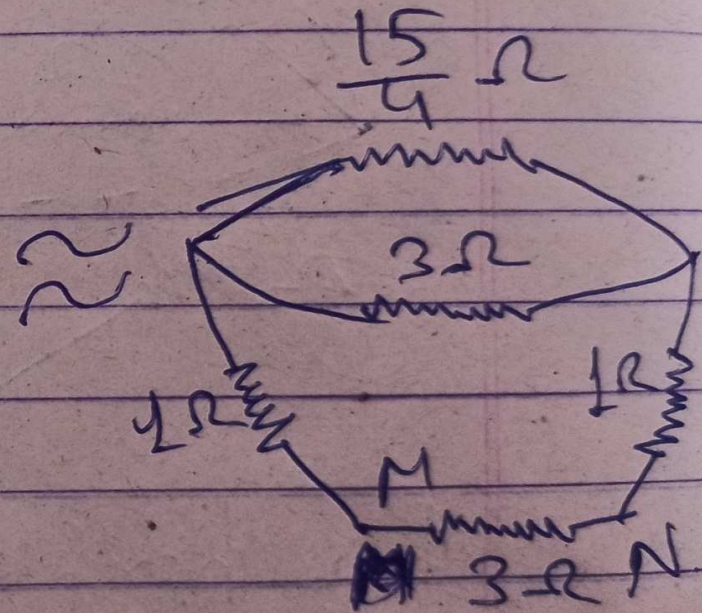


figure 4(f)

Circuit Theorem

Now $\left(\frac{15}{4} \Omega \text{ \& } 3\Omega\right)$ are in $||$. So,
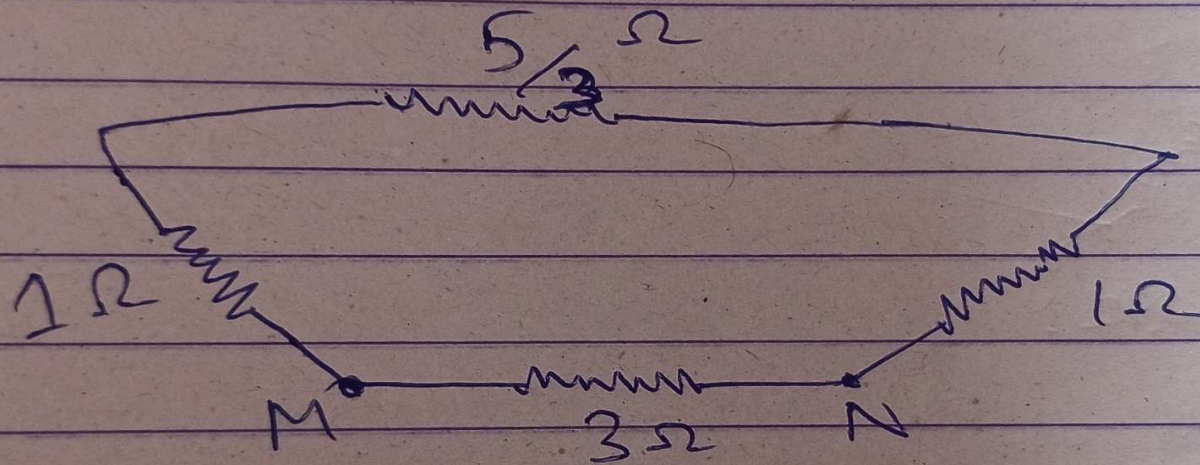
$$\frac{\frac{15}{4} \times 3}{\frac{15}{4} + 3} = \frac{45}{4} = \frac{45 \cdot 05}{27 \cdot 3}$$




Now $\frac{5}{3}\Omega$, 1Ω & 1Ω will be series

Circuit Theorem

Now $\frac{5}{3}\Omega$, 1Ω & 1Ω will be series
as to find Req for terminal M & N, and
this whole series combination is in || to
to 3Ω of MN branch.

$$\frac{5}{3} + 2 = \frac{11}{3}\Omega$$

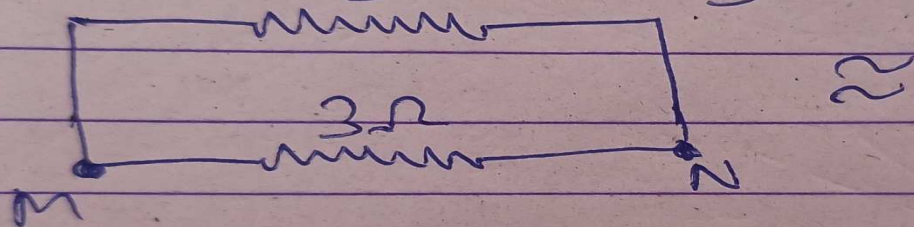

$$\begin{aligned} \text{Req} &= \left(3\Omega \parallel \frac{11}{3}\Omega \right) = \frac{3 \times \frac{11}{3}}{3 + \frac{11}{3}} \\ &= \frac{11 \times 3}{20} \\ &= \frac{33}{20} \Omega = 16.5\Omega \end{aligned}$$

Circuit Theorem

In next lecture we start next chapter. For any query or problem discuss on What's App or contact on number available.

THANK YOU