

**Paper 1, TDC Part-1**  
**Chapter– 4, Circuit Theorems**  
**Lecture - 4**

**By:**

**Mayank Mausam**

**Assistant Professor (Guest Faculty)**

**Department of Electronics**

**L.S. College, BRA Bihar University,**

**Muzaffarpur, Bihar**

# Circuit Theorem

- In previous lectures we have discussed “Thevenin’s Theorem” and did one examples. Today we will see some problems based on Thevenin’s theorem

Questions based on thevenin's theorem

Q2) Find the current in  $8\Omega$  resistor using Thevenin's theorem:

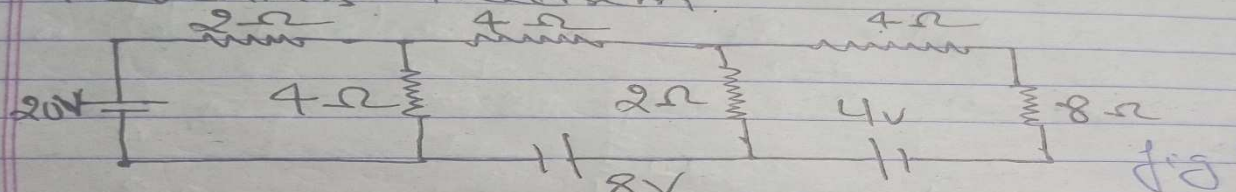


fig B(1)

Soln. To find the current in the  $8\Omega$  we will remove the  $8\Omega$  resistor from ckt and redraw it.


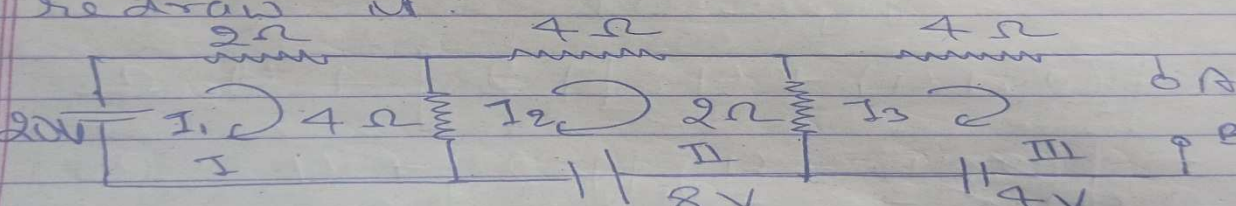



fig B(2)

Detailed description of the handwritten solution: The problem asks to find the current in an  $8\Omega$  resistor using Thevenin's theorem. The circuit in fig B(1) consists of a  $20V$  DC source on the left. A  $2\Omega$  resistor is in series with the source. This is followed by a  $4\Omega$  resistor connected in parallel to the common ground. The circuit then continues with a  $4\Omega$  resistor in series, followed by another  $4\Omega$  resistor in parallel to ground. Next is a  $2\Omega$  resistor in series, followed by a  $4V$  DC source in parallel to ground. Finally, an  $8\Omega$  resistor is connected in parallel to ground. An  $8V$  source is also indicated in parallel to ground between the two  $4\Omega$  resistors. The solution involves removing the  $8\Omega$  resistor and redrawing the circuit as shown in fig B(2). In this redrawn circuit, the  $8\Omega$  resistor is replaced by an open circuit labeled '0A'. The current through the  $4\Omega$  resistor is labeled  $I_1$ , the current through the  $2\Omega$  resistor is labeled  $I_2$ , and the current through the  $4\Omega$  resistor is labeled  $I_3$ . The  $8V$  and  $4V$  sources are also shown in parallel to ground.

# Circuit Theorem

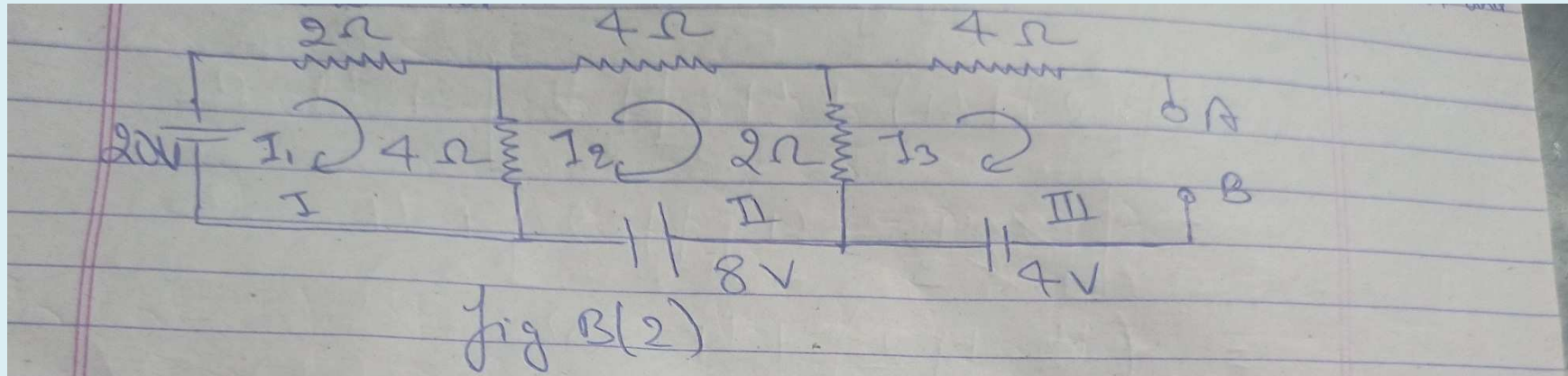

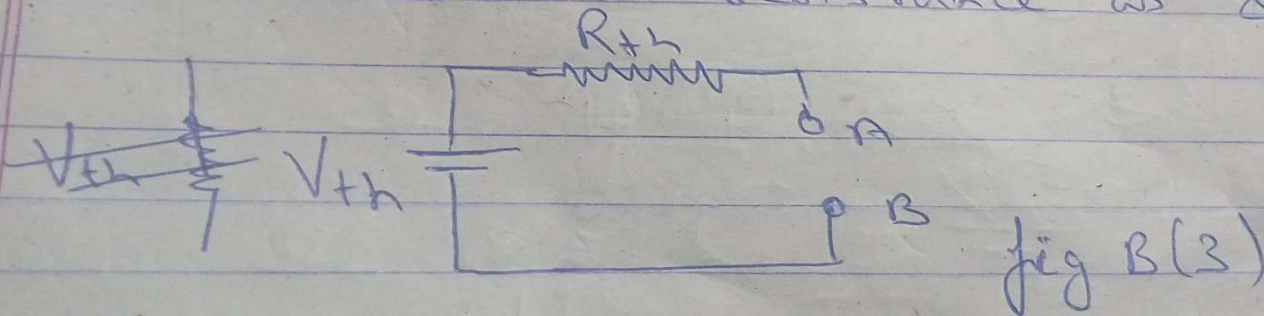Now the ckt of figure B(2) can be replaced or considered as thevenin's voltage in series with thevenin's resistance as shown below



To find the  $R_{th}$  we look into the from the terminals AB in figure B(2) and short

# Circuit Theorem

Circuit the <sup>all</sup> voltage sources and open circuit the current sources. (There is no current sources so there will be no open circuit)

To calculate  $R_{th}$  we red draw ckt as below

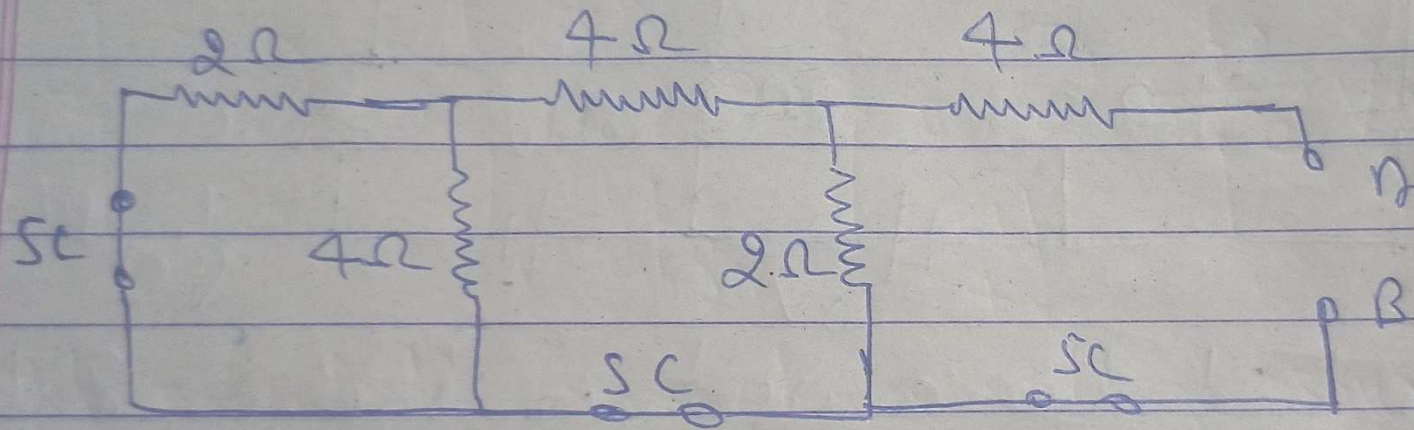


Figure B(4)

# Circuit Theorem

$$R_{th} = \left[ \left\{ (2 \parallel 4) + 4 \right\} \parallel 2 \right] + 4 \Omega$$

$$= \left[ \left( \frac{2 \times 4}{2+4} + 4 \right) \parallel 2 \right] + 4 \Omega$$

$$= \left( \frac{16}{3} \parallel 2 \right) + 4 \Omega$$

$$= \frac{(16 \times 2)}{3} + 4 \Omega$$

$$\frac{16}{3} + 2$$

$$= \frac{16 \cancel{2} / \cancel{3}}{11 \cancel{2} / \cancel{3}} + 4 \Omega$$

$$= \frac{60}{11} \Omega$$

$$R_{th} = \frac{60}{11} \Omega$$

# Circuit Theorem

Now we calculate  $V_{th}$ , for that we will find out different loop current or branch current of ckt shown in figure B(2).

As shown in figure B(2), current  $I_3$  in loop 3 will be zero because the loop is open so no current flow in that loop.

$$I_3 = 0 \text{ A.}$$

Now considering loop 1 of figure B(2) we will write loop eqn. as per KVL.

$$-20V + 2I_1 + 4I_1 - 4I_2 = 0$$

$$6I_1 - 4I_2 = 20$$

$$3I_1 - 2I_2 = 10 \quad \text{--- (i)}$$

# Circuit Theorem

$$6I_1 - 4I_2 = 20$$

$$3I_1 - 2I_2 = 10 \quad \text{--- (i)}$$

Considering loop 2 now of figure B(2).

$$4I_2 + 2I_2 + 4I_2 - 4I_1 + 8 = 0$$

$$-4I_1 + 10I_2 = -8$$

$$-2I_1 + 5I_2 = -4 \quad \text{--- (ii)}$$

Solving eqn. (i) & (ii) as below.

$$6I_1 - 4I_2 = 20$$

$$\underline{-6I_1 + 15I_2 = -12}$$


$$11I_2 = 8$$

$$I_2 = \frac{8}{11} \text{ A}, \quad I_1 = \frac{10 + (2 \times \frac{8}{11})}{3}$$
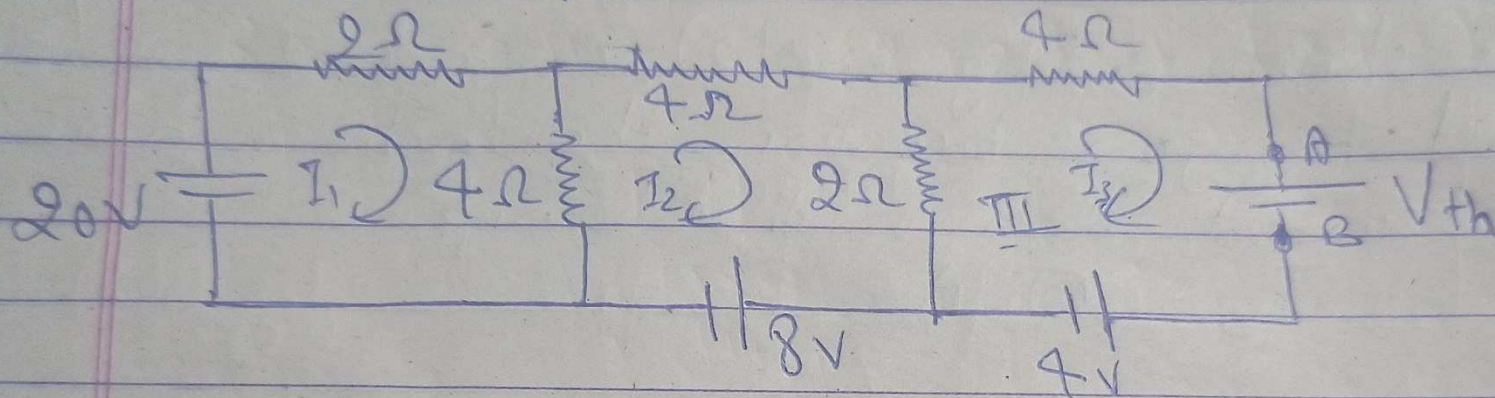
# Circuit Theorem

$$I_1 = \frac{110 + 16}{11 \times 3} = \frac{126}{11 \times 3} = \frac{42}{11} \text{ A}$$

Now we again redraw the ckt of figure B(2) to show  $V_{th}$ .



We ~~calculate~~ connect a voltage source  $V_{th}$  at the terminal A and B solve the loop 3 Now to calculate  $V_{th}$ .

As  $I_3 = 0$ ,  $I_2 = \frac{8}{11} \text{ A}$  so we


# Circuit Theorem

can write KVL for loop 3 as below

$$4\Omega \times 0 + V_{th} - 4V - 2 \times \frac{8}{11} = 0$$

$$V_{th} = 0 + 4 + \frac{16}{11} = \frac{60}{11} \text{ V}$$

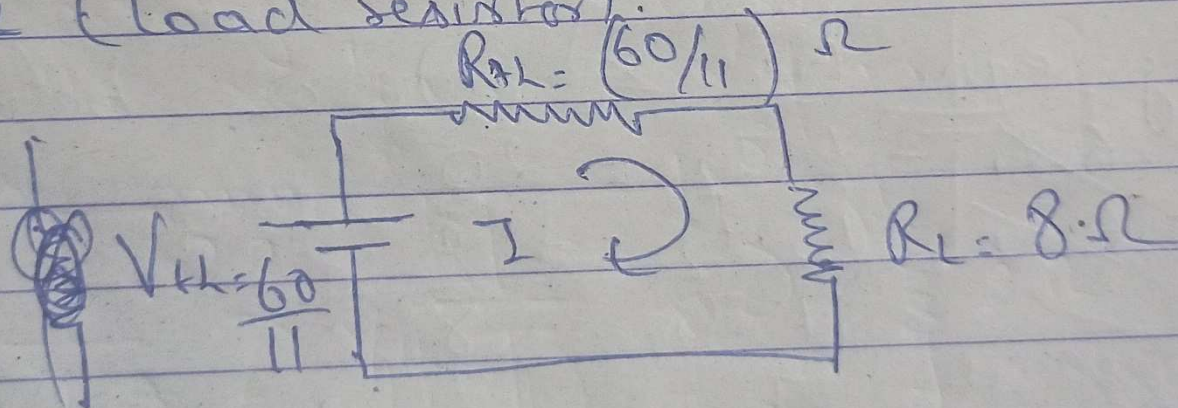So now the ckt of figure B(2) can be replaced by ckt of figure B(3) to find out current in  $8\Omega$  (load resistor).



# Circuit Theorem

$I_L$  i.e. current through load resistance  $R_L$  is


$$I_L = \frac{V_{th}}{(R_{th} + R_L)} = \frac{60/11}{\left(\frac{60}{11} + 8\right)} = \frac{60/11}{148/11} \text{ A}$$

$$= \frac{15}{37} \text{ A}$$

So the current through  $8\Omega$  resistor is  $\frac{15}{37} \text{ A}$ .

# Circuit Theorem

Q3)

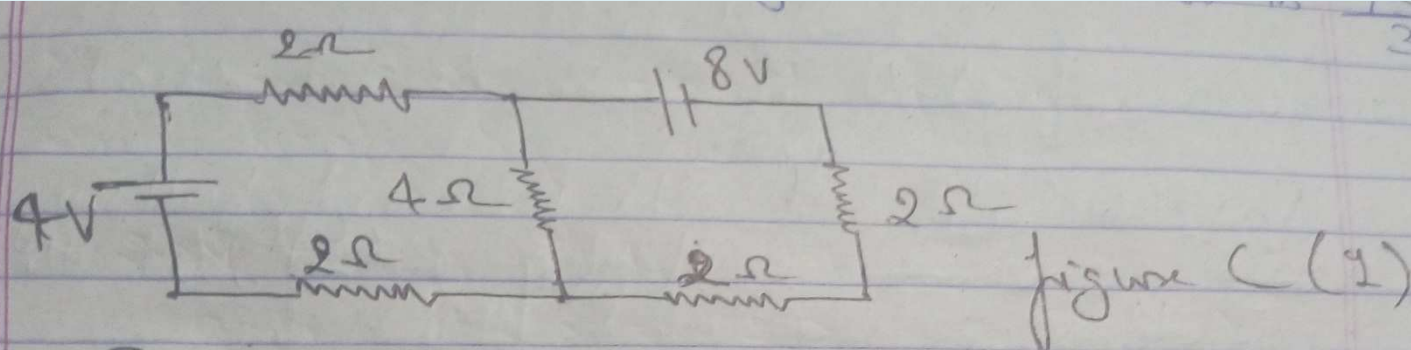

Find current in  $4\Omega$  resistor. using thevenin's theorem.

Sol. Here ~~8Ω~~  $4\Omega$  resistor is load resistor because we have to find current in this resistor. , we draw the ckt as per thevenin's theorem as below.

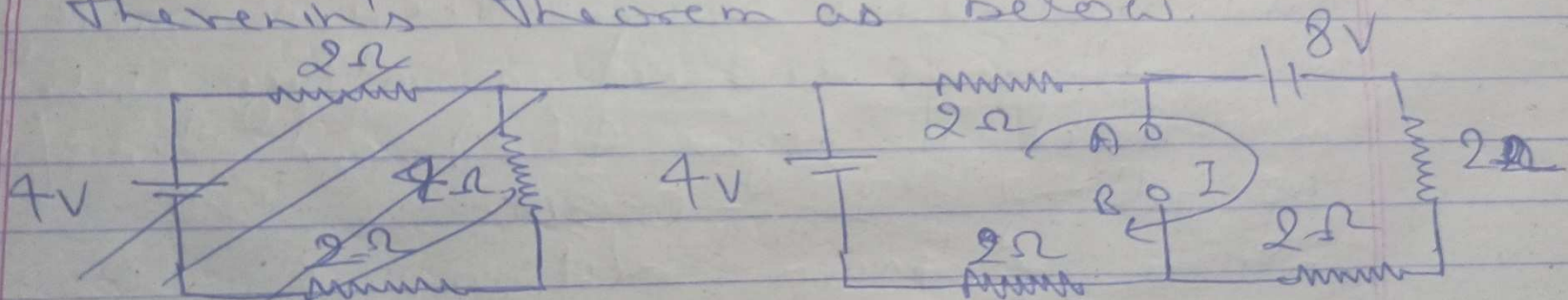


fig (2)

# Circuit Theorem

Soln. Here ~~8Ω~~  $4\Omega$  resistor is load resistor because we have to find current in this resistor, we draw the ckt as per theorem's theorem as below.


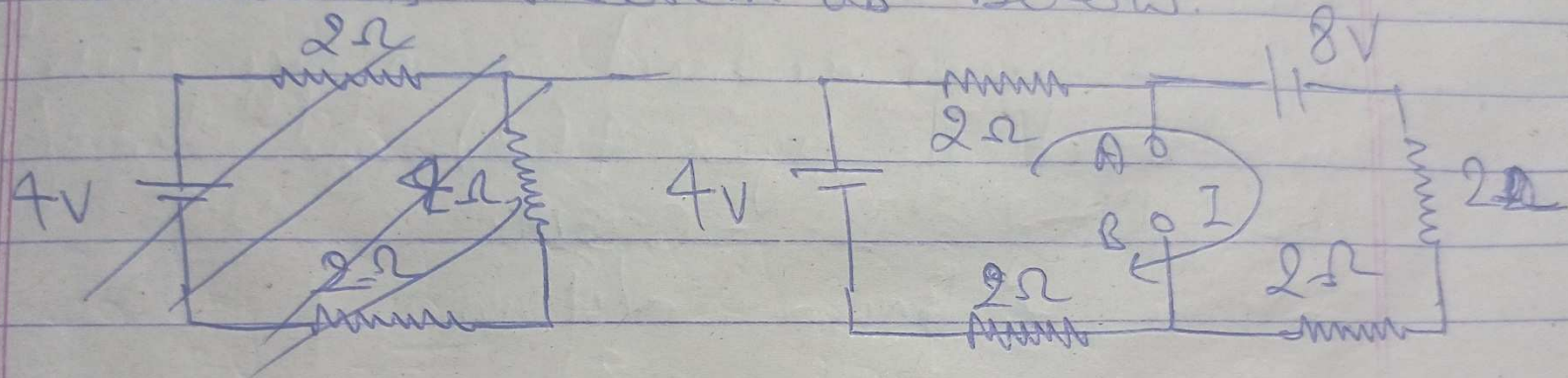


Fig (2)

find  $R_{th}$ , i.e. we will calculate  $R_{th}$  first. for that we will short the voltage sources of figure (2) and redraw the ckt. as in figure (3).

# Circuit Theorem

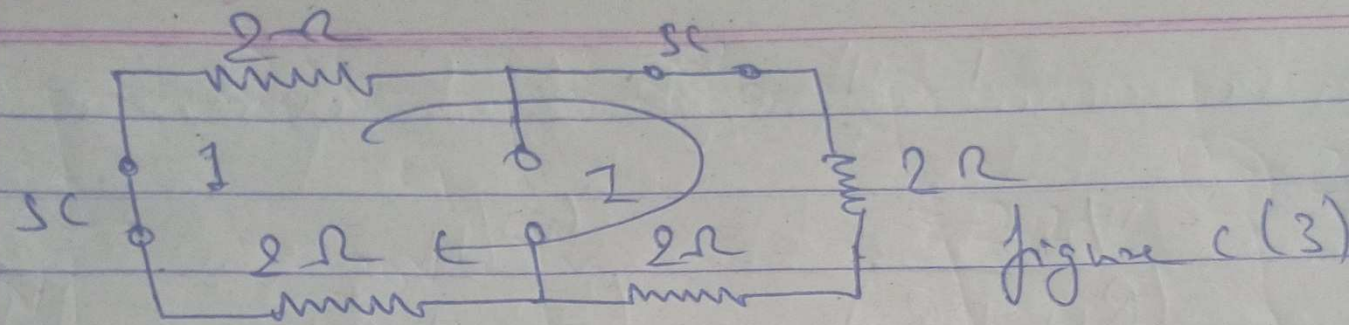

$$R_{th} = \cancel{2\Omega} \left[ (2+2) \parallel (2+2) \right] \Omega$$

$$= (4 \parallel 4) \Omega$$

$$= \frac{4 \times 4}{4+4} = 2 \Omega$$

$$R_{th} = 2 \Omega$$

Now we will find the current following in the ckt as shown in figure c (2), let the current  $I$  flow in the ckt. then



# Circuit Theorem

We can find  $V_{th}$  by taking any one of the loop because both loop contain  $V_{th}$ .

Let us consider loop 1. The writing KVL we will have.

In loop 1.

$$2x - 0.5 + V_{th} + 2x - 0.5 + -4 = 0$$

$$-1 + V_{th} + 1 - 4 = 0$$

$$V_{th} = 6 \text{ V}$$

Or,

through loop 2.


$$8 + 2x - 0.5 + 2x - 0.5 - V_{th} = 0$$

# Circuit Theorem

$$8 - 1 - 1 - V_{th} = 0$$
$$V_{th} = 6 \text{ V}$$

So we see that value of  $V_{th}$  is same by taking any loop.

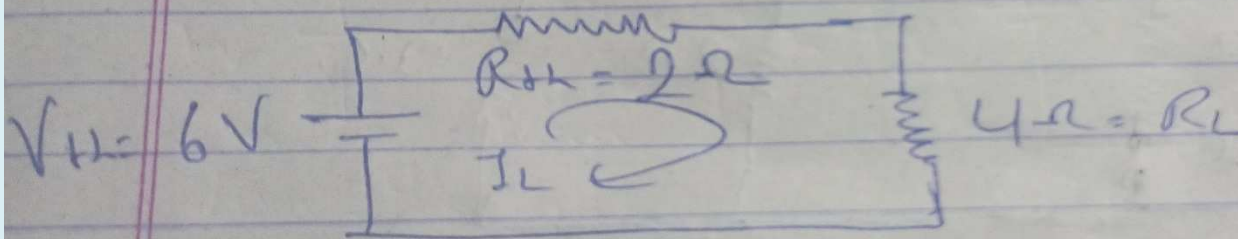Now drawing thevenin equivalent ckt to find current through load resistor  $4\Omega$



$$I_L = \frac{V_{th}}{(R_{th} + R_L)} = \frac{6}{(2+4)} = 1 \text{ A}$$

ans

# Circuit Theorem


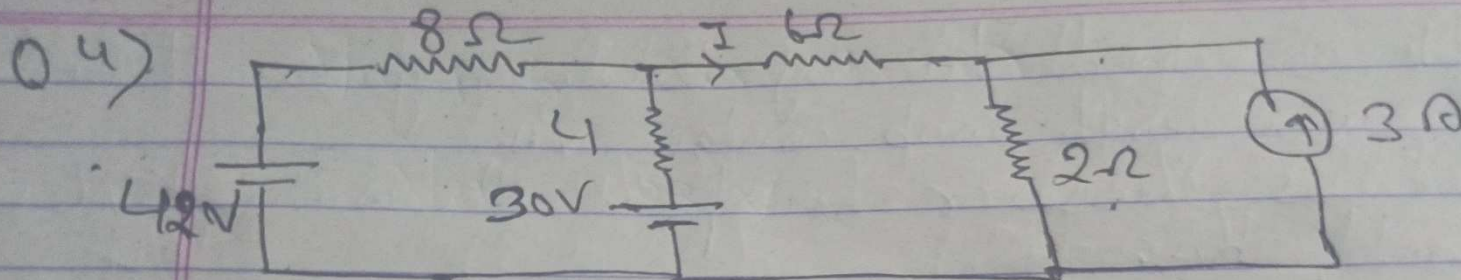


Fig D(1)  
Find current in 6Ω resistor.

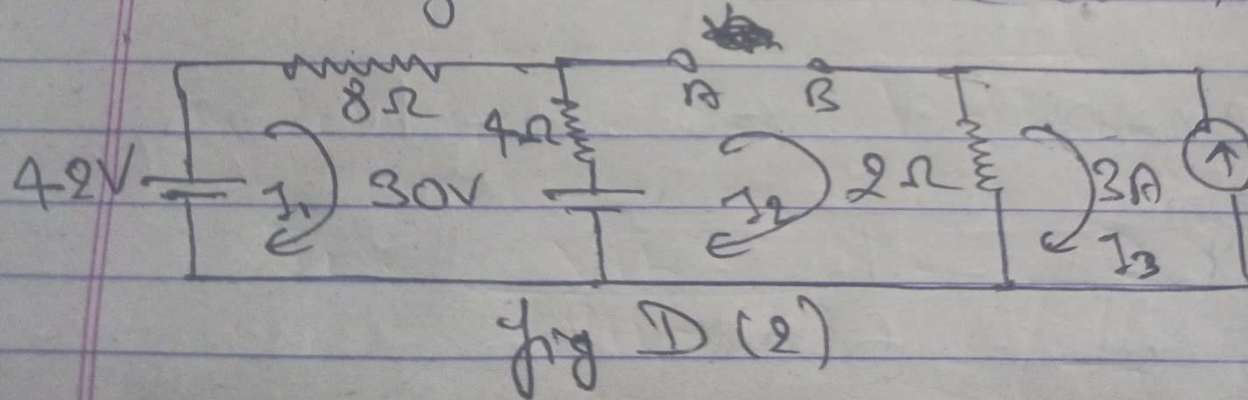Soln - We will apply thevenin theorem in the above ckt: for that we will draw the ckt by removing load resistance (6Ω) resistor.



# Circuit Theorem

We will calculate  $R_{th}$  first, for that short circuiting the voltage source and open circuit the current source. the drawing the ckt as shown in figure D (3).

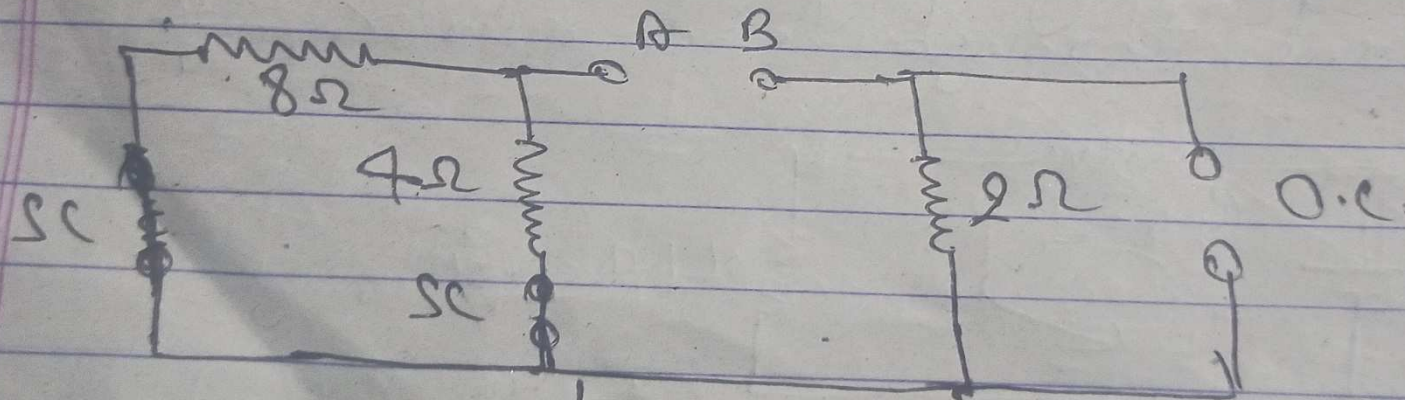


figure D (3)


So

$$R_{th} = (8 \parallel 4) + 2 = \frac{8 \times 4}{8 + 4} + 2$$
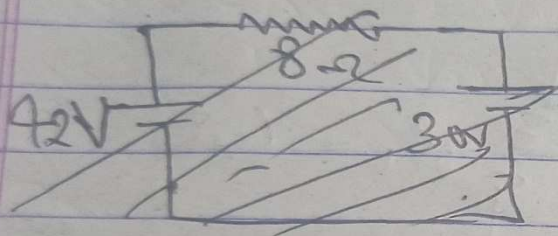
# Circuit Theorem

$$R_{th} = \frac{14}{3} \Omega$$

Now we will calculate  $V_{oc}$  as below, first we will find currents in different loop of ckt shown in figure D(2).



In loop 1, we have KVL

$$8I_1 + 4I_1 + 30 - 42 = 0$$

$$12I_1 - 12 = 0$$

$$I_1 = \frac{12}{12} = 1A$$


In loop 2,  $I_2 = 0$  as it is open loop and in loop 3,

$$I_3 = -3A$$
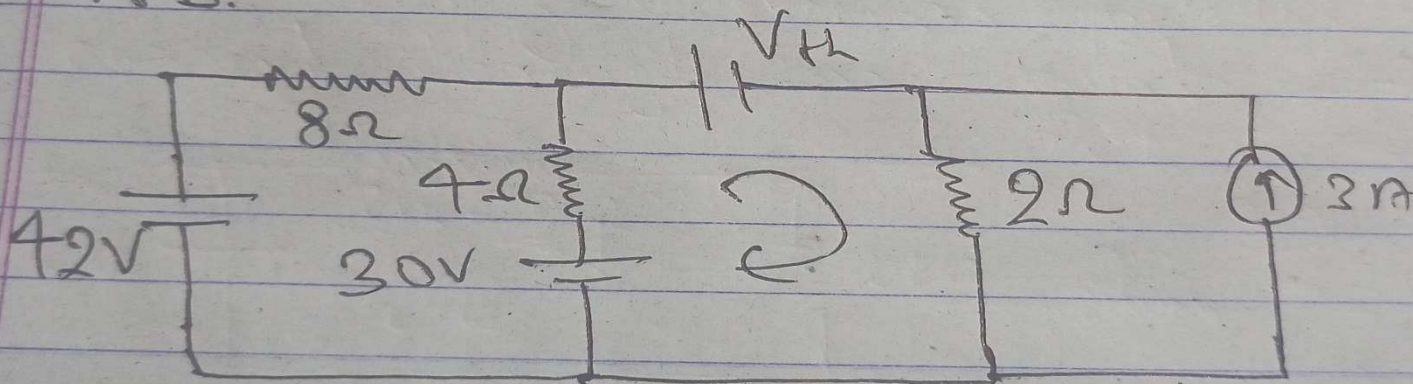
# Circuit Theorem

In loop 2,  $I_2 = 0$  as it is open loop.  
and in loop 3,  
 $I_3 = -3A$ .

Now redrawing the ~~ckt~~ ckt of figure D(2)  
as below with  $V_H$  connected at terminal  
AB.



Applying KVL in loop 2 we have


$$V_H + (2 \times 3) - 30V - (4 \times 1) = 0$$

# Circuit Theorem

$$V_{th} + 6 - 30 - 4 = 0$$

$$V_{th} = 28 \text{ V}$$

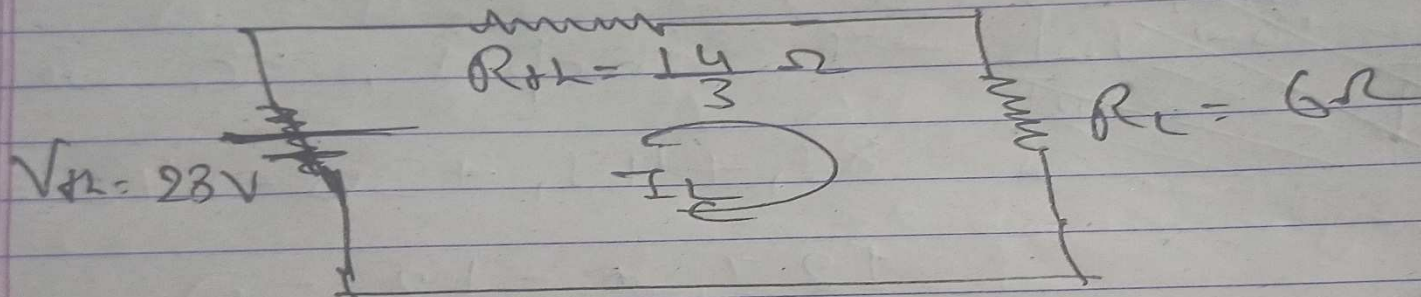So thevenin's equivalent circuit is as below



So let  $I_L$  is current through  $6\Omega$  resistor

$$I_L = \frac{V_{th}}{(R_{th} + R_L)} = \frac{28}{\left(\frac{14}{3} + 6\right)} \text{ A}$$

$$= \frac{28 \times 3}{(14 + 18)} = \frac{7 \times 28 \times 3}{8 \times 22} \text{ A}$$

$$= \frac{21}{8} \text{ A}$$