

Paper 7, TDC Part-3
Chapter– 4, Combinational Logic Design
Lecture - 11

By:

Mayank Mausam

Assistant Professor (Guest Faculty)

Department of Electronics

L.S. College, BRA Bihar University,

Muzaffarpur, Bihar

Combinational Logic Design

⊛ Minimisation of Logic Functions Not specified in Minterms/Maxterms

Here we consider the cases where the functions are not specified in canonical forms. If the logic function is not specified in canonical form then we should 1st convert the logic function expression in canonical form. Then map the function into the K-map and minimise. Alternately, we can directly prepare K-map using the following algorithm:

Combinational Logic Design


1. Enter ones for minterms and zeros for maxterms.
2. Enter a pair of ones/zeros for each of the terms with one variable less than the total number of variables.
3. Enter 4 adjacent ones/zeros for terms with two variable less than the total number of variables.
4. Repeat for other terms in the similar way.
5. Once the logical function is mapped into the K-map, the minimisation procedure is

Combinational Logic Design

same as discussed earlier.

Ex-1) Minimise the 4 variable logic function
 $f(A, B, C, D) = \bar{A}\bar{B}CD + A\bar{B}\bar{C}D + ABCD +$
 $A\bar{B}\bar{C} + AB\bar{C} + \bar{B}\bar{D} + \bar{D}$

Soln →

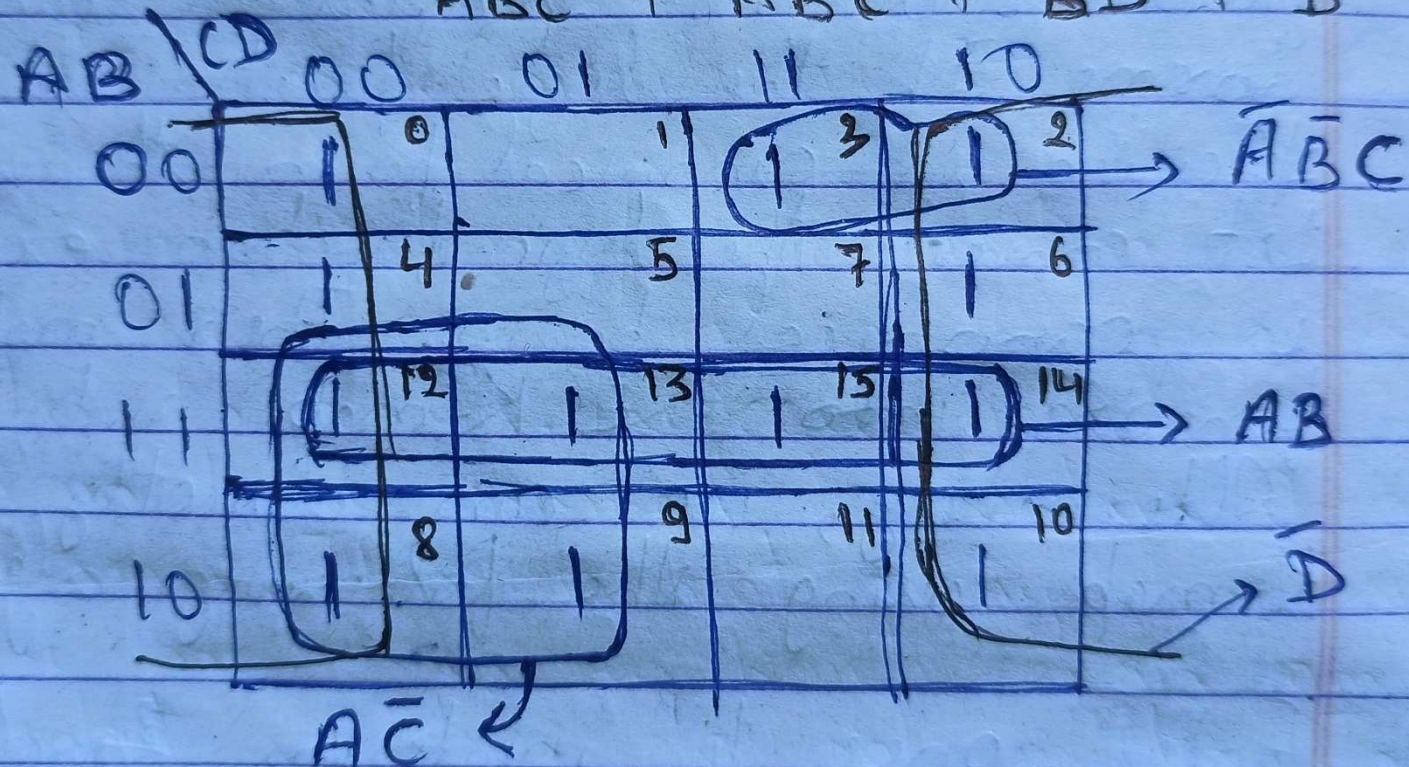

Combinational Logic Design

$A\bar{C}$ ←

$\bar{A}\bar{B}CD$ corresponds to cell $0011 \rightarrow 3$
 $A\bar{B}\bar{C}D$ " " " $1001 \rightarrow 9$
 $AB\bar{C}D$ " " " $1111 \rightarrow 15$
 $A\bar{B}\bar{C}$ " " " 2 cells ~~0000~~ 1000 & 1001
i.e. 8 & 9 resp.

$AB\bar{C}$ corresponds to 2 cells 1100 & 1101
i.e. 12 & 13 resp.

$B\bar{D}$ corresponds to 4 cells $0100, 0110,$
 1100 & 1110 i.e. 4, 6, 12 & 14
resp.

\bar{D} corresponds to 8 cells $0000, 0010, 0100,$
 $0110, 1000, 1010, 1100$ & 1110
i.e. 0, 2, 4, 6, 8, 10, 12 & 14

Combinational Logic Design

The minimized expression for the given logic function is,

$$f(A, B, C, D) = \bar{A}\bar{B}C + AB + A\bar{C} + \bar{D}$$

Eg-2 Minimise the 4 variable logic function.

$$f(A, B, C, D) = (A+B+\bar{C}+\bar{D})(\bar{A}+\bar{B}+C)(A+B+\bar{D})(\bar{B}+C)(A)$$

Soln:

AB \ CD	00	01	11	10
00	0	0	0	0
01	0	0	0	0
11	0	0		
10				

The Karnaugh map shows a 2x2 square of 0s in the first two rows (AB=00 and 01) for CD=00 and 01, which is labeled \bar{A} .
 Another 2x2 square of 0s is in the first two rows for CD=11 and 10, which is labeled \bar{D} .
 A 2x2 square of 0s is in the first two rows for CD=00 and 01, which is labeled $(\bar{B}+C)$.

Combinational Logic Design

Maxterm $(A+B+\bar{C}+\bar{D})$ corresponds to cell $0011 \rightarrow '3'$
" $(\bar{A}+\bar{B}+C)$ corresponds to 2 cells $'1100$ &
 $1101'$ i.e. $'12$ & $13'$

Maxterm $(A+B+\bar{D})$ corresponds to 2 cells $'0001$ & $0011'$
i.e. $'1$ & $3'$

Maxterm $(\bar{B}+C)$ corresponds to 4 cells $'0100, 0101,$
 1100 & $1101'$ i.e. $'4, 5, 12$ & $13'$

Maxterm (A) corresponds to 8 cells $'0000, 0001, 0010,$
 $0011, 0100, 0101, 0110$ & $0111'$ i.e. $'0, 1, 2,$
 $3, 4, 5, 6$ & $7'$

Combinational Logic Design

The minimised expression for the given logic function as obtained from K-Map is

$$f(A, B, C, D) = A(\bar{B} + C)$$

DON'T - Case Conditions :-

For simplification of logic function using K-Map we make the entries in the map for either 1's or 0's. The cells which do not contain 1 are assumed to contain 0 and vice-versa. This is not always true since there are cases in which certain combination of input variables do not matter. In such

Combinational Logic Design


cases. The designer has a flexibility and it is left to him whether to assume a 0 or a 1 as output for each of these combinations. This condition is known as "don't-care" condition and can be represented on the K-map as a 'x' mark in the corresponding cell. The 'x' mark in the cell may be assumed to be a '1' or a '0' depending upon which one leads to a simpler expression. The function can be specified in one of the following ways:

- 1) In terms of minterms and don't-care condition.
For example.

$$f(A, B, C, D) = \sum m(5, 6, 10, 13, 15) + d(7, 8, 4)$$

Combinational Logic Design

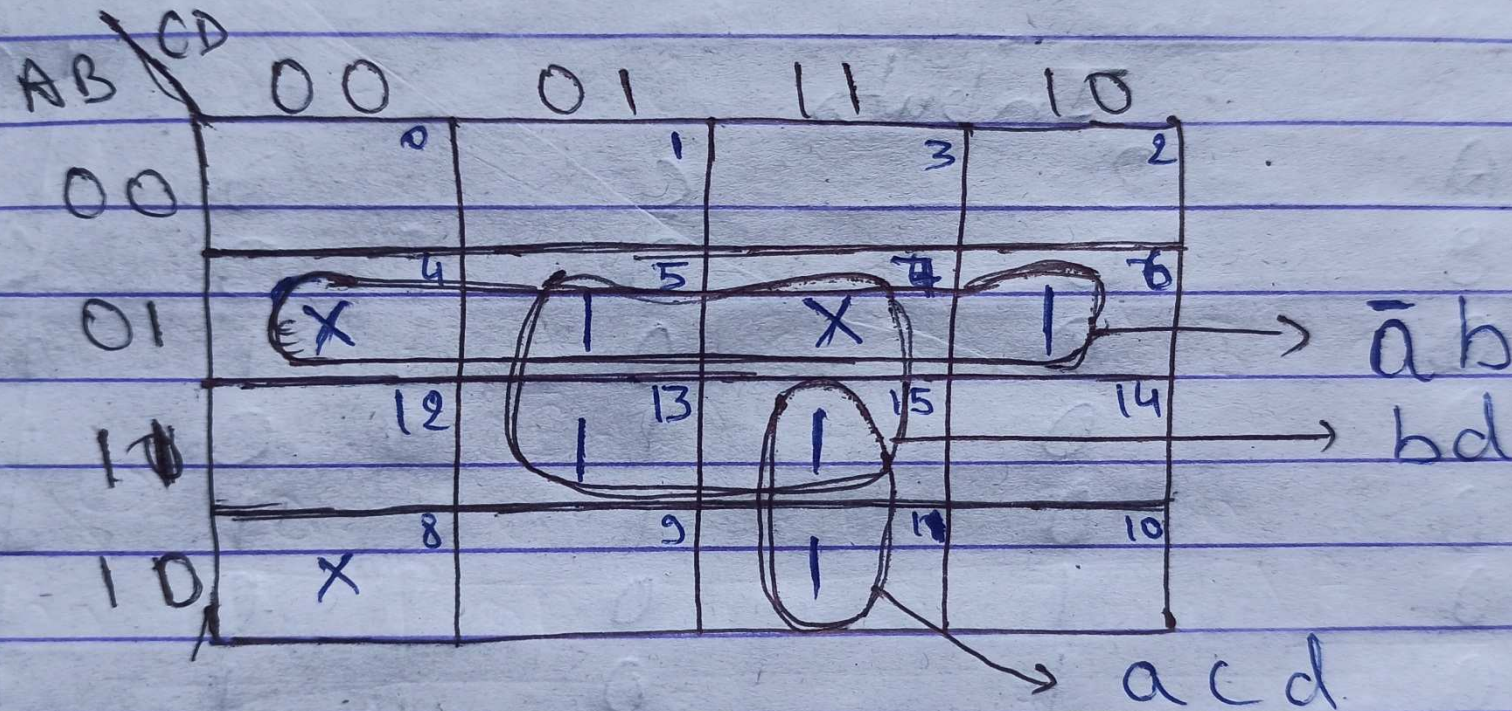Its K-map and the minimised expression are given below,



$$\text{So } f(A, B, C, D) = \bar{a}b + bd + acd$$

Combinational Logic Design

(2). In terms of maxterms and don't care conditions. For example

$$f(A, B, C, D) = \prod M(1, 2, 6, 7, 8) \cdot d(0, 5, 10, 13)$$

Its K-map and the minimized expression are given below,

AB \ CD	00	01	11	10
00	X ⁰	0 ¹		0 ²
01		X ⁴	0 ⁷	0 ⁶
11		X ¹²		
10	0 ⁸			X ¹⁰

Annotations on the K-map:
- A horizontal group of 0s in the first row (cells 0, 1, 2) is labeled $(B+D)$.
- A horizontal group of 0s in the second row (cells 7, 6) is labeled $(A+\bar{B}+\bar{C})$.
- A vertical group of 0s in the first column (cells 0, 8) is labeled $(A+B+C)$.

$$\therefore f(A, B, C, D) \Rightarrow (B+D)(A+\bar{B}+\bar{C})(A+B+C)$$

Combinational Logic Design

Refer book- Modern Digital Electronics by RP Jain.

Thank You