

**Paper 7, TDC Part-3**  
**Chapter– 4, Combinational Logic Design**  
**Lecture - 15**

**By:**

**Mayank Mausam**

**Assistant Professor (Guest Faculty)**

**Department of Electronics**

**L.S. College, BRA Bihar University,**

**Muzaffarpur, Bihar**

# Combinational Logic Design

The subtraction process is explained in detail as follows.

Case 1  $\rightarrow A_n = 0, B_n = 0$  &  $B_{n-1} = 0,$

$$B_n + B_{n-1} = 0 + 0 = 0$$

$$\text{So, } A_n (0) - \{B_n + B_{n-1}\} (0) = 0$$

$$\text{i.e. } 0 - 0 = 0$$

Case 2  $\rightarrow A_n = 0, B_n = 0$  &  $B_{n-1} = 1$

$$B_n + B_{n-1} = 0 + 1 = 1$$

$$\text{So, } A_n (0) - \{B_n + B_{n-1}\} (1)$$

$$= 0 - 1$$

will give  $D_n = 1$  with  $B_n = 1$

# Combinational Logic Design

borrowing 1 from higher bit make

$$A = (0) + (10)_2 = (10)_2 =$$

$$\text{Now, } (10)_2 - (1)_2 = (2)_{10} - (1)_{10} = (1)_{10} \\ = (1)_{10} - (1)_2$$

So, Case 2 results in  $D_n = 1$  &  $B_{w_n} = 1$ .

Case 3: Same as the result for case 3 i.e.

$$A_n = 0, B_n = 1 \text{ \& } B_{w_{n-1}} = 0; B_n + B_{w_{n-1}} = 1$$

$$\Rightarrow A_n(0) - \{B_n + B_{w_{n-1}}\}(1)$$

$\Rightarrow 0 - 1$  will result  $D_n = 1$  and  $B_{w_n} = 1$

# Combinational Logic Design

Case 4:  $A_n = 0$ ,  $B_n = 1$  &  $B_{n-1} = 1$

then  $B_n + B_{n-1} = 1 + 1 = (10)_2$

Now,  $A_n(0) - \{B_n + B_{n-1}\}(10)_2$

Here again  $A_n$  has to borrow 1 from higher bit. On borrowing '1' from higher bit  $A_n$  will become  $(10)_2$  then.

$A_n(10)_2 - \{B_n + B_{n-1}\}(10)_2$

will result  $D_n = 0$  &  $B_{n-1} = 1$

Case 5:  $A_n = 1$ ,  $B_n = 0$  &  $B_{n-1} = 0$

then  $B_n + B_{n-1} = 0 + 0 = 0$

So,  $A_n(1) - \{B_n + B_{n-1}\}(0)$

$\Rightarrow 1 - 0 = 1$

i.e.  $D_n = 1$  &  $B_{n-1} = 0$

# Combinational Logic Design

Case 6:  $A_n = 1$ ,  $B_n = 0$  &  $B_{n-1} = 0$

~~Will be same as in case 5.~~

then,  $B_n + B_{n-1} = 0 + 0 = 0$

So,  $A_n(1) - \{B_n + B_{n-1}\}(1)$

$= 0$  i.e.  $D_n = 0$  &  $B_n = 0$

Case 7:  $A_n = 1$ ,  $B_n = 1$  &  $B_{n-1} = 0$

Will be same as in case 6

i.e.  $B_n + B_{n-1} = 1 + 0 = 1$

So,  $A_n(1) - \{B_n + B_{n-1}\}(1)$

$= 0$  i.e.  $D_n = 0$  &  $B_n = 0$

# Combinational Logic Design

Case 8:  $A_n = 1$ ,  $B_n = 1$  &  $B_{n-1} = 1$   
i.e.  $B_n + B_{n-1} = 1 + 1 = (10)_2$

So,  $A_n(1) = \{B_n + B_{n-1}\} (10)_2$

Here  $A_n$  will borrow 1 from higher bit and on borrowing 1 from higher bit  $A_n$  will become  $[1 + (10)_2] = (11)_2$

Now,  $A_n(11)_2 = \{B_n + B_{n-1}\} (10)_2$

$$= (11)_2 - (10)_2$$

$$= (3)_{10} - (2)_{10}$$

$$= (1)_{10}$$

$$= (01)_2$$

So,  $D_n = 1$  &  $B_n = 1$ .

# Combinational Logic Design

For realization of Full Subtractor using gates let us plot K-Map for  $D_n$  & K-Map for  $B_n$ .

So from truth table of Full Subtractor.

$D_n$

$A_n \backslash B_n B_{n-1}$	00	01	11	10
0		1		1
1	1		1	

$$\therefore D_n = \bar{A}_n \bar{B}_n B_{n-1} + \bar{A}_n B_n \bar{B}_{n-1} + A_n B_n B_{n-1} + A_n \bar{B}_n \bar{B}_{n-1}$$

$$D_n = A_n \oplus B_n \oplus B_{n-1}$$

# Combinational Logic Design


$B_{n+1}$ $A_n$	$B_n$	$B_{n-1}$	$B_{n-2}$
0	0	0	0
0	1	0	0
1	0	0	0
1	1	0	0
1	1	1	0
1	1	1	1

$$B_{n+1} = \bar{A}_n \bar{B}_n + A_n B_n + B_n B_{n-1}$$

So full subtractor can be realized using Ex-OR gates, AND gates, NOT gates & OR gate as shown in figure FS.1

AND-NAND realization of full subtractor is shown in FS.2.

# Combinational Logic Design

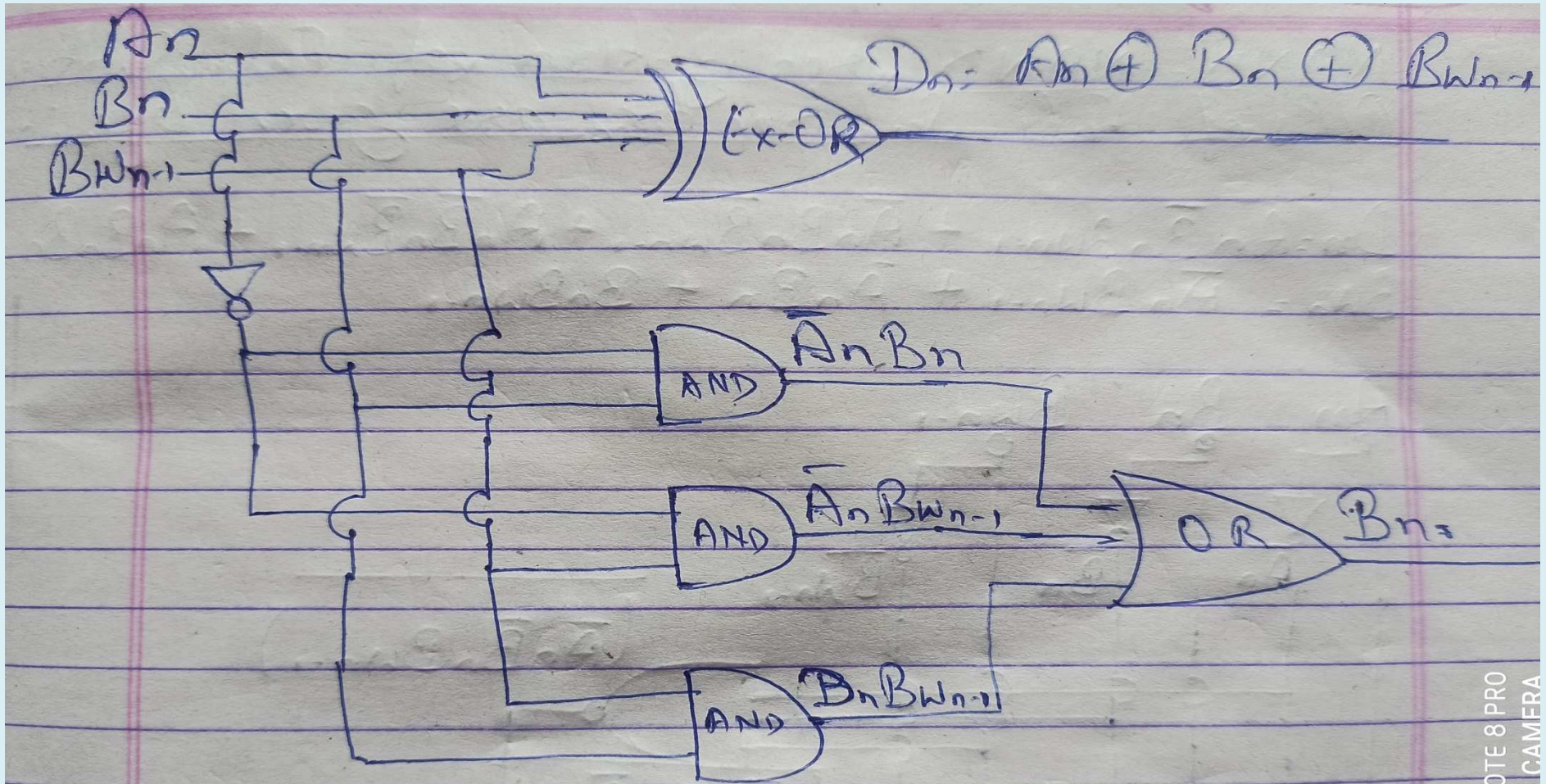


FS.1 Realization of Full Subtractor using gates.

# Combinational Logic Design


NAND-NAND realization of Full Subtractor  
O/P's of Full Subtractor are given by :-

$$D_n = A_n \bar{B}_n B_{n-1} + \bar{A}_n B_n \bar{B}_{n-1} + A_n \bar{B}_n \bar{B}_{n-1} + A_n B_n B_{n-1}$$
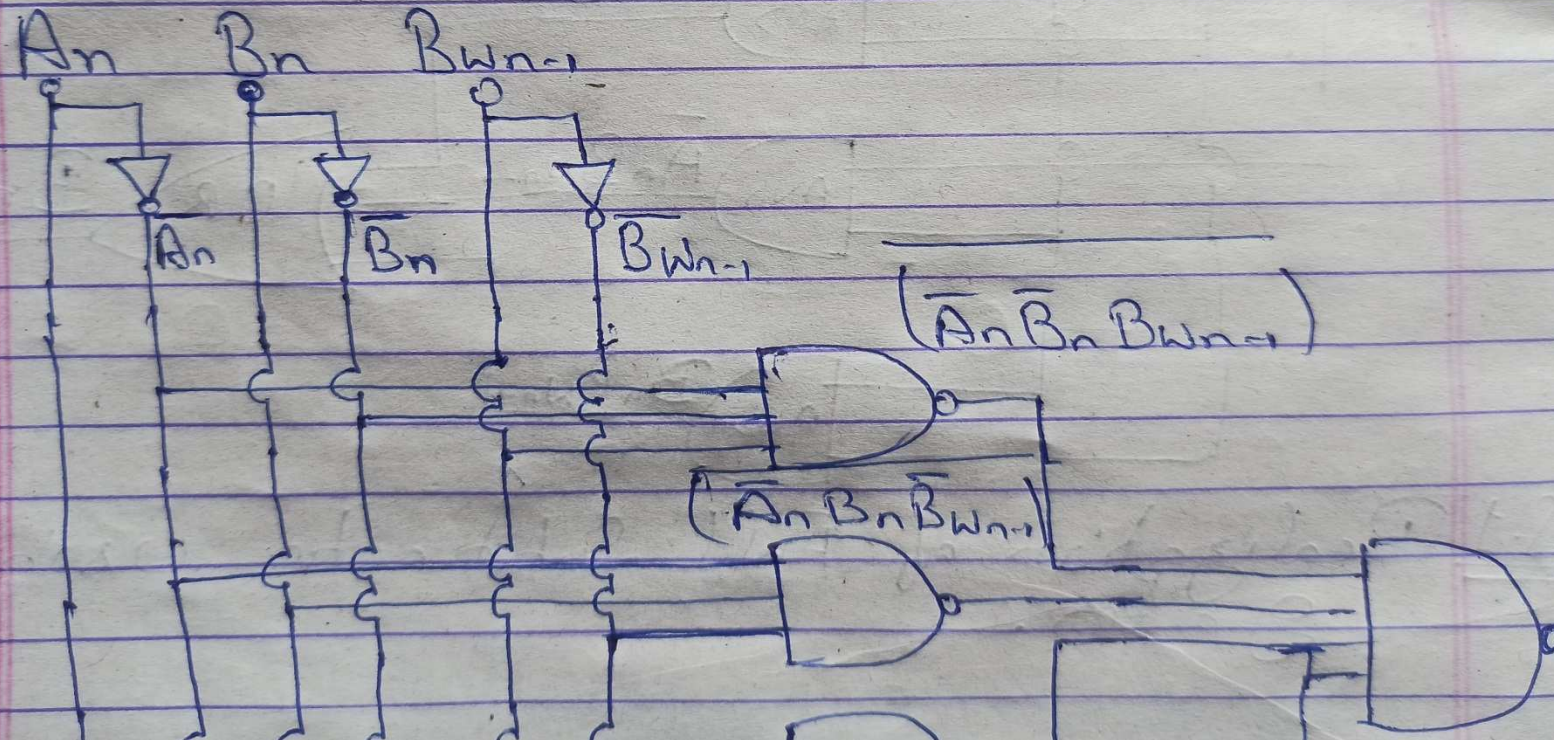
$$B_n = \bar{A}_n B_{n-1} + \bar{A}_n B_n + B_n B_{n-1}$$



# Combinational Logic Design

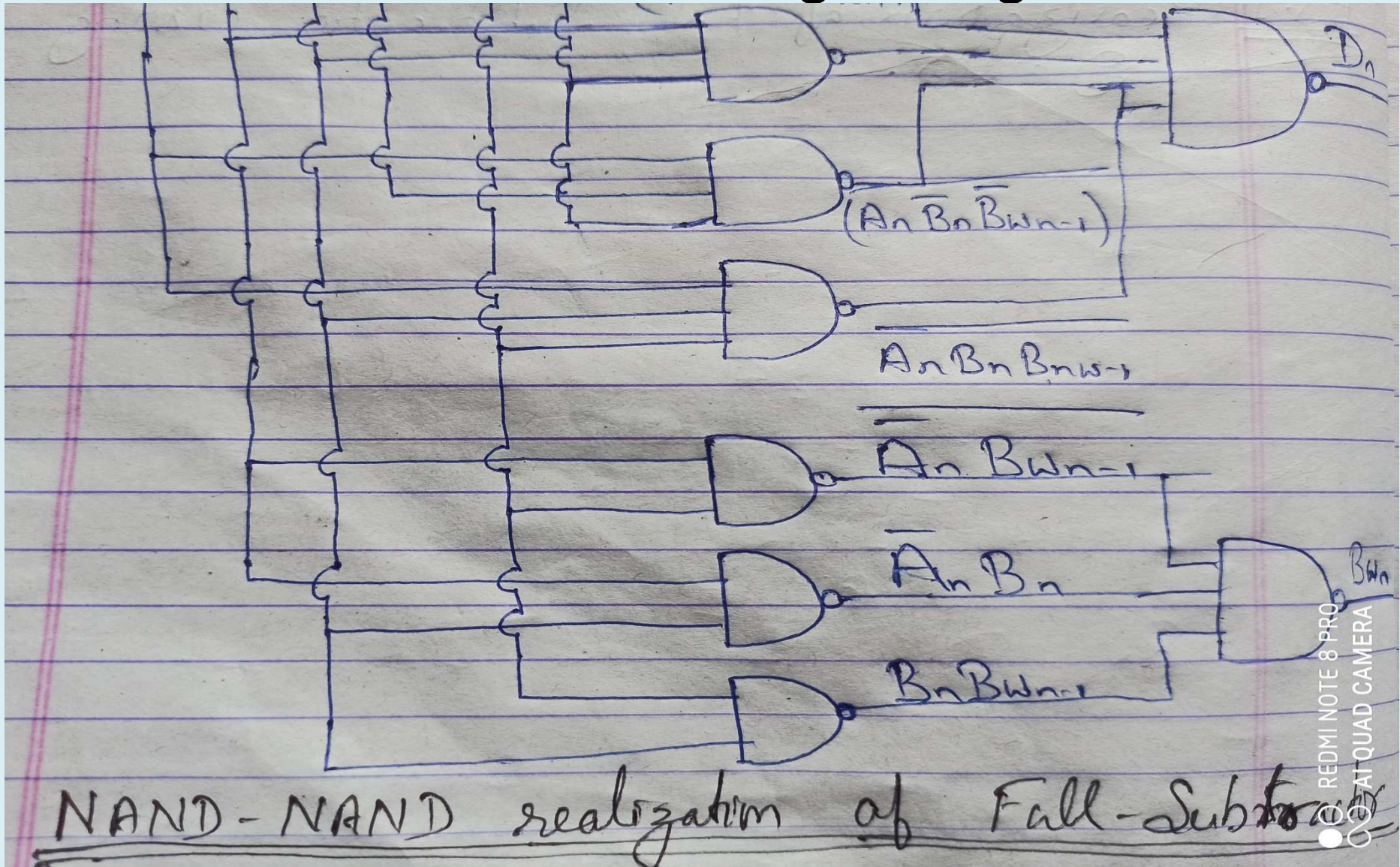

REDMI NOTE 8 PRO  
AI QUAD CAMERA

# Combinational Logic Design

NAND-NAND realization of Full Subtractor  
O/P's of Full Subtractor are given by :-

$$D_n = A_n \bar{B}_n B_{n-1} + \bar{A}_n B_n \bar{B}_{n-1} + A_n \bar{B}_n \bar{B}_{n-1} + A_n B_n B_{n-1}$$

$$B_n = \bar{A}_n B_{n-1} + \bar{A}_n B_n + B_n B_{n-1}$$



REDMI NOTE 8 PRO  
 QUAD CAMERA

realization of Full-Subtractor

# Combinational Logic Design

Refer book- Modern Digital Electronics by RP Jain.

**Thank You**