

Four Layer P-N-P-N Switching Devices

(Shockley Diode)

Lecture – 4

TDC PART – II

Paper - III (Group - A)

Chapter - 4

by:

Dr. Niraj Kumar,

Assistant Professor (Guest Faculty)

Department of Electronics

**L. S. College, BRA Bihar University,
Muzaffarpur.**

Four Layer P-N-P-N Switching Devices (Shockley Diode)

Lecture – 4

TDC PART – II

Paper - III (Group - A)


Chapter - 4

- P-N-P-N Diode or Shockley Diode
- Lecture Content :-
 - (4) The Two – Transistor Analogy

P-N-P-N Diode or Shockley Diode

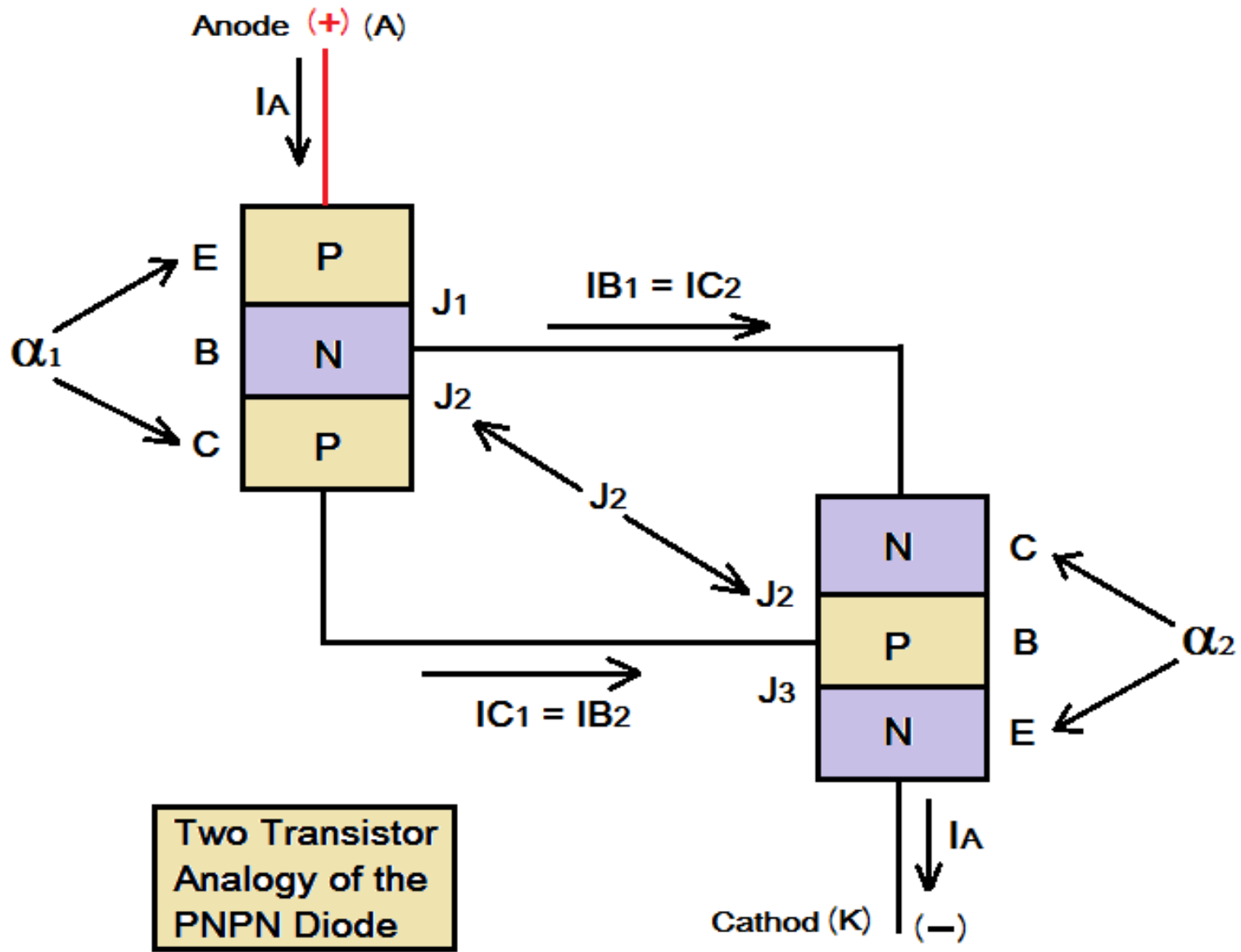- (4) The Two – Transistor Analogy
- The Four-layer configuration of **Figure (3)** suggest that the **P-N-P-N Diode** can be considered as two coupled transistor **J1** and **J2** form the **Emitter and Collector Junction** respectively, of a **PNP** transistor; similarly **J2** and **J3** form the **Collector and Emitter Junctions** of a **NPN** transistor (Note the Emitter of the **NPN** is on the right, which is the reverse of what we usually draw).

- In this analogy the **Collector region** of the **NPN transistor** is in common with the **Base** of the **PNP transistor** and the **Base** of the **NPN transistor** serves as the **Collector region** of the **PNP transistor**. The **Centre Junction J2** serves as the **Collector Junction** for the **both transistors**. This **Two-Transistor Analogy** is illustrated in **Figure (5)** below.



■ Fig (5) Shown Two Transistor Analogy of the P-N-P-N Diode or Shockley Diode.

- The **Collector Current I_{C1}** of the **P-N-P** transistor drives the Base of the **N-P-N** transistor, and the **Base Current I_{B1}** of the **P-N-P** transistor is dictated by the **Collector Current I_{C2}** of the **NPN** transistor. If we associate an **Emitter-to-Collector Current Transfer Ratio α** with each transistor, we can analysis to solve for the **Current I_c** . Using following equation,

$$\blacksquare I_C = \alpha_N I_E - I_{CO} \left(e^{qV_{CB} / KT} - 1 \right) \dots\dots\dots (1)$$

■ Where,

I_C = Collector Current,

I_E = Emitter Current,


I_{CO} = Magnitude of the Collector Saturation Current,

K = Boltzman Constant,

T = Temperature,


α = Emitter-to-Collector Current Transfer Ratio of a BJT Transistor.

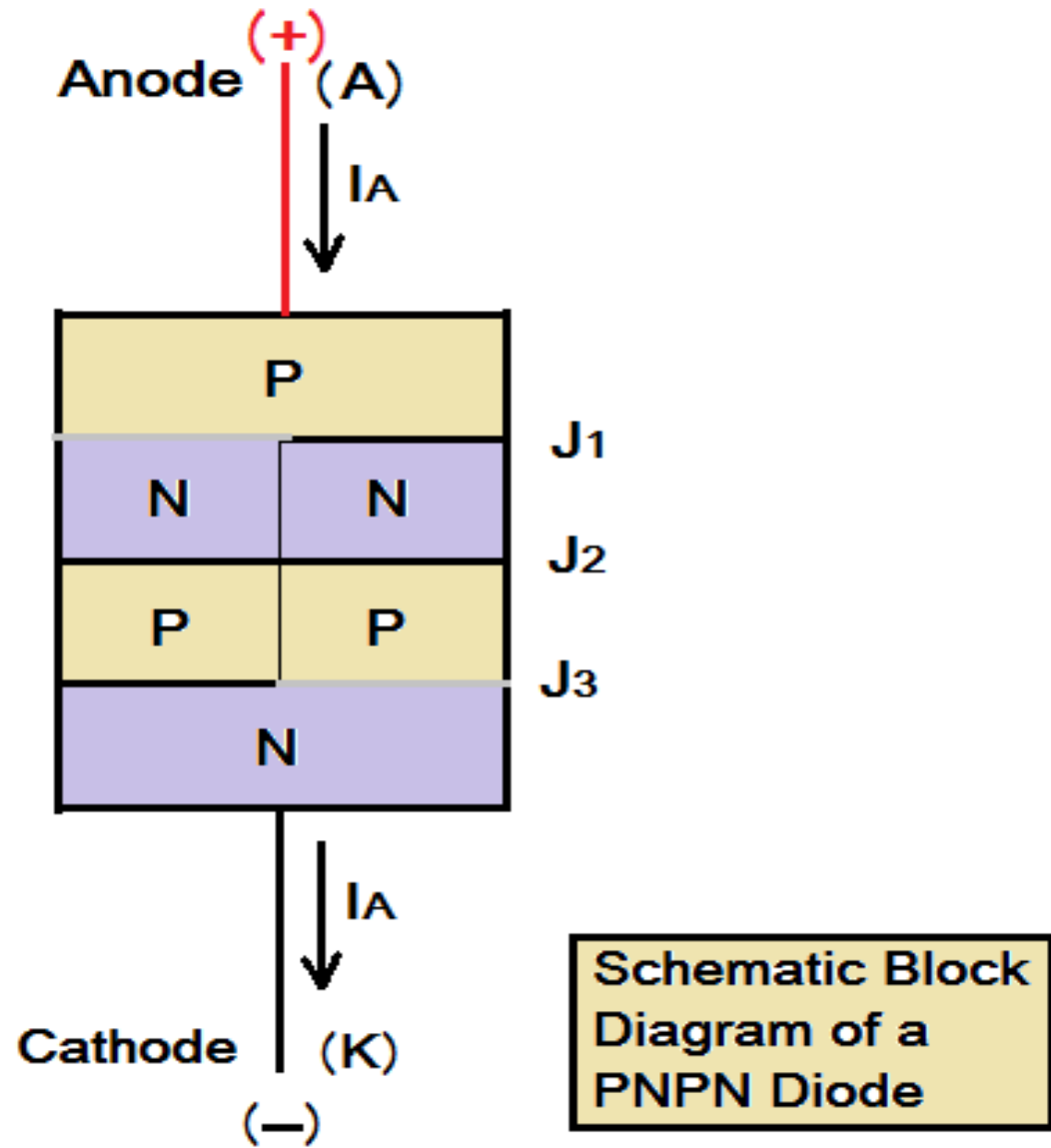- The principle of **P-N-P-N Diode** or **Shockley Diode** operation can be explained with the use of its **Two-Transistor- Model** (or **Two-Transistor-Analogy**). **Figure (6)** shows below schematic diagram of a **P-N-P-N Diode** or **Shockley Diode**.




- Fig (6) Shown Schematic Block Diagram of a P-N-P-N Diode or Shockley Diode.

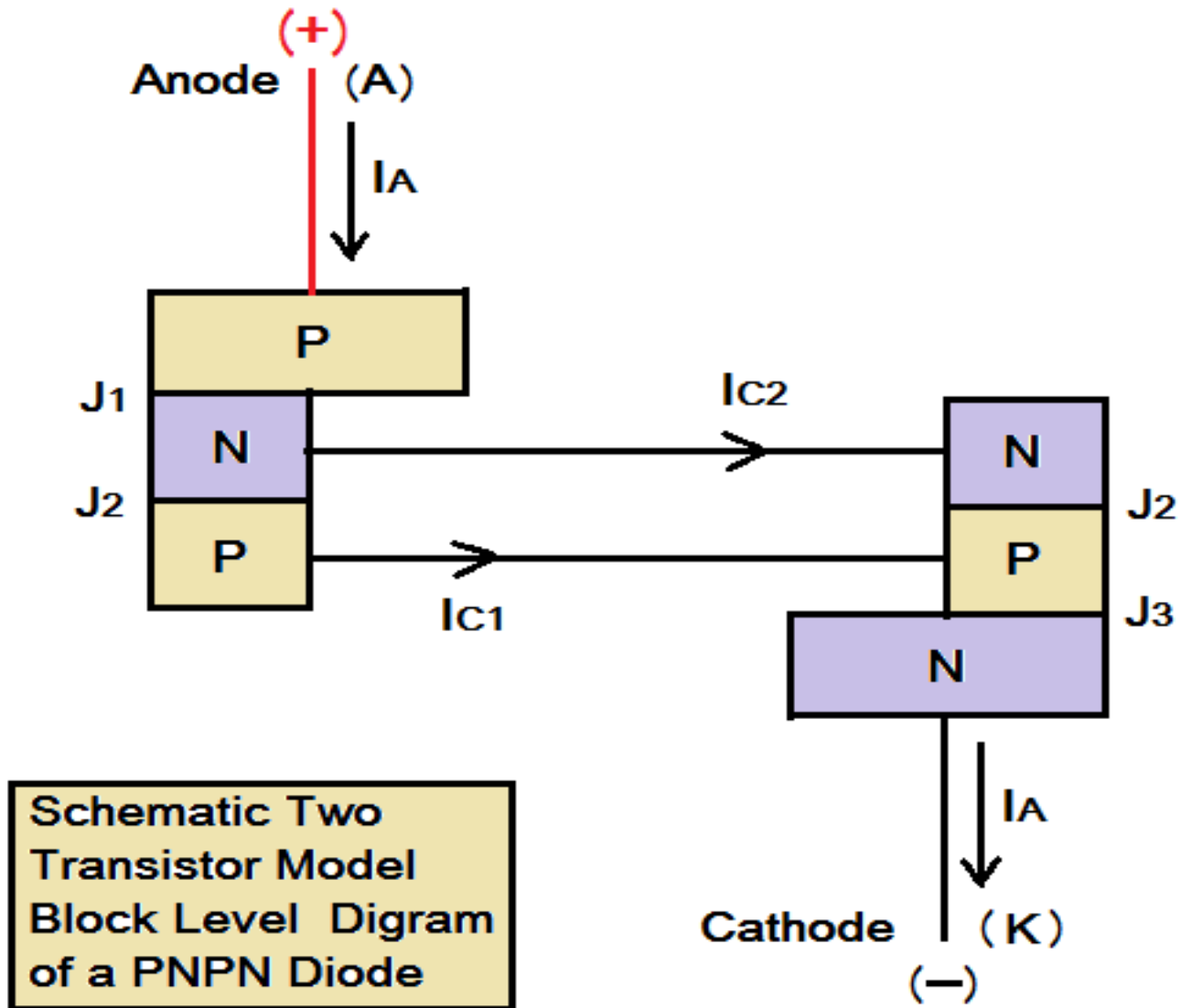- From the above **Figure (6)**, **Two-Transistor-Model** is obtained by **Bisecting the Two Middle Layers**, along the **Dotted Line**, in **Two Separate Halves** as shown in **Figure (7)** below.



- Fig (7) Shown Schematic Two Transistor Model Block Level Diagram of a P-N-P-N Diode or Shockley Diode.

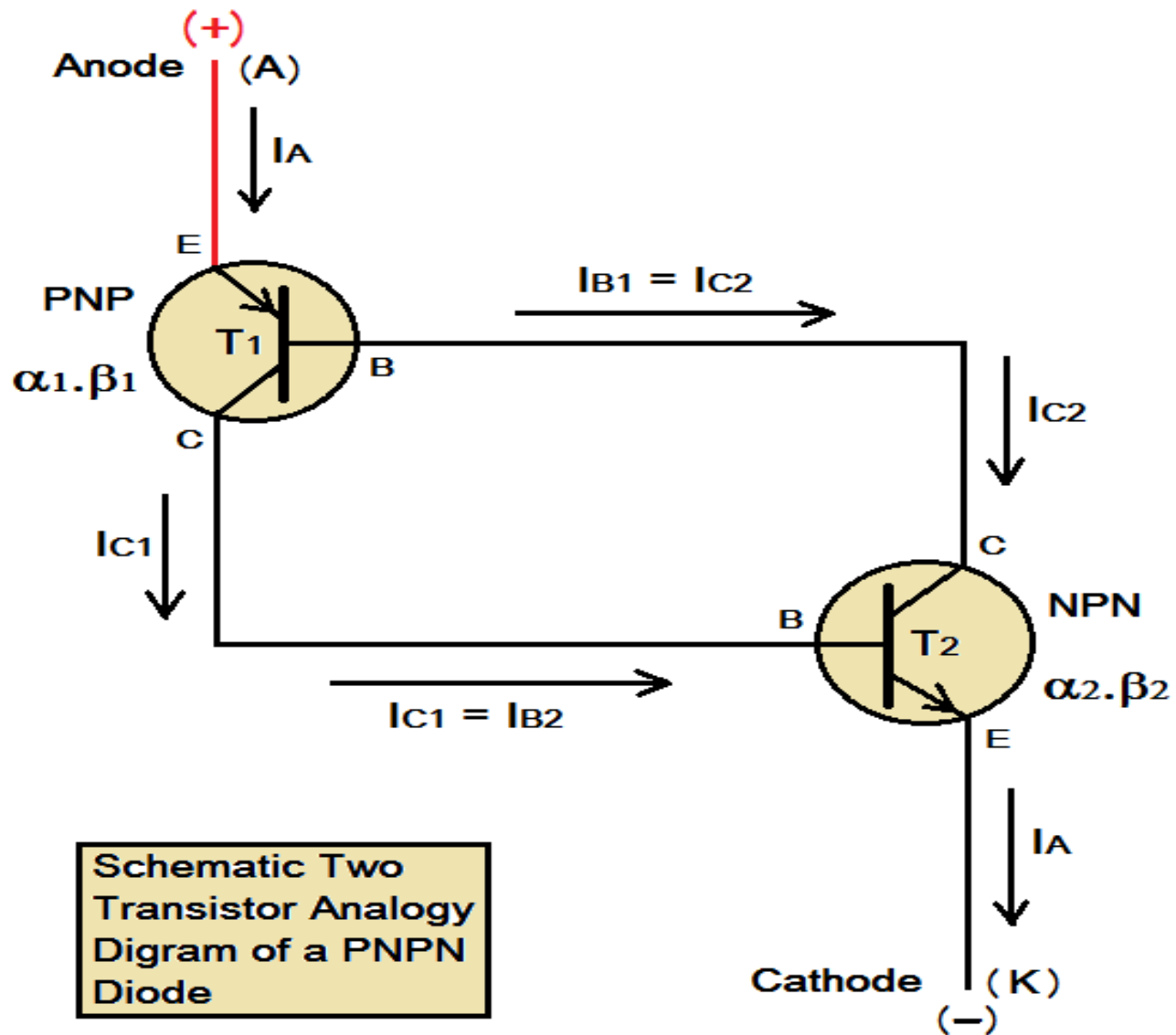- In this **Figure (7)**, Junction J1-J2 and J2-J3 can be considered to constitute **P-N-P** and **N-P-N Transistors** separately. The circuit representation of the **Two-Transistor-Model** of a **P-N-P-N Diode** or **Shockley Diode** is shown in **Figure (8)** below.



■ Fig (8) Shown Schematic Two Transistor Analogy Diagram of a P-N-P-N Diode or Shockley Diode.

■ In the **OFF-State** of a Transistor, **Collector Current I_C** is related to **Emitter Current I_E** as,

■ $I_C = \alpha I_E + I_{CBO}$

(2)

■ **Where,**

α = is the Common Base Current Gain,

I_{CBO} = is the Common Base Leakage Current at Collector Base junction of a transistor and

I_E = Emitter Current of a transistor.

- For **Transistor T1** from **Figure (8)**,
- The Collector Current I_{C1} is **given by**,
Emitter Current $I_E = \text{Anode Current } I_a$ and
Collector Current $I_C = I_{C1}$

■ Therefore, for **Transistor T1**,

■ $I_{C1} = \alpha_1 I_a + I_{CBO1} = I_{B2}$

..... (3)

■ Where,

α_1 = Common Base Current Gain of Transistor T1,

I_{CBO1} = Common Base Leakage Current of Transistor T1.

I_a = Emitter Current of Transistor T1.

■ Similarly,

■ For Transistor T2 from Figure (8),

The Collector Current I_{C2} is given by,

Emitter Current $I_E =$ Cathode Current I_K
and

Collector Current $I_C = I_{C2}$

■ Therefore for Transistor T2,

■ $I_{C2} = \alpha_2 I_K + I_{CBO2} = I_{B1}$

..... (4)

■ Where,

α_2 = Common Base Current Gain of Transistor T₂,

I_{CBO2} = Common Base Leakage Current of Transistor T₂,

I_K = Emitter Current of Transistor T₂.

■ Now, the sum of two Collector Currents given by Equation (3) and (4) is equal to the external circuit current I_a (Anode Current) entering at Anode (A) Terminal of P-N-P-N Diode.

$$\mathbf{I_a = I_{C1} + I_{C2}}$$

or,

$$\mathbf{I_a = \alpha_1 I_a + I_{CBO1} + \alpha_2 I_k + I_{CBO2} \dots\dots\dots (5)}$$

■ Here we study the **Two Terminal P-N-P-N Diode**. So here **Gate Terminal** not present. Then **Gate Current $I_g = 0$** , then **Cathode Current I_k** will be the summation of **Anode Current (I_a)** and **Gate Current (I_g)** i.e.,

■ $I_k = I_a + I_g$

■ or, $I_k = I_a + 0$

■ therefore, $I_k = I_a$

■ Substituting the above value of **Emitter Current I_k** in **Equation (5)** gives,

$$\blacksquare I_a = \alpha_1 I_a + I_{CBO1} + \alpha_2 I_a + I_{CBO2}$$

$$\blacksquare I_a = I_a (\alpha_1 + \alpha_2) + I_{CBO1} + I_{CBO2}$$

$$\blacksquare I_a - I_a (\alpha_1 + \alpha_2) = I_{CBO1} + I_{CBO2}$$

$$\blacksquare I_a (1 - (\alpha_1 + \alpha_2)) = I_{CBO1} + I_{CBO2}$$


$$\blacksquare I_a = I_{CBO1} + I_{CBO2} / 1 - (\alpha_1 + \alpha_2)$$

..... (6)

- For a Silicon Transistor, Current Gain α is very low at Low Emitter Current. With an increase in Emitter Current, α builds up rapidly as shown in **Figure (9)** below. With Gate Current $I_g = 0$ and with P-N-P-N Diode Forward Biased, $(\alpha_1 + \alpha_2)$ is very low as per **Equation (6)** and Forward Leakage Current somewhat more than $(I_{CBO1} + I_{CBO2})$ flows.

- If, by some means, the **Emitter Current** of **Two Component Transistors** can be **increased** so that $\alpha_1 + \alpha_2$ approaches **Unity**, then as per **Equation (6)**, **Anode Current I_a** would tend to become **Infinity** thereby **Turning-ON** the **P-N-P-N Diode** or **Shockley Diode** device.

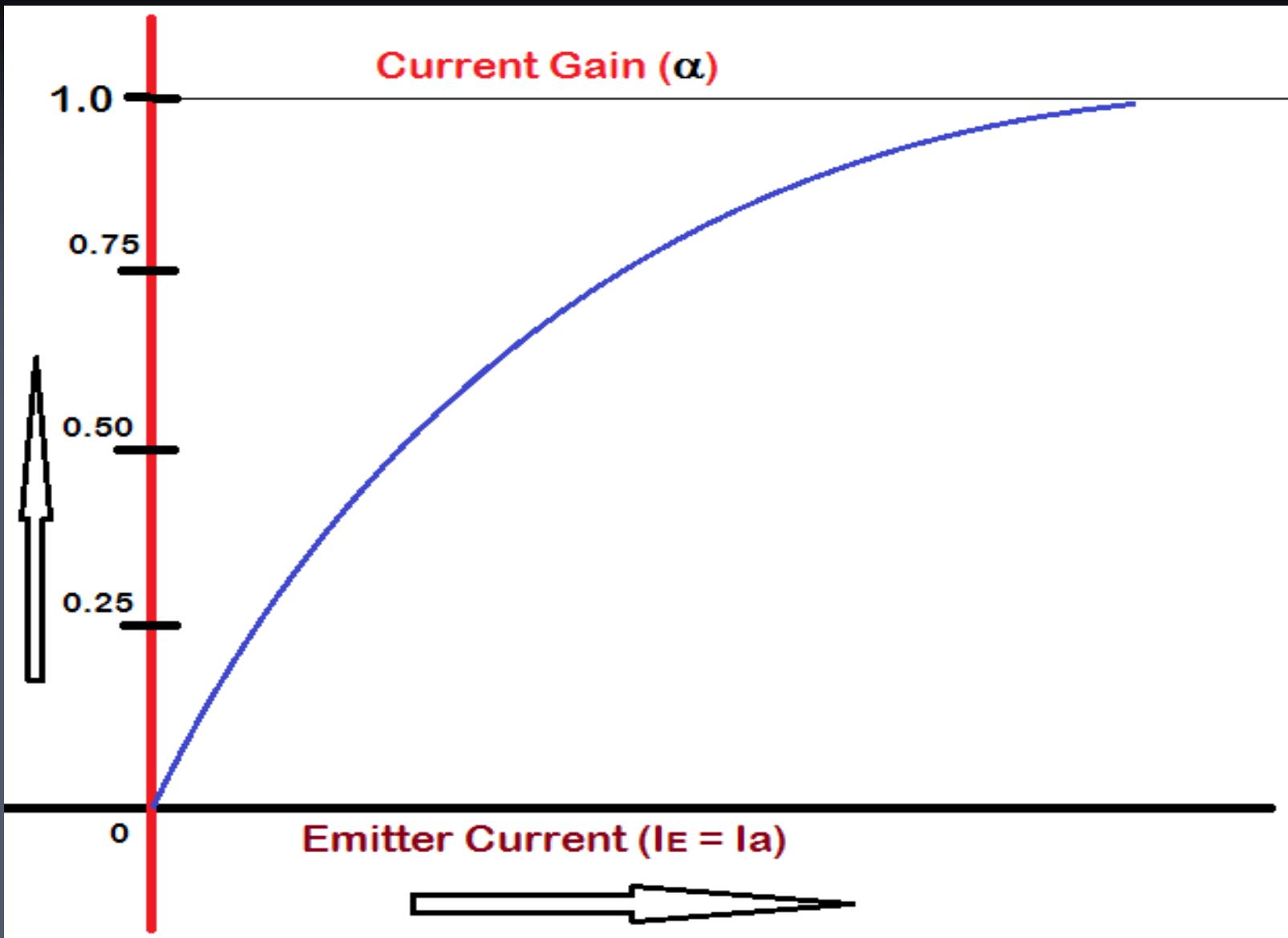- Actually, **External Load Limits** the **Anode Current I_a** to a safe value after the **P-N-P-N Diode** begins **Conduction**. The methods of **Turning-ON** a **P-N-P-N diode** or **Shockley diode**, in fact are the methods of making $\alpha_1 + \alpha_2$ to approach **Unity**.



- **Fig (9)** Shown Typical Variation of **Current Gain (α)** builds up with **Emitter Current (I_E)** or **Anode Current** of a Two Terminal P-N-P-N diode or Shockley diode.

- In other word, as **Equation (6)** indicates, the **Anode current I_a** through the **P-N-P-N Diode** devices is **small** (approximately the combined Common-Base Leakage Current of two equivalent transistors) as long as the **Sum $\alpha_1 + \alpha_2$** is **small** compared with **Unity**. As the **Sum of the Alphas approaches Unity**, the **Current $I_a = I$** increases rapidly.

- The current does not increase without limit at **Equation (6)** implies, however, because the derivation is no longer valid as $\alpha_1 + \alpha_2$ approaches Unity. Since Junction J2 becomes Forward Biased in the Forward Conducting State, both Transistors Become Saturated after Switching. The Two Transistors remain in Saturation while the device is in the Forward Conducting State, being held in Saturation by the device current.

to be continued