

Paper 7, TDC Part-3
Chapter– 1, Fundamental Concept of Digital
Electronics
Lecture - 2

By:

Mayank Mausam
Assistant Professor (Guest Faculty)
Department of Electronics
L.S. College, BRA Bihar University,
Muzaffarpur, Bihar

Fundamental Concepts of Digital Electronics

In this lecture we will see some other basic gates.

- **OR Gate :-**


The OR operation is defined as:- When one or more than one inputs are at logic 1 then the output is also at logic 1 else the output is at logic 0. The OR Gate can have N inputs ($N \geq 2$) and One output. The logical expression of OR operation is given by

$$Y = A \text{ OR } B \text{ OR } C \text{ OR } \dots \text{ OR } N$$

$$Y = A + B + C + \dots + N$$

Fundamental Concepts of Digital Electronics

- **Symbol for OR Gate :-**

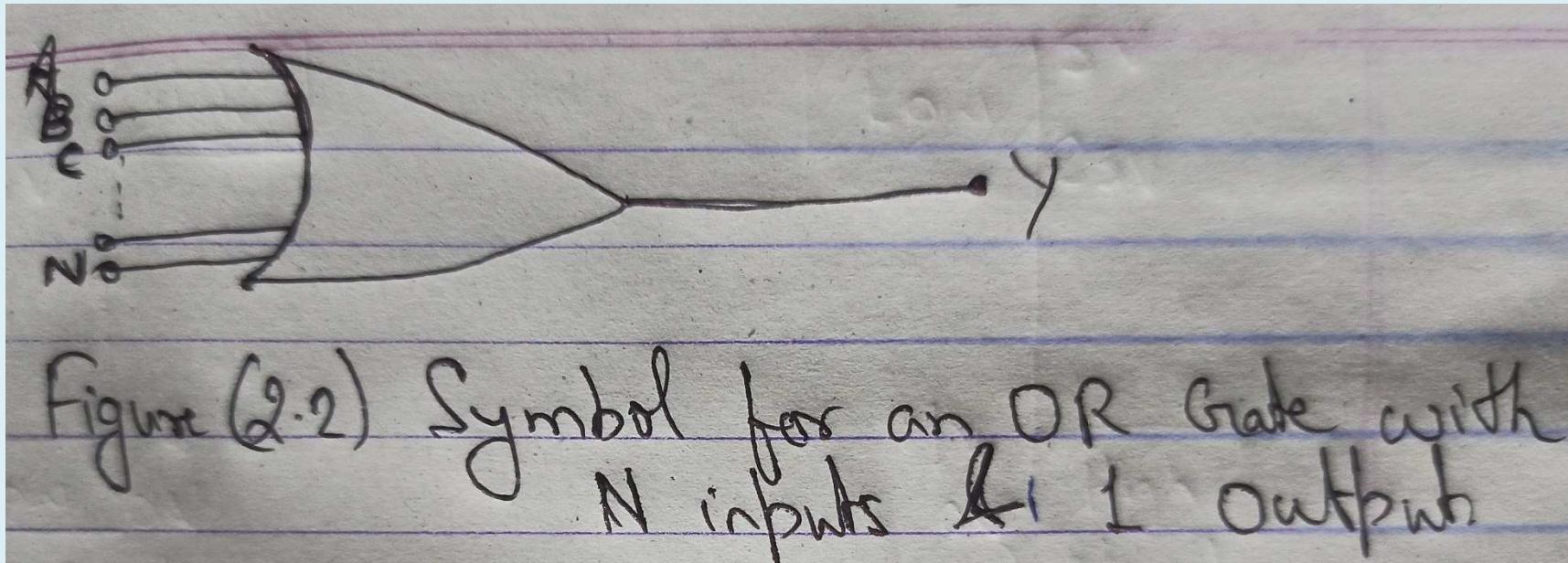

Operation of an OR Gate with any numbers of inputs can be shown through its truth table.

Fundamental Concepts of Digital Electronics

- **Truth Table for OR Gate : -**

The below truth table is of an OR Gate with 2 nos. of inputs.

Input (A)	Input (B)	Output (Y)
0	0	0
0	1	1
1	0	1
1	1	1

Truth Table for 2- Input OR Gate

Fundamental Concepts of Digital Electronics

Input (A)	Input (B)	Input (C)	Output (Y)
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

Truth table of a 3- Input OR Gate

Fundamental Concepts of Digital Electronics

Similarly the truth table for any numbers of input signals can be written. The output of an OR Gate will be “Low (0)” when all the input signals are “Low (0)” otherwise the output will be “High (1).”

The OR operation is also referred to as logical sum and so it is also symbolised algebraically by a summation sign (+).

Let us see few problems

Fundamental Concepts of Digital Electronics

Example 1.1) In a chemical process an Alarm is required to be activated if either temperature or pressure or both exceed certain limits. Is it possible to express this operation in terms of a digital operation? If yes, find the operation.

Solution -> Let the temperature and pressure be converted into electrical signals with the help of transducers. $T=1$ if Temperature exceeds the specified limit and $P=1$ if pressure exceeds the specified limit. If $T=1$ or $P=1$ or both T and P are 1 then the alarm is required to be activated, ~~is~~ This operation can be expressed as,


$$Y = T \text{ OR } P$$

$$Y = T + P$$

That is an OR operation.

Fundamental Concepts of Digital Electronics

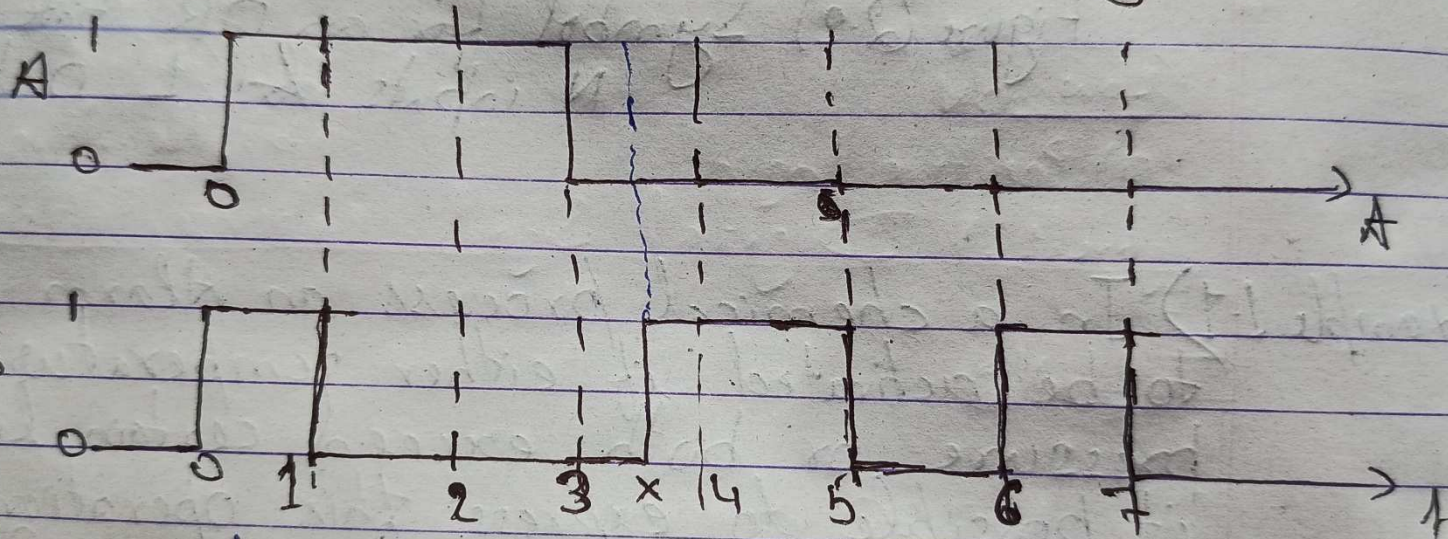Example 1.2) Determine the output waveform for of a two input OR- Gate to which applied signals A & B waveform are given below.



Solution As we know that the output of an OR Gate is ~~is~~ "low" or "0" only when all the input signals are "low" or "0" else the ~~output~~ output of the OR- Gate is "High" or "1"

Fundamental Concepts of Digital Electronics

Gate is ~~go~~ low or "0" only when all the input signals are low or "0" else the output of the OR-gate is "High" or "1"

So from above wave form we can find the output of the OR-gate

From $t=0$ to $t=1$; $A=1$, $B=1$ so, $O/p(Y) = 1$

" $t=1$ to $t=2$; $A=1$, $B=0$ so, $O/p(Y) = 1$

" $t=2$ to $t=3$; $A=1$, $B=0$ " $Y = 1$

" $t=3$ to $t=X$; $A=0$, $B=0$ so, $Y = 0$

" $t=X$ to $t=4$; $A=0$, $B=1$ so, $Y = 1$

" $t=4$ to $t=5$; $A=0$, $B=1$ so, $Y = 1$


" $t=5$ to $t=6$; $A=0$, $B=0$ so, $Y = 0$

$t=6$ to $t=7$; $A=0$, $B=1$ so, $Y = 1$

Fundamental Concepts of Digital Electronics

As for $A > 7$; $A = B = 0$; so $Y = 0$

O/P waveform, of the OR Gate is.

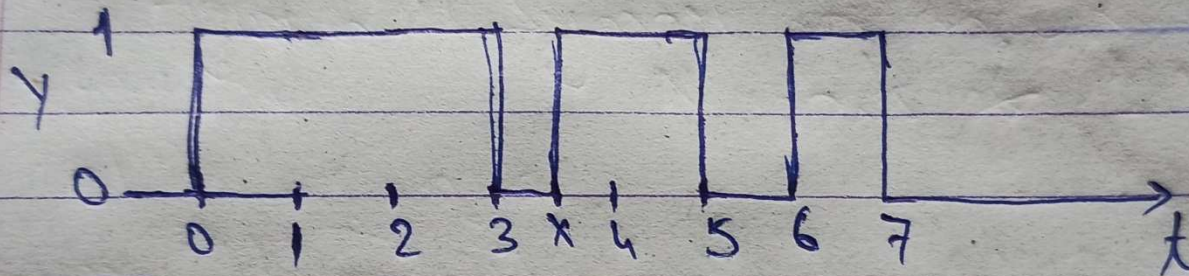

Fundamental Concepts of Digital Electronics

- **AND Gate :-**

The AND operation is defined as:- When all the inputs are at logic 1 then only the output is at logic 1 else the output is at logic 0. The AND Gate can have N inputs ($N \geq 2$) and One output. The logical expression of AND operation is given by


$$Y = A \text{ AND } B \text{ AND } C \text{ AND } \dots \text{ AND } N$$

$$Y = A \cdot B \cdot C \cdot \dots \cdot N$$

$$Y = ABC \dots N$$

Fundamental Concepts of Digital Electronics

- **Symbol for AND Gate :-**

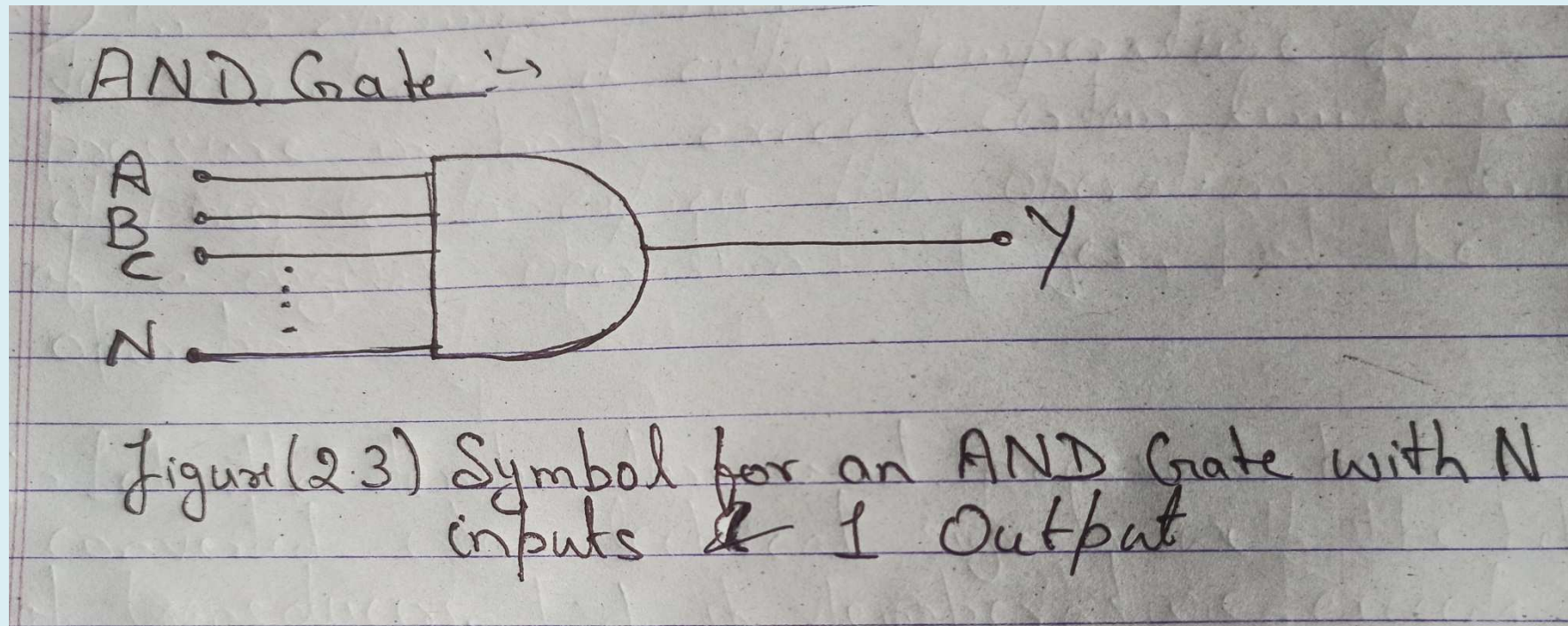

Operation of an AND Gate with N numbers of inputs can be shown through its truth table.

Fundamental Concepts of Digital Electronics

- **Truth Table for AND Gate :-**

The below truth table is of an AND Gate with 2 nos. of inputs.

Input (A)	Input (B)	Output (Y)
0	0	0
0	1	0
1	0	0
1	1	0

Truth Table for 2- Input AND Gate

Fundamental Concepts of Digital Electronics

Input (A)	Input (B)	Input (C)	Output (Y)
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

Truth table of a 3- Input AND Gate


Fundamental Concepts of Digital Electronics

Similarly the truth table for an AND Gate with any numbers of input signals can be written. The output of an AND Gate will be “High (1)” when all the input signals are “High (1)” otherwise the output will be “Low (0)”.

The AND operation is also referred to as logical multiplication and so it is also symbolised algebraically by a multiplication dot (\cdot).

Fundamental Concepts of Digital Electronics

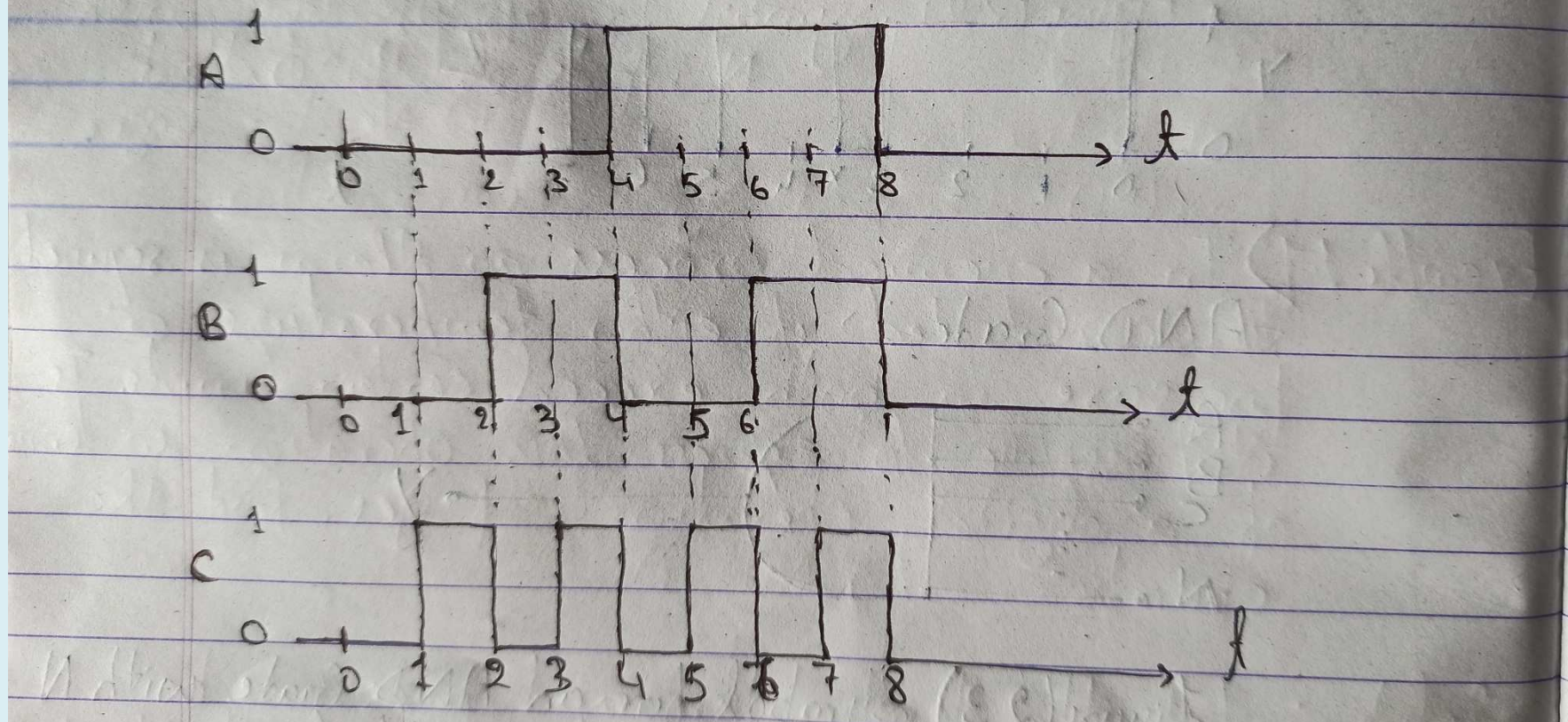Example (1.3) Determine the output waveform of a 3 input AND gate, to which applied signals A, B & C waveform are given below.



Fundamental Concepts of Digital Electronics

