

**Paper 1 Group A, TDC Part-1
Solved Question of Previous Year
Lecture-1**

By:

Mayank Mausam

Assistant Professor (Guest Faculty)

Department of Electronics

L.S. College, BRA Bihar University,

Muzaffarpur, Bihar

Paper 1 Group A- 2016

T.D.C Part 1 ->

2016

Paper -> I

Q1(a) State and prove Superposition theorem.

Ans: Statement of Superposition theorem is

The theorem states that in any ~~linear~~ linear, bilateral, active network having more than one source (current or voltage), the response across any element is the sum of the responses obtained from each source considered separately and all other sources are replaced by their internal resistance.

Paper 1 Group A- 2016

Proof:-

Let us consider a linear bilateral n/w as shown in figure 1(a).

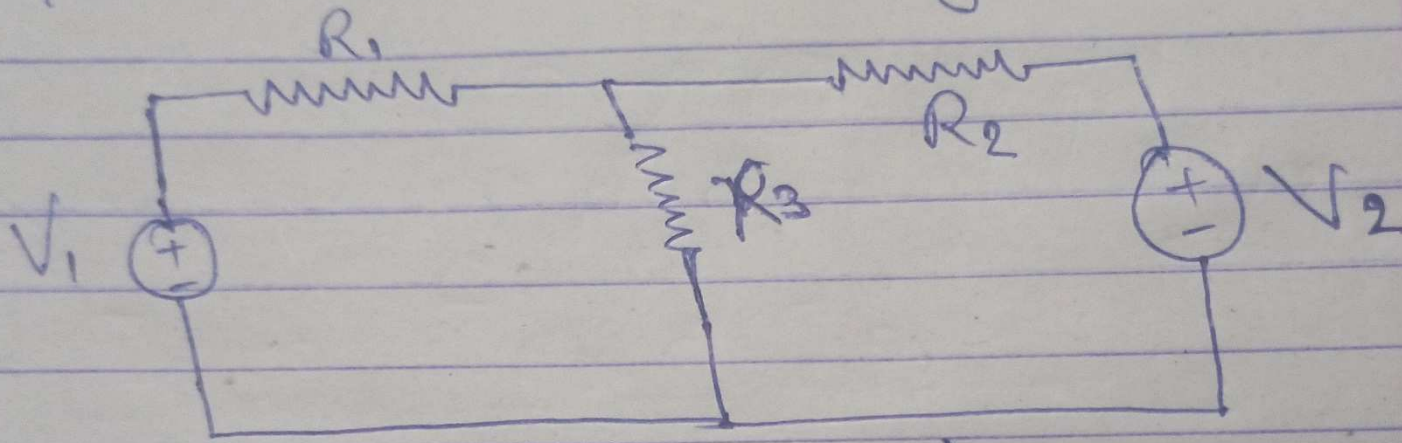


figure \rightarrow 1(a)

To find the current through Resistance R_3 of figure 1(a), we will apply

Paper 1 Group A- 2016

apply superposition theorem

So first let us consider voltage source V_1 ,
 ~~S_1~~ and ~~shortplace (remove)~~ V_2 by short circuit

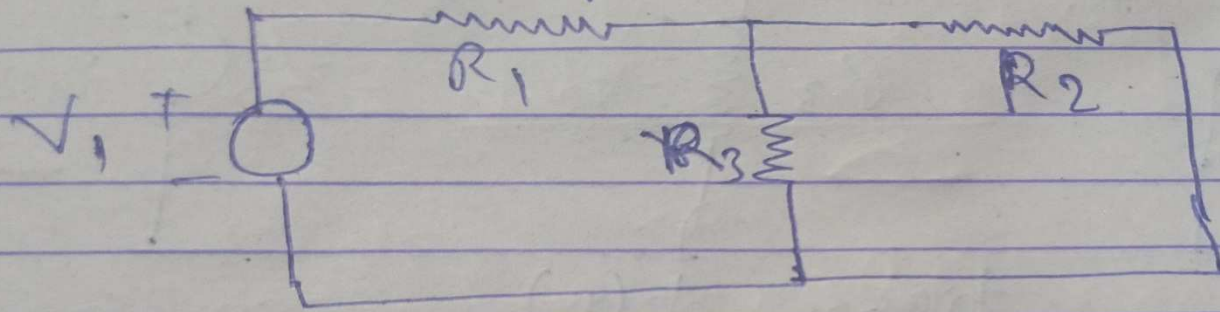


figure 1(b)

In above n/w R_2 & R_3 ~~will now be~~ ^{is} in parallel combination and in series with R_1 , so net resistance of n/w is,

$$R_1 + \frac{R_2 R_3}{(R_2 + R_3)} = \frac{R_1 R_2 + R_1 R_3 + R_2 R_3}{R_2 + R_3}$$

Paper 1 Group A- 2016

So total current in the ckt is

$$I_T = \frac{V_1 \times (R_2 + R_3)}{R_1 R_2 + R_1 R_3 + R_2 R_3}$$

Current through R_3 due to V_1 only is

$$I_{R_3} = \frac{I_T \times R_2}{(R_2 + R_3)}$$

$$= \frac{V_1 \times R_2}{R_1 R_2 + R_1 R_3 + R_2 R_3}$$

[Putting value of I_T]
①

Now, we take another voltage source V_2

Paper 1 Group A- 2016

and replace V_1 by short circuit as shown
in figure 1(c) below,

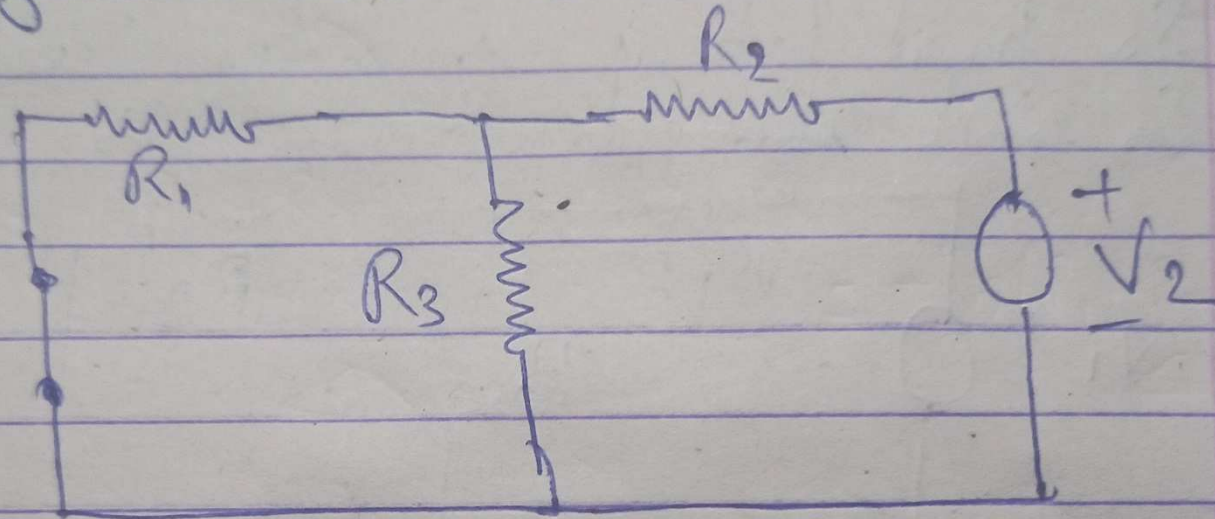


figure 1(c)

In above n/w, now, R_1 & R_3 are in // and then in series with R_2

Paper 1 Group A- 2016

As we obtained the current I'_{R_3} , similarly we find current in R_3 due to source V_2 given as,

$$I''_{R_3} = \frac{V_2 \times R_1}{R_1 R_3 + R_1 R_2 + R_2 R_3} \quad \text{--- (ii)}$$

Adding eqn. (i) & (ii) we get total current through R_3 due to V_1 & V_2

$$\text{in, } I_{R_3} = I'_{R_3} + I''_{R_3}$$

$$I_{R_3} = \frac{V_1 R_2 + V_2 R_1}{R_1 R_3 + R_1 R_2 + R_2 R_3} \quad \text{--- (iii)}$$

Paper 1 Group A- 2016

Now, let us find the current in R_3 of n/w of figure 1(a) without applying superposition theorem.

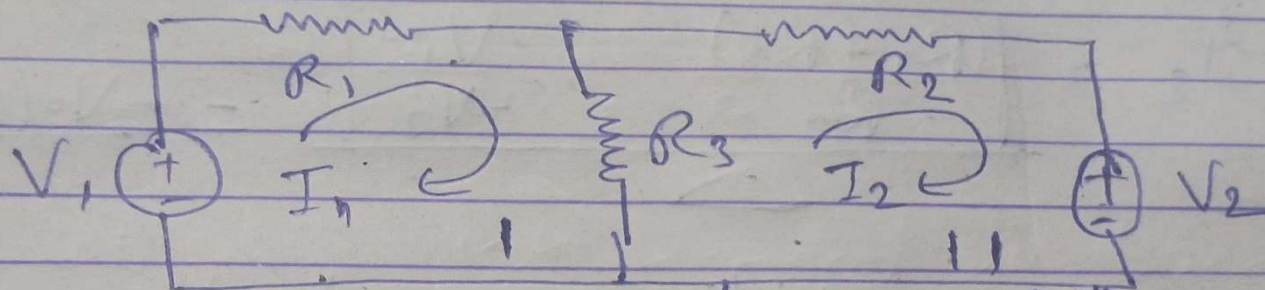


Figure \rightarrow 1(a)

Let current I_1 flows in loop 1 and I_2 flow in loop 2. Now applying KVL in loop 1.

$$R_1 I_1 + R_3 (I_1 - I_2) = V_1 \quad \text{---}$$

$$(R_1 + R_3) I_1 - R_3 I_2 = V_1 \quad \text{--- (iv)}$$

Paper 1 Group A- 2016

Applying KVL in loop II, we get,

$$I_2 R_2 + I_2 R_3 - I_1 R_3 = -V_2$$

$$-I_1 R_3 + I_2 (R_2 + R_3) = -V_2 \quad \text{--- (v)}$$

Using Cramer's Rule, from eqn. (iv) & (v)

$$\Delta = \begin{vmatrix} (R_1 + R_3) & -R_3 \\ -R_3 & (R_2 + R_3) \end{vmatrix} = R_1 R_2 + R_2 R_3 + R_3 R_1 \quad \cancel{R_3^2 - R_3^2}$$

$$\Delta = R_1 R_2 + R_2 R_3 + R_3 R_1$$

Paper 1 Group A- 2016

$$\text{So, } I_1 = \frac{\begin{vmatrix} V_1 & -R_3 \\ -V_2 & (R_2 + R_3) \end{vmatrix}}{\Delta} = \frac{V_1(R_2 + R_3) - V_2 R_3}{\Delta} \quad \text{--- (vi)}$$

Similarly

$$I_2 = \frac{\begin{vmatrix} (R_1 + R_3) & V_1 \\ -R_3 & -V_2 \end{vmatrix}}{\Delta} = \frac{-V_2(R_1 + R_3) + V_1 R_3}{\Delta} \quad \text{--- (vii)}$$

from figure 1(d) current through R_3 is

$$I_1 - I_2 = \frac{V_1 R_2 + V_1 R_3 - V_2 R_3 + V_2 R_1 + V_2 R_3 - V_1 R_3}{\Delta}$$


from eq. (vi) & (vii)

Paper 1 Group A- 2016

$$I_{R_3} = I_1 - I_2 = \frac{V_1 R_2 + V_2 R_1}{R_1 R_2 + R_2 R_3 + R_3 R_1} \quad \text{--- (ix)}$$

So, from eqn. (iii) & (ix) we observe that current through resistor R_3 is same, ~~and~~ this proves superposition theorem.

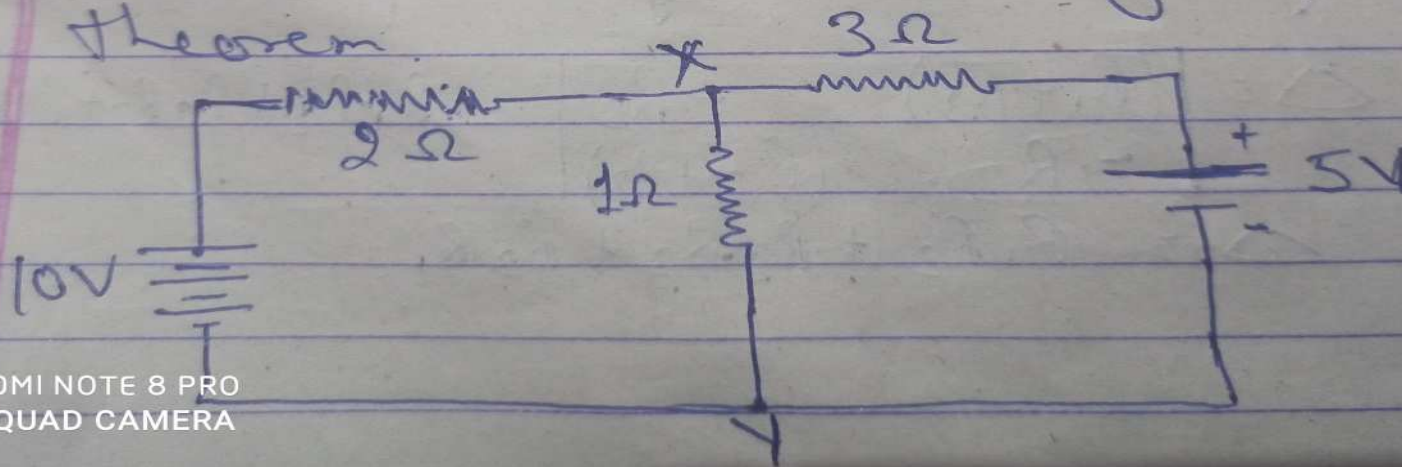Q 1(b) Find the current in branch XY in the circuit shown below using superposition theorem.



Paper 1 Group A- 2016

Soln: Applying superposition theorem let us first consider source of 10V and remove 5V by the short circuit, then

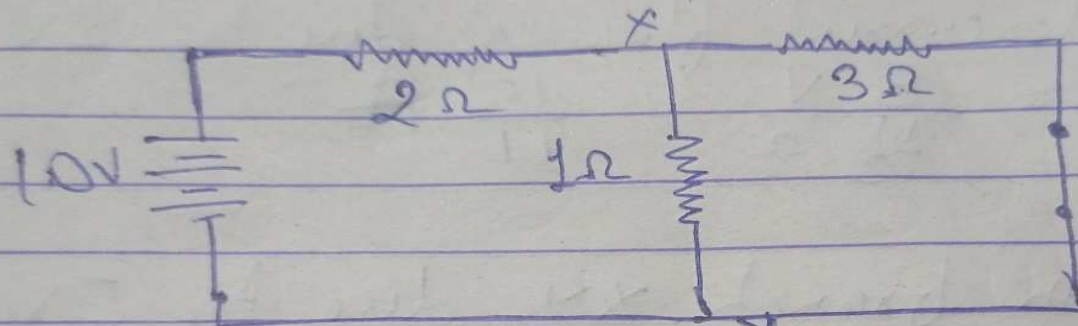


fig 2 (a)

In above ckt, 1Ω & 3Ω are in || and then in series with 2Ω,

$$\therefore R_{eq} = 2 + \frac{3 \times 1}{3+1} = 2 + \frac{3}{4} = \frac{11}{4} \Omega$$

So current due to 10V is,

$$I_{10V} = \frac{10 \times 4}{11} \text{ A} = \frac{40}{11} \text{ A}$$

Paper 1 Group A- 2016

$$I_{10V} = \frac{10 \times 4}{11} = \frac{40}{11}$$

Current in branch XY due to 10V is,

$$I_{(x-y)_{10V}} = \frac{10 \times \frac{40}{11} \times 3}{11 \times (3+1)} = \frac{30}{11} \text{ A} \quad \text{--- (i)}$$

Now, considering 5V ^{source}, and removing 10V by short ckt.

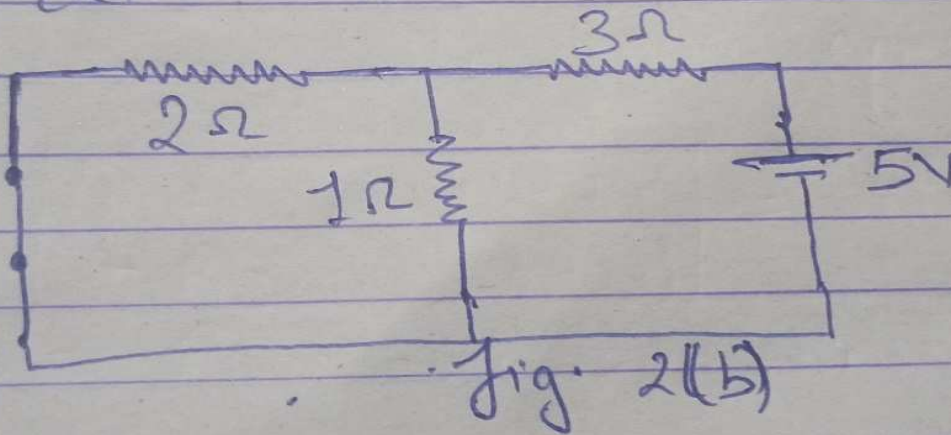


Fig. 2(b)

In above ckt, 2Ω & 1Ω are in parallel and then in series with 3Ω, So,

Paper 1 Group A- 2016

$$R_{eq} = \frac{2 \times 1}{2+1} + 3 = 2 + \frac{2}{3} = \frac{11}{3} \Omega$$

So, total current flowing due to 5V source is

$$I_{5V} = \frac{5V}{\frac{11}{3} \Omega} = \frac{15}{11} A$$

Current in branch XY due to 5V source

$$I_{(x-y)5V} = \frac{5 \times \frac{15}{11} \times 2}{11 \times (2+1)} = \frac{10}{11} A \quad \text{--- (ii)}$$

So current in branch XY is given by adding eqn. (i) & (ii)

$$I_{(x-y)} = I_{(x-y)10V} + I_{(x-y)5V}$$

$$= \left(\frac{30}{11} + \frac{10}{11} \right) A = \frac{40}{11} A$$

Paper 1 Group A- 2016

Students are advised to see other theorems also. The lecture for those theorem available on college website.

Solution for other question will also be provided

For any query contact- 9771474020

Thank You