

# **Silicon Controlled Rectifier (SCR)**

## **Lecture – 21**

**TDC PART – I**

**Paper - II (Group - B)**

**Chapter - 5**

**by:**

**Dr. Niraj Kumar,**

**Assistant Professor (Guest Faculty)**

**Department of Electronics**

**L.S. College, BRA Bihar University,  
Muzaffarpur.**

# Silicon Controlled Rectifier (SCR)

## Lecture – 21

TDC PART – I

Paper - II (Group - B)

Chapter - 5

- **SCR Turning-OFF Methods (PART – 9)**
- **Lecture Content :-**
  - **(2) Forced Commutation**
  - **(V) Class-F Commutation - AC Line Commutated**


# Class-F Commutation : AC Line Commutated

- Natural or Line commutation is a Class-F SCR-Commutation-type in which, a SCR (thyristor) is Turned OFF due to Natural Current Zero and Voltage Reversal after every Half Cycle. This commutation method is only applicable for AC circuit and mostly used in Phase-Controlled Converters, Line-Commutated Inverters, AC Voltage Controllers and Step-down Cyclo-Converters.
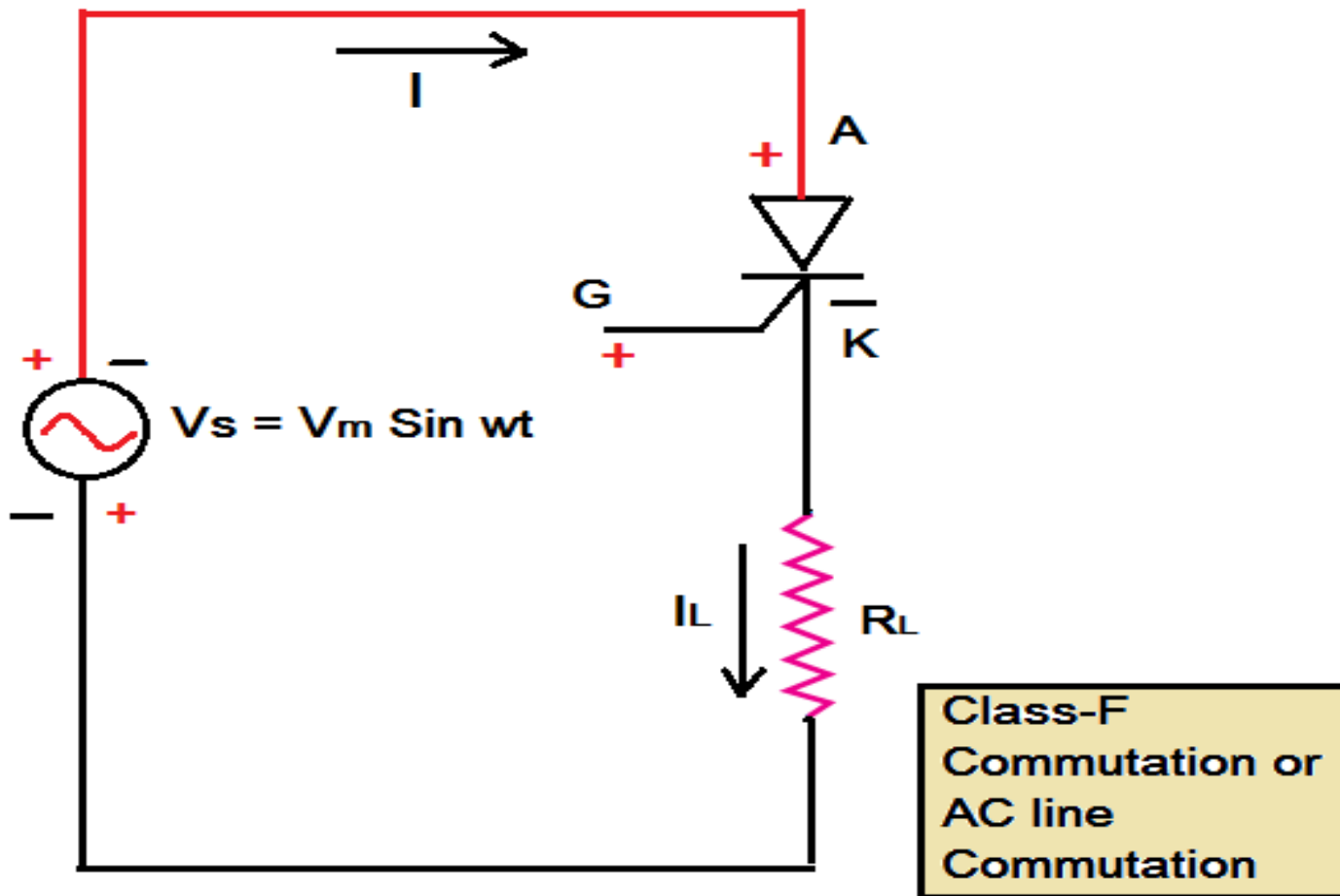
## Why it called Natural Commutation?


- The Commutation of SCR (thyristor) does not involve any External Circuit. SCR (thyristor) is Commutated just because of the Natural Reversal of AC Load Current ( $I_{RL}$ ) and Source Voltage ( $V_s$ ), this is the reason it is Called Natural Commutation.

- **Figure (101)** shows below the **Class-F Commutation** and it is **Voltage and Current Waveforms** are depicted in **Figure (102)** below. This type of commutation is also known as **Natural Commutation** or **AC Line Commutation**. This type of commutation only occurs when the **Input Voltage is AC**.



- Fig (101) Shown Class-F Commutation or AC Line Commutation Circuit Diagram.

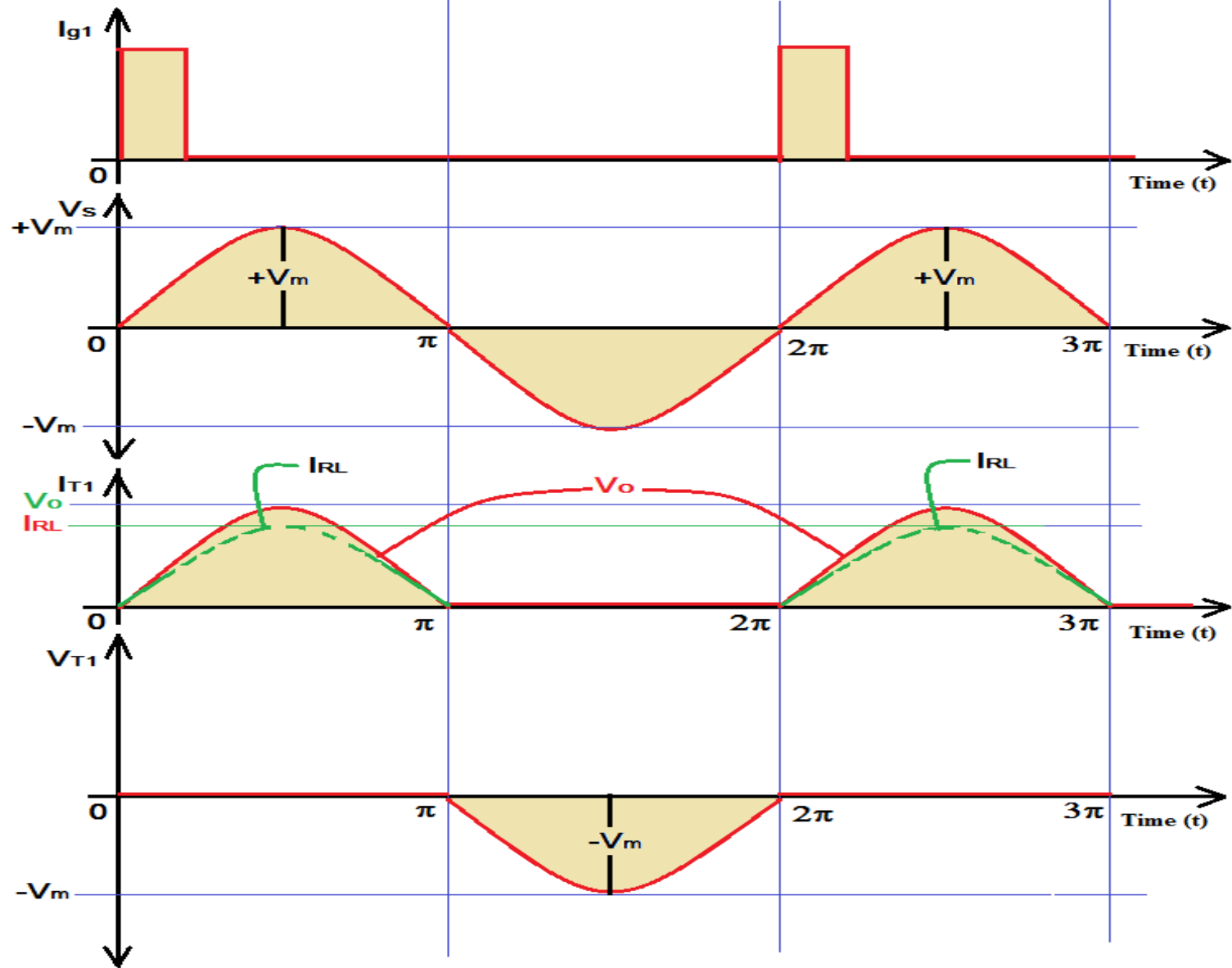- When the **SCR (thyristor)** based converter circuit is energised by an **AC Source Voltage** and the **Gate (G) signal** is applied to **SCR (thyristor) T1** during **Positive Half-Cycle** of supply voltage, **SCR (thyristor) T1** becomes **Turn ON** and **Current  $I_L$**  flows through **SCR (thyristor) T1** and **Load Resistance  $R_L$** .



■ Fig (102) Shown Class-F Commutation or AC Line Commutation Voltage and Current Waveforms.

- At the end of each **Positive Half-Cycle** of supply voltage, Current passes through its **Natural Zero** and then AC source applies a **Reverse Voltage** across **SCR (thyristor) T1** automatically. Consequently, **SCR (thyristor) T1** will be **Turned OFF**.

- There are **no Commutating Components** used in this method therefore it is not called as **Forced Commutation method**. This commutation technique is called **Natural Commutation** as no **External Circuit** is required to **Turn OFF** the **SCR (thyristor) T1**. Usually, this commutation method is commonly used in **Controlled Rectifiers, Line Commutated Inverters, AC Voltage Controllers and Cyclo-Converters**.

# Principle of Class-F or Natural or Line Commutation


- When an **SCR (thyristor)** circuit is energized from an **AC source**, **Current** has to pass through its **Natural Zero** at the end of every **Half Cycle**. The **AC source** then applies a **Negative Voltage** across **Cathode** and **Anode** terminals of **SCR (thyristor)**.

- As we know that, the required conditions for **SCR (thyristor) to Turn OFF** are,
  - Current through **SCR (thyristor)** must reach below its **Holding Current**, and
  - **SCR (thyristor)** must be **Reversed Biased** for a time more than its **Turn OFF time ( $t_q$ )** so that it may recover the stored charges.

- Since, **Current reaches zero** at the end of every **Half Cycle** and **Voltage** across the **SCR (thyristor)** is **Negative**, hence **SCR (thyristor)** will **Turn OFF** provided the **Half time period** must be greater than **SCR (thyristor) Turn OFF time  $t_q$** .
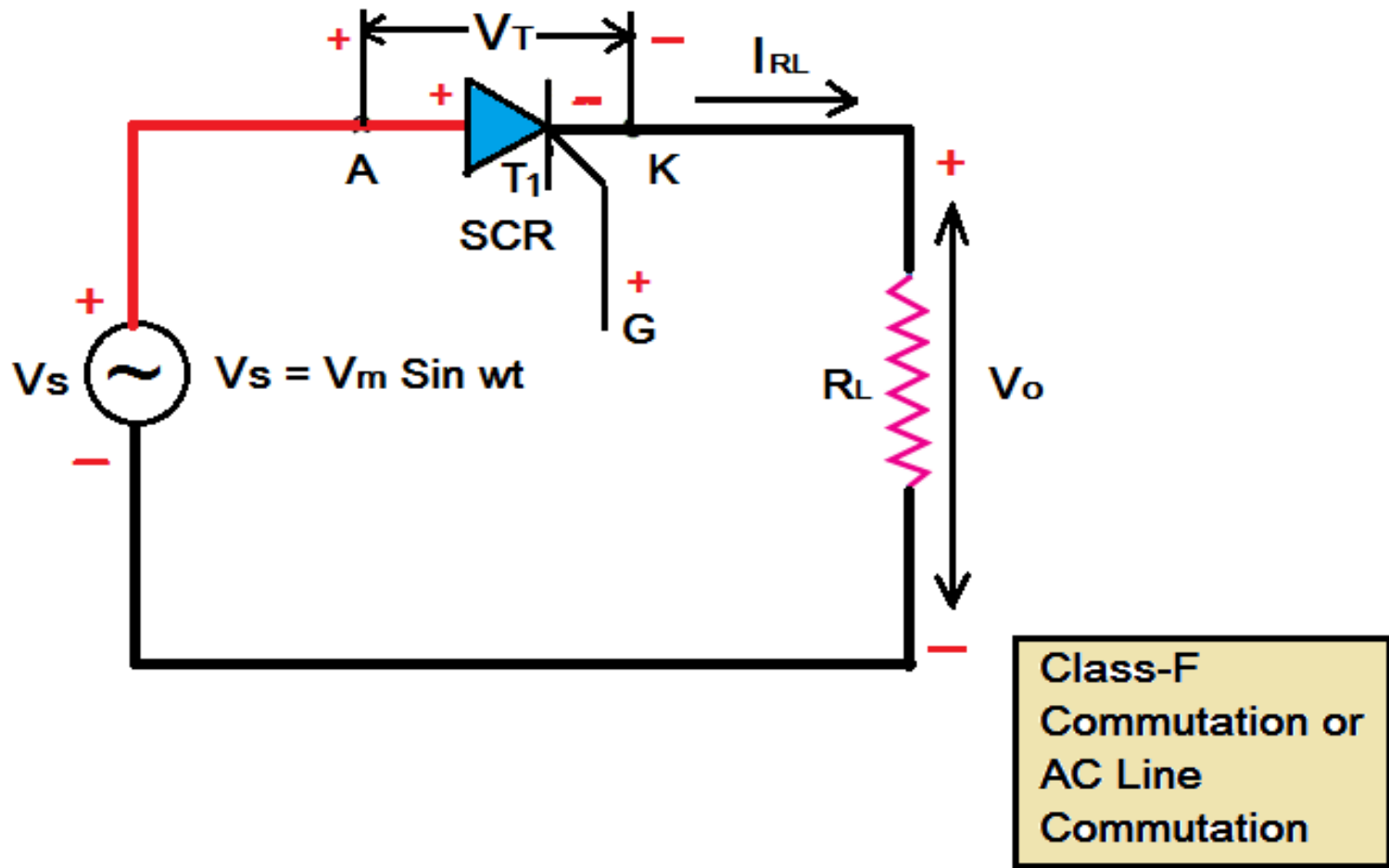
# Circuit Diagram of Natural or Line Commutation


- Let us consider a simple circuit as shown in **Figure (103)** below. The circuit is energized by an AC Source Voltage ( $V_s$ ).



■ Fig (103) Shown Class-F Commutation or AC Line Commutation Circuit Diagram.

- Let us also assume that, **SCR (thyristor) T1** is **Fired or Gated at Firing Angle equal to Zero** i.e.  $\omega t = 2n\pi$  where n is 0, 1, 2, 3....., . Since **Load is Resistive**, with **Zero degree Firing Angle**, the **SCR (thyristor)** behaves like a **Diode**. During **Positive Half Cycle**, the **SCR (thyristor)** will **Conduct** as it is **Forward Biased**.

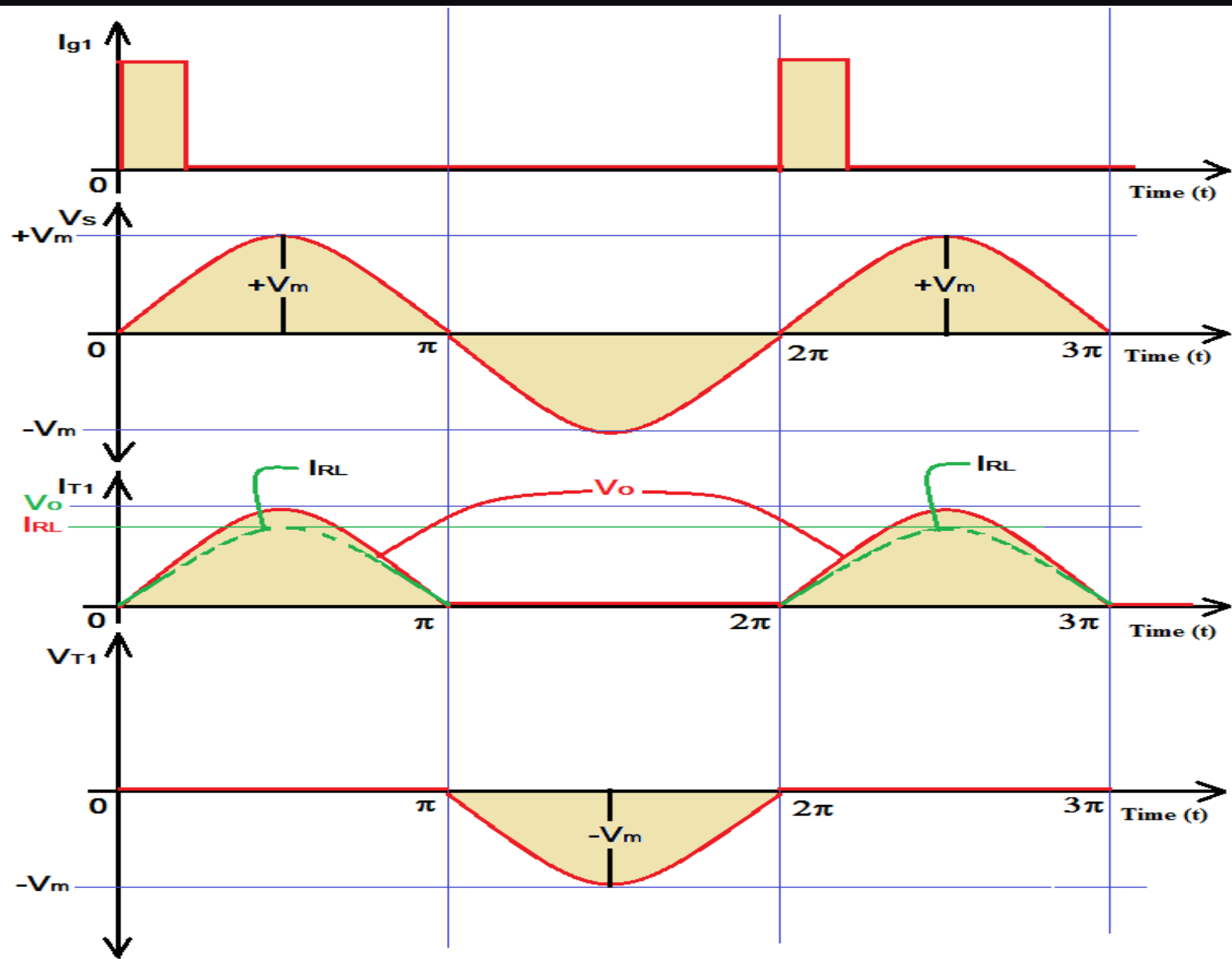- The Output Voltage  $V_o = (V_s/R)$  will have same Wave Shape as that of Source Voltage ( $V_s$ ). Load Current ( $I_{RL}$ ) will be in Phase with the Load Voltage ( $V_o$ ), hence Load Current ( $I_{RL}$ ) will have Wave Shape similar to Load Voltage ( $V_o$ ) & Source Voltage ( $V_s$ ).



■ Fig (104) Shown Class-F Commutation or AC Line Commutation Voltage and Current Waveforms.

- At  $\omega t = \pi$ , Source Voltage  $V_s = 0$ , Load Voltage  $V_o = 0$  and Load Current  $I_{RL} = 0$ . Therefore, the Current through the SCR (thyristor) becomes Zero at this instant and it is Reversed biased from  $\omega t = \pi$  to  $2\pi$ . Refer the Voltage Profile Curve  $V_T$  across SCR (thyristor) in the **Figure (104)**. This means, SCR (thyristor) is Reversed Biased for a time of  $t = (\pi/\omega)$ .

- If this time  $t$  is more than SCR (thyristor) Turn OFF time  $t_q$ , the SCR (thyristor) will Turn OFF or Commutated. Time  $t$  for which SCR (thyristor) is Reversed Biased is called Circuit Turn OFF time  $t_c$ .
- Hence Circuit Turn OFF time for Natural or Line or Class-F Commutation is  $t_c = (\pi/\omega)$ .

to be continued .....