

Paper 1, TDC Part-1
Chapter– 1, Introduction to Passive Elements
Inductor Lecture 6

By:

Mayank Mausam

Assistant Professor (Guest Faculty)


Department of Electronics

L.S. College, BRA Bihar University,

Muzaffarpur, Bihar

Introduction to Passive Elements- Inductor

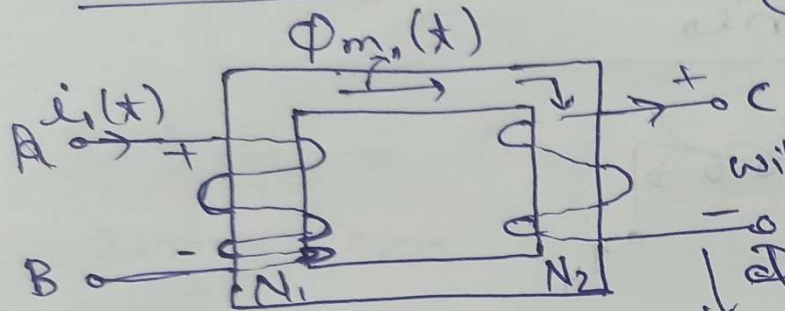When coils carry time varying current :->



Φ_m & i_1 in phase



As per Faraday's law, there will voltage at terminal C & D

$$N_2 \frac{d(\Phi_m, t)}{dt} = \frac{d(N_2 \Phi_m(t))}{dt}$$

no current

$$= \frac{d(M i_1)}{dt} = M \frac{di_1}{dt}$$
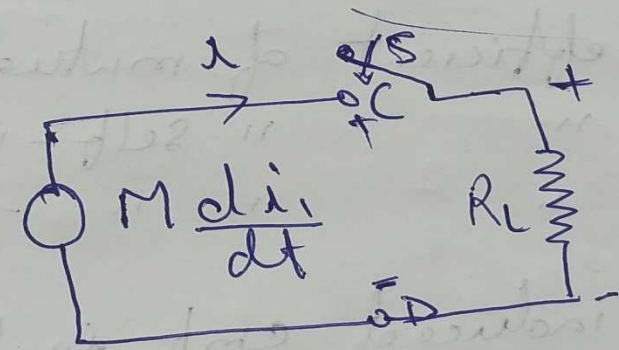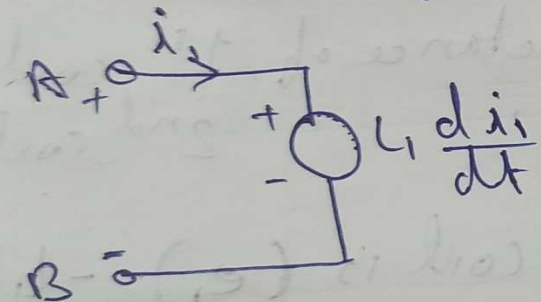
$$e_1 = \frac{d(L_1 i_1)}{dt} = L_1 \frac{di_1(t)}{dt}$$



For increasing current,

$$\frac{di_1}{dt} > 0$$



Introduction to Passive Elements- Inductor

For increasing current,

$$\frac{di_1}{dt} > 0$$

and $V_{AB} = L \frac{di_1}{dt}$

Dot convention :->

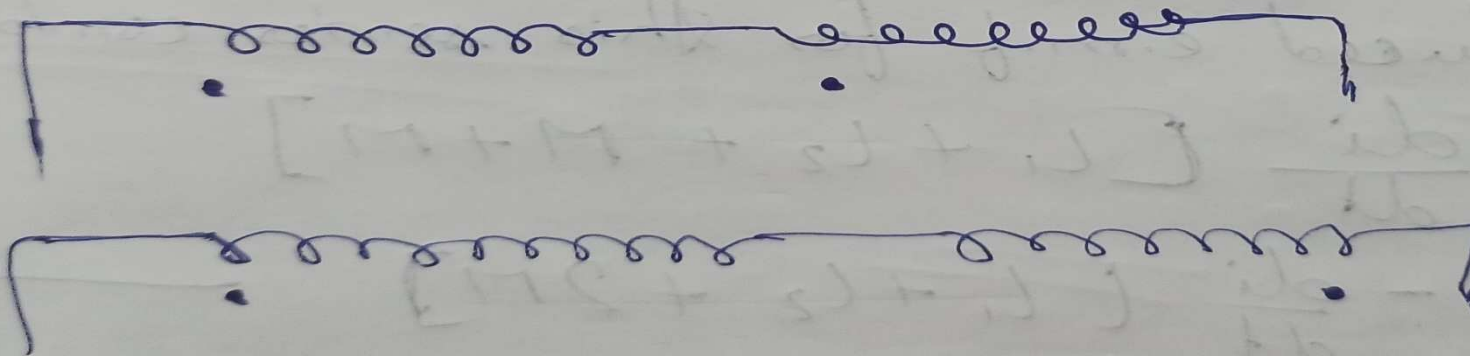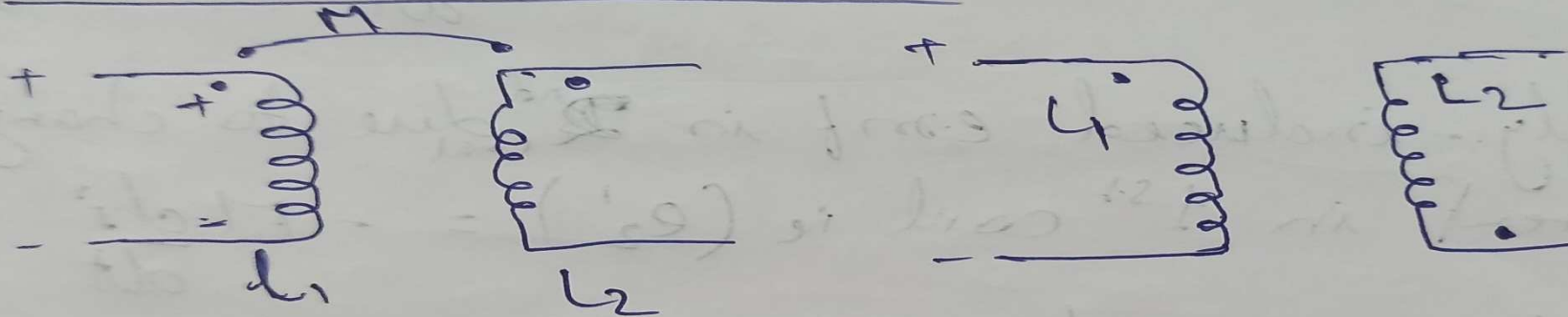

Introduction to Passive Elements- Inductor

Inductance in Series

(i) Let the two coils be so joined in series that their fluxes are additive i.e. in the same direction.

Let M = coefficient of mutual inductance

L_1 = " " " " self-inductance of 1st coil.

L_2 = " " " " " 2nd coil.

then self induced emf in 1st coil is $(e_1) = -L_1 \frac{di}{dt}$

1st coil " " " " " 2nd " " " $(e_2) = -L_2 \frac{di}{dt}$

Now,

Introduction to Passive Elements- Inductor

Now,

Mutually-induced e.m.f in ^{1st coil} due to change of current in ^{2nd coil} is $(e_1') = -M \frac{di}{dt}$

Similarly

Mutually-induced e.m.f in ^{2nd coil} due to change of current in ^{1st coil} is $(e_2') = -M \frac{di}{dt}$


All voltage are of same sign.

Total induced e.m.f for this series combination

$$is = - \frac{di}{dt} [L_1 + L_2 + M + M]$$

$$= - \frac{di}{dt} [L_1 + L_2 + 2M] \quad \text{--- (i)}$$

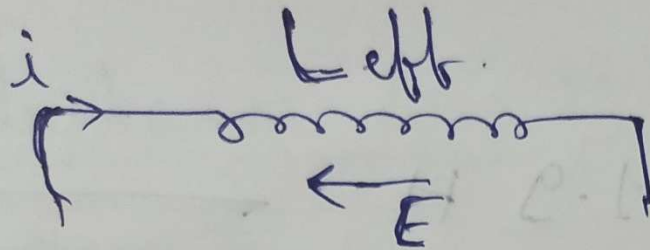Introduction to Passive Elements- Inductor



If L_{eff} is the equivalent inductance of this series combination then we have

$$E = -L_{\text{eff}} \frac{di}{dt} \quad \text{--- (ii)}$$

from (i) & (ii) we have


$$-L_{\text{eff}} \frac{di}{dt} = -[L_1 + L_2 + 2M] \frac{di}{dt}$$

$$\therefore L_{\text{eff}} = [L_1 + L_2 + 2M]$$

Introduction to Passive Elements- Inductor

Case 2

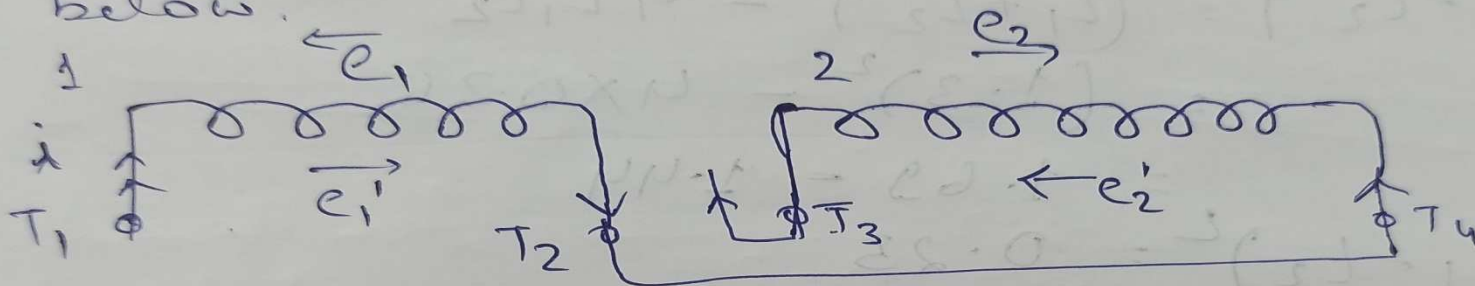When the coils are so joined that their fluxes are in opposite directions, as shown below.



So, like earlier

$$e_1 = -L_1 \frac{di}{dt}$$

$$e_2 = -L_2 \frac{di}{dt}$$

$$e_1' = M \frac{di}{dt}$$

$$e_2' = -M \frac{di}{dt}$$

$$\text{Total induced emf} = -\frac{di}{dt} [L_1 + L_2 - 2M]$$

$$\text{So, } \underline{L_{\text{eff}} = L_1 + L_2 - 2M}$$

when m.m.f.s are subtractive

Introduction to Passive Elements- Inductor

Example 7.27. Two coils with a coefficient of coupling of 0.5 between them, are connected in series so as to magnetise (a) in the same direction (b) in the opposite direction. The corresponding values of total inductances are for (a) 1.9 H and for (b) 0.7 H. Find the self-inductances of the two coils and the mutual inductance between them.

$$L = L_1 + L_2 + 2M \quad \text{or} \quad 1.9 = L_1 + L_2 + 2M \quad (a)$$

Introduction to Passive Elements- Inductor

Sol. (a) $L_s = L_1 + L_2 + 2M = 1.9 \text{ H}$ ————— (i)

$L_o = L_1 + L_2 - 2M = 0.7 \text{ H}$ ————— (ii)

Subtracting eqn. (ii) from (i) we get

$$4M = 1.2 \text{ H} \Rightarrow M = 0.3 \text{ H}$$

$\therefore L_1 + L_2 = 1.3 \text{ H}$ ————— (iii)

$M = k \sqrt{L_1 L_2}$ k = coefficient of coupling.

$$0.3 = 0.5 \sqrt{L_1 L_2}$$

$$L_1 L_2 = \left(\frac{0.3}{0.5} \right)^2 = \frac{9}{25} = 0.36$$

Introduction to Passive Elements- Inductor

$$\begin{aligned}(L_1 - L_2)^2 &= (L_1 + L_2)^2 - 4L_1L_2 \\ &= (1.3)^2 - 4 \times 0.36 \\ &= 1.69 - 1.44\end{aligned}$$

$$(L_1 - L_2)^2 = 0.25$$

$$L_1 - L_2 = 0.5 \text{ H} \quad \text{--- (iv)}$$

Adding (iii) & (iv) gives

$$L_1 = 0.9 \text{ H}$$


$$\text{Then } L_2 = \underline{\underline{0.4 \text{ H}}}$$

Introduction to Passive Elements- Inductor

Inductance in ||ol →

~~In fig.~~

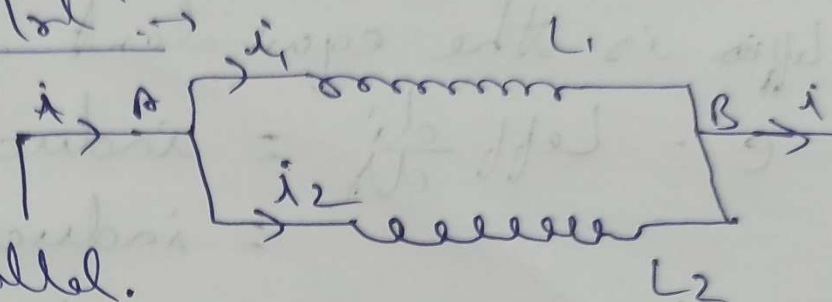Two inductance are connected in parallel.



The co-efficient of mutual inductance between the two ~~is~~ M. 'i' is the main current and i₁ is current through L₁ & i₂ is current through L₂.

$$\text{So, } i = i_1 + i_2$$

$$\frac{di}{dt} = \frac{di_1}{dt} + \frac{di_2}{dt} \quad \text{[Differentiating both side]}$$

Since the coils are in ||ol so the ^{total} emf induced in each coil are equal i.e. ϵ then,

Introduction to Passive Elements- Inductor

If L_{eff} is the equivalent inductance then,

$$e = L_{\text{eff}} \frac{di}{dt} = \text{induced emf in the 1st combination}$$
$$= \text{induced emf. in any one coil}$$

$$L_{\text{eff}} \frac{di}{dt} = L_1 \frac{di_1}{dt} + M \frac{di_2}{dt}$$

$$\text{or, } \frac{di}{dt} = \frac{1}{L} \left(L_1 \frac{di_1}{dt} + M \frac{di_2}{dt} \right)$$

$$\text{or, } \frac{di}{dt} = \frac{1}{L} \left[L_1 \left(\frac{L_2 - M}{L_1 - M} \right) + M \right] \frac{di_2}{dt} \quad \text{--- (10)}$$

Introduction to Passive Elements- Inductor

Equating eqn. (ii) and (iii) we get

$$\frac{L_2 - M}{L_1 - M} + 1 = \frac{1}{L} \left[L_1 \frac{(L_2 - M)}{(L_1 - M)} + M \right]$$

$$\frac{L_1 + L_2 - 2M}{\cancel{(L_1 - M)}} = \frac{1}{L} \left[\frac{L_1 L_2 - \cancel{L_1 M} + \cancel{L_1 M} - M^2}{\cancel{(L_1 - M)}} \right]$$

$$L = \frac{L_1 L_2 - M^2}{L_1 + L_2 - 2M} \quad \text{when fields are additive.}$$

and $L = \frac{L_1 L_2 - M^2}{L_1 + L_2 + 2M}$ when 2 fields oppose each other.

Introduction to Passive Elements - Inductor

For any query contact- 9771474020

Thank You

To be Contd..