

Paper 1, TDC Part-1
Chapter– 1, Introduction to Passive Elements
Inductor

By:

Mayank Mausam


Assistant Professor (Guest Faculty)

Department of Electronics

L.S. College, BRA Bihar University,

Muzaffarpur, Bihar


Introduction to Passive Elements

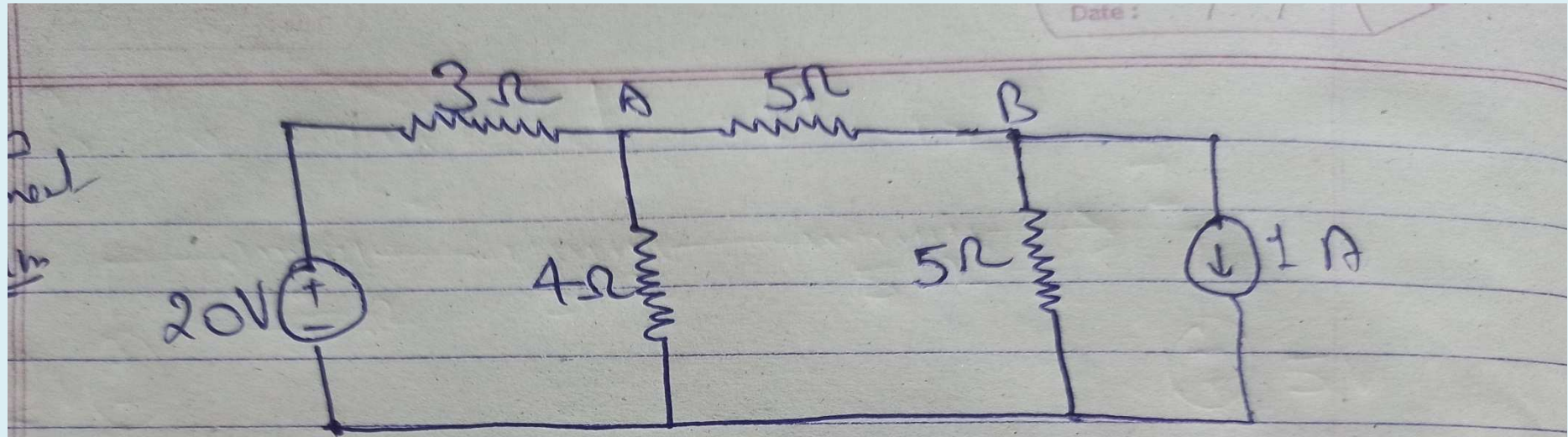

To find the magnitude and direction of current in 5Ω resistor connected in branch AB using source transformation technique.

Here we can convert voltage source with of $20V$ with series resistor of 3Ω into equivalent current source. i.e.


Introduction to Passive Elements

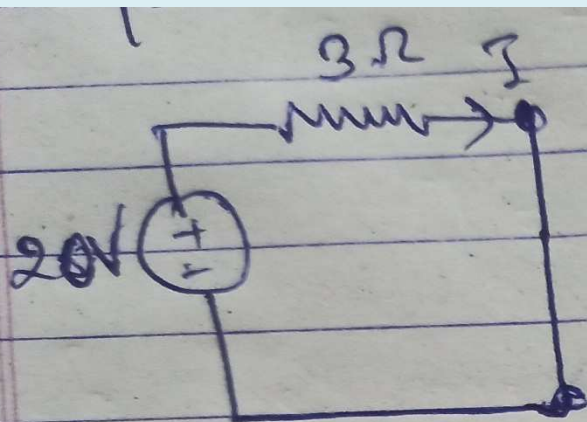


$$I = \frac{20}{3} \text{ A}$$

So equivalent current source have magnitude of $\frac{20}{3} \text{ A}$ and parallel resistor of 3Ω . Then

the n/w can be redrawn as.

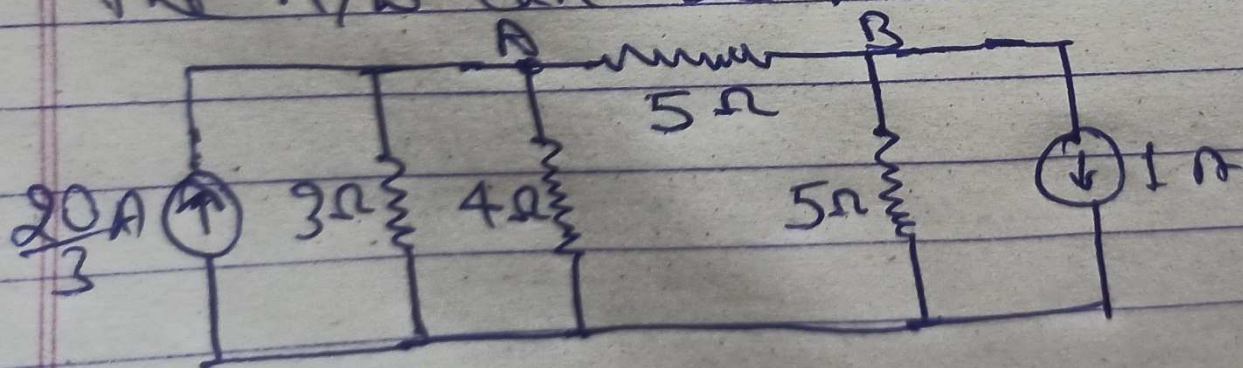

Introduction to Passive Elements

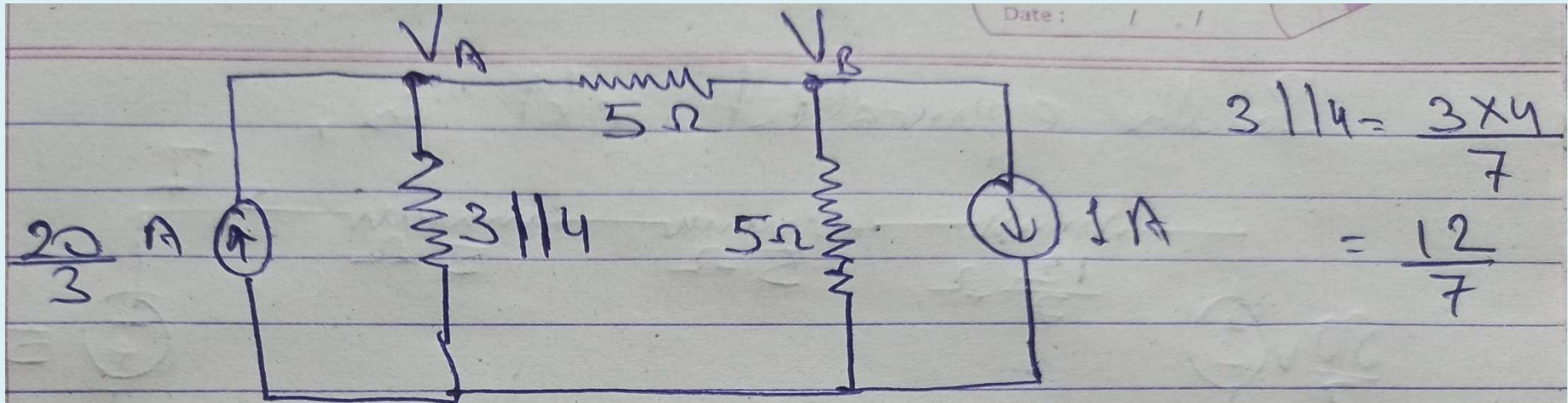

Now we can convert (i) $\frac{20}{3} \text{ A}$ current source and parallel resistor of $\frac{12}{7} \Omega$ into voltage source

with series resistance of $\frac{12}{7} \Omega$

$$\text{i.e. } V_{\frac{12}{7} \Omega} = \frac{12}{7} \times \frac{20}{3} = \frac{80}{7} \text{ V}$$

Introduction to Passive Elements

So the practical voltage source with supply voltage of $\frac{80}{7} \text{ V}$ in series with $\frac{12}{7} \Omega$


1) We convert $\textcircled{\downarrow} 1 \text{ A}$ current source and parallel resistor of 5Ω into practical voltage source ~~is~~ with series resistance of 5Ω

$$\text{i.e. } V_{5\Omega} = 5 \times 1 = 5 \text{ V}$$

So the practical voltage source with supply voltage of 5 V in series with 5Ω resistor.

Introduction to Passive Elements

So the equivalent ckt is,

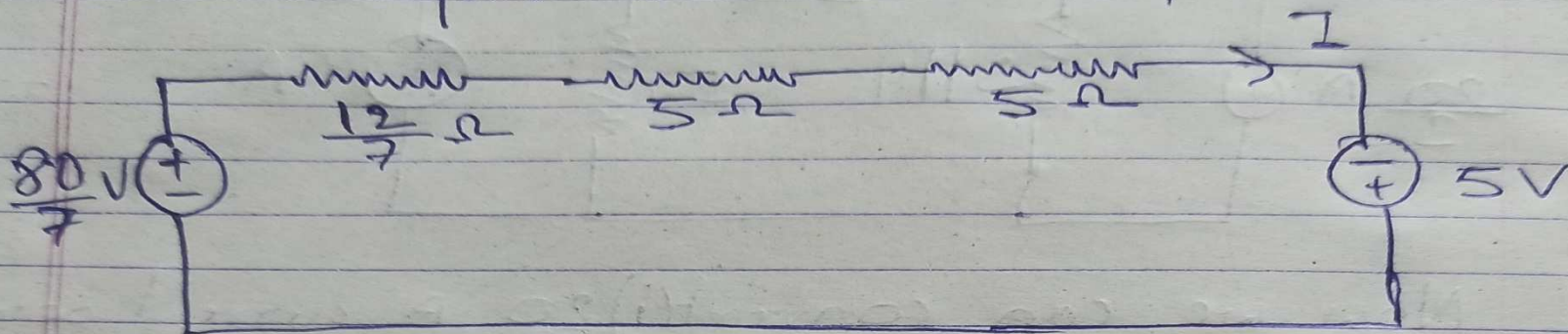

Now apply KVL we find current I in the above ckt.

$$-\frac{80}{7}V + \frac{12}{7}I + 5I + 5I - 5V = 0$$

$$\text{or, } \frac{12I + 70I}{7} = \frac{115}{7}V$$

$$\text{or, } I = \frac{115}{82} \approx 1.4A$$


So the magnitude of current through 5Ω resistor is $1.4A$ and its direction is from A to B.

Introduction to Passive Elements


Unit - 1 (Inductor) -

In We denote Inductor by 'L'.

It is represented by

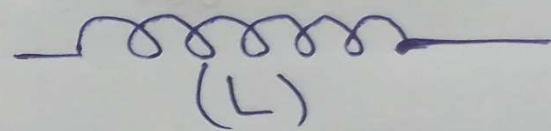

It's unit is Henry (H)

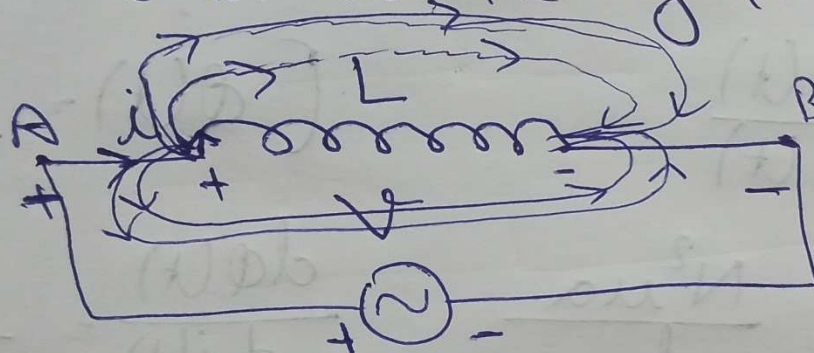

$$V_{AB}(t) = L \frac{di(t)}{dt}$$

Suppose it has 'N' no. of turns then.

when current flows through this inductor then magneto motive force (mmf) develop

and $mmf = Ni(t)$

$N \cdot i(A)$

Introduction to Passive Elements

$$\text{flux } (\Phi) = \frac{\text{MMF}}{\text{Reluctance}} = \frac{N \cdot i(A)}{R}$$

Reluctance represents opposition to magnetic flux. and is given by

$$R = \frac{l}{\mu A} \quad l = \text{length}$$

$A = \text{Cross-section Area}$

$\mu = \text{permeability of the material.}$

When alternating current passes through the inductor then.

$$\Phi(t) = \frac{N \cdot I_m \sin \omega t}{R} = \Phi_m \sin \omega t$$

Introduction to Passive Elements

$$e(t) = \frac{N d\phi(t)}{dt} = \frac{N d\phi(t)}{di(t)} \times \frac{di(t)}{dt}$$
$$= L \frac{di(t)}{dt}$$

$$\text{So } L = N \frac{d\phi(t)}{di(t)}$$

$$\left[\phi(t) = \frac{N i(t)}{R} \right]$$


$$L = \frac{N^2}{R} = \frac{N^2 \mu a}{l}$$

$$\frac{d\phi(t)}{di(t)} = \frac{N}{R}$$

So we can define the inductance as the property of material that oppose change of current through material.

Introduction to Passive Elements

material

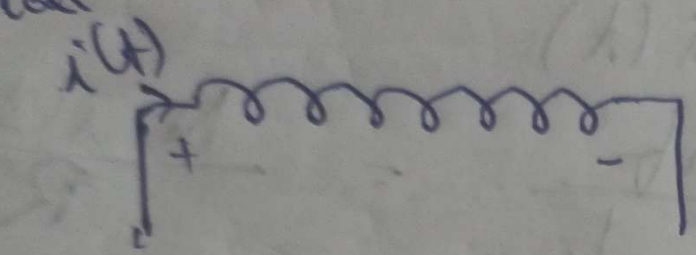

$v_L(t) = \frac{L \cdot di_L(t)}{dt}$

$di_L(t) = \frac{1}{L} v_L(t) dt$

$\int_{i_L(0)}^{i_L(t)} di_L(t) = \frac{1}{L} \int_0^t v_L(t) dt$

$i_L(t) - i_L(0) = \frac{1}{L} \int_0^t v_L(t) dt$

$i_L(t) = i_L(0) + \frac{1}{L} \int_0^t v_L(t) dt$

Introduction to Passive Elements

For any query contact- 9771474020

Thank You