

Paper 1, TDC Part-1
Chapter– 1, Introduction to Passive Elements
Lecture - 1

By:

Mayank Mausam

Assistant Professor (Guest Faculty)

Department of Electronics

L.S. College, BRA Bihar University,

Muzaffarpur, Bihar

Introduction to Passive Elements

Introduction to passive element →

In a electrical (electronic) ckts we deal with two types of elements:- one is active elements and other is passive elements.

Active Elements are those elements which are able to supply energy to the network or it can amplifies the power of a signal (voltage or current).

For Example :- Current source, Voltage source, Transistors e.t.c.

Introduction to Passive Elements

On the other hand "passive elements" are those elements which take energy from the source and either convert it to another form or store it in an electric or magnetic field.

For example \rightarrow Resistance, Capacitor, Inductor.

These passive elements are defined by the manner in which the voltage and current are related for the individual element.

For example - if the voltage and current is related by a constant, then the element is resistance. Similarly if the voltage

Introduction to Passive Elements

is proportional to the time derivative of current, then the element is an inductance and if the current in the element is proportional to the time derivative of the voltage, then the element is a capacitance.


Resistance →

It is the property of the a substance due to which it opposes (or restricts) the flow of electricity (i.e. electrons) through it.

All electrical devices that consume energy must have a resistor (also called a resistance) in their model.

Introduction to Passive Elements

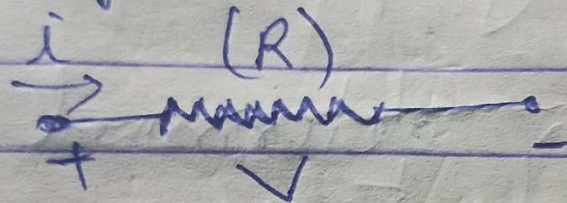In a circuit or network resistance is ~~also~~ represented by symbol (R)



Circuit/Network representation of Resistance

The practical unit of resistance is "ohm".
A conductor is said to have a resistance of one ohm if it permits one ampere current to flow through it when one volt is applied across its

Introduction to Passive Elements

terminal.

Symbol for ohm Ω is R .

Resistance of electrical conductor is very low
" " Insulator is very high
" " Semi-conductor lie in between
conductor and insulator.

~~Current~~ Voltage - Current relationship of
the Resistance is given by Ohm's law

$$V = RI \Rightarrow R = \frac{V}{I}$$

Introduction to Passive Elements

Power in the resistor, given by ~~$p = VI$~~

$$p = VI = \frac{V^2}{R} = I^2 R.$$

Power is always positive.

Energy is then determined as the integral of the instantaneous power

$$W = \int_{t_1}^{t_2} p \, dt = R \int_{t_1}^{t_2} I^2 \, dt = \frac{1}{R} \int_{t_1}^{t_2} V^2 \, dt.$$

(2) A $4.0 \, \Omega$ resistor has a current $i = 2.5 \sin \omega t$ (A). Find the voltage, power and energy over one cycle given, $\omega = 500 \text{ rad/s}$

Introduction to Passive Elements

Soln:

$$V = RI = 4.0 \times 2.5 \sin \omega t \text{ (A)} \\ = 10 \sin \omega t \text{ (V)}$$

$$P = VI = 2.5 \sin \omega t \times 10 \sin \omega t \\ = 25 \sin^2 \omega t \text{ (W)}$$

$$W = \int_0^t P dt = \int_0^t 25 \sin^2 \omega t \\ = 25.0 \left[\frac{t}{2} - \frac{\sin 2\omega t}{4\omega} \right] \text{ J}$$

The resistance of any material with uniform cross-sectional area A depends on R and its length l and is mathematically expressed as,

Introduction to Passive Elements

is expressed as,

$$R = \rho l / A$$

where ρ is known as the resistivity of a material in ohm-meters.

Ohm's law states that the voltage V across a resistor is directly proportional to current I flowing through the resistor. $V \propto I$

Ohm defined the constant of proportionality for a resistor to be the resistance, R .

$$V = IR \rightarrow \cancel{V = IR}$$

Introduction to Passive Elements

For any query contact- 9771474020

Thank You