

Paper 1, TDC Part-1
Chapter– 3, Mesh and Node Analysis
Nodal Analysis -2

By:

Mayank Mausam

Assistant Professor (Guest Faculty)

Department of Electronics

L.S. College, BRA Bihar University,

Muzaffarpur, Bihar

Mesh and Nodal Analysis in Passive Circuits

Now to solve for V_{AO} , V_{BO} & V_{CO} we will write KCL at nodes A, B, & C respectively,

KCL at Node A can be written as,

$$I_1 - I_2 - I_3 = 0 \quad [\text{A/c to KCL } \Sigma I = 0 \text{ at any node}]$$

$$\therefore I_1 = I_2 + I_3$$

$$\therefore \frac{E_1 - V_{AO}}{R_1} = \frac{V_{AO} - V_{BO} + E_2}{R_2} + \frac{V_{AO} - V_{CO} + E_4}{R_3}$$

[from eqn. (i), (v) & (vi)]

$$\text{or, } V_{AO} \left[\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right] - V_{BO} \left[\frac{1}{R_2} \right] - V_{CO} \left[\frac{1}{R_3} \right] = \frac{E_1}{R_1} - \frac{E_2}{R_2} - \frac{E_4}{R_3} \quad \text{--- (vii)}$$

Mesh and Nodal Analysis in Passive Circuits

Now writing KCL at node B,

$$I_2 - I_4 - I_6 = 0$$

$$\Rightarrow \frac{V_{A0} - V_{B0} + E_2}{R_2} - \frac{V_{B0} - V_{C0}}{R_4} - \frac{V_{B0} - E_2}{R_2} = 0$$

[from eqn. i, ii & iii]

$$\text{or, } \frac{V_{A0}}{R_2} - V_{B0} \left(\frac{1}{R_2} + \frac{1}{R_4} + \frac{1}{R_2} \right) + \frac{V_{C0}}{R_4} = -\frac{E_2}{R_2} - \frac{E_2}{R_2}$$

$$\text{or, } -\frac{V_{A0}}{R_2} - V_B \left(\frac{1}{R_2} + \frac{1}{R_4} + \frac{1}{R_2} \right) - \frac{V_{C0}}{R_4} = \frac{2E_2}{R_2} \quad (\text{vii})$$

Mesh and Nodal Analysis in Passive Circuits

Now writing KCL at node C,

$$I_3 + I_4 - I_5 = 0 \quad (I_3 \text{ \& } I_4 \text{ are incoming current \& } I_5 \text{ is outgoing})$$

$$\text{So, } \frac{V_{AO} - V_{CO} + E_4}{R_3} + \frac{V_{BO} - V_{CO}}{R_4} - \frac{V_{CO} + E_3}{R_5} = 0$$

$$\text{or, } -\frac{V_{AO}}{R_3} - \frac{V_{BO}}{R_4} + V_{CO} \left(\frac{1}{R_3} + \frac{1}{R_4} + \frac{1}{R_5} \right) = \frac{E_4}{R_3} - \frac{E_3}{R_5}$$

(ix)

As we have three eqns. (vii), (viii) & (ix) and three unknowns, V_{AO} , V_{BO} , & V_{CO} . So on solving, we can find the value of V_{AO} , V_{BO} & V_{CO} .


Mesh and Nodal Analysis in Passive Circuits

Once we obtained the values of V_{a0} , V_{b0} & V_{c0} we can find the different branch currents.

Q. If we solve the same the same problem using mesh analysis then there will be 4 unknowns and hence we need 4 equations to solve to obtain all the values.

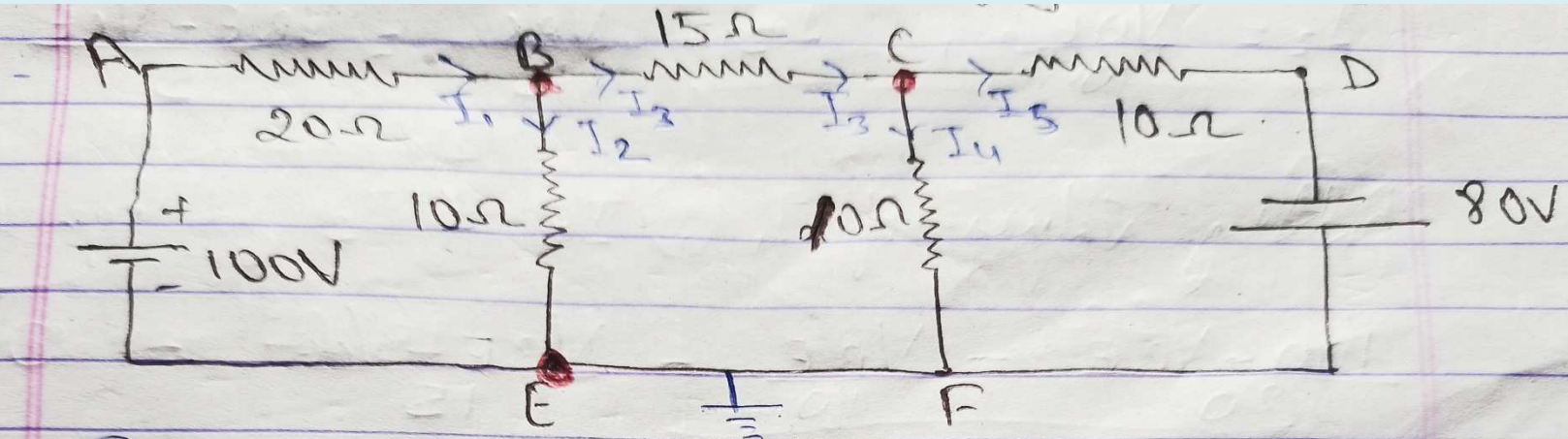1) Find the currents in various branches of the circuit shown in figure.

Mesh and Nodal Analysis in Passive Circuits



Soln: First of all let us identify the nodes and the nodes are B, C and E/F

$n = 3$ where reference node is E i.e.
 $V_E = 0$

Now let us assign the current at the nodes B & C,

Let I_1 is incoming current and I_2 & I_3 are out-

Mesh and Nodal Analysis in Passive Circuits

going current at node B. I_3 is incoming current and I_4 & I_5 are outgoing currents at node C.

Now writing KCL at node B.

$$I_1 = I_2 - I_3 = 0 \quad \text{--- (i)}$$

$$\text{where } I_1 = \frac{V_{AB}}{20} = \frac{V_{AE} - V_{BE}}{20} = \frac{100 - V_{BE}}{20}$$

(As $V_{AD} = 100\text{V}$)

$$I_2 = \frac{V_{BE}}{10}, \quad I_3 = \frac{V_{BC}}{15} = \frac{V_{BE} - V_{CE}}{15}$$

Mesh and Nodal Analysis in Passive Circuits

putting values of I_1 , I_2 & I_3 in eqn. (i)

$$\frac{100 - V_{BE}}{20} - \frac{V_{BE}}{10} - \frac{V_{BE} - V_{CE}}{15} = 0$$

$$5 = V_{BE} \left(\frac{1}{20} + \frac{1}{10} + \frac{1}{15} \right) - \frac{V_{CE}}{15}$$

$$\text{or } \frac{13 V_{BE}}{60} - 4 V_{CE} = 5$$

$$\text{or } 13 V_{BE} - 4 V_{CE} = 300 \quad \text{--- (ii)}$$

Writing KCL at node C,

$$I_3 - I_4 - I_5 = 0 \quad \text{--- (iii)}$$

Mesh and Nodal Analysis in Passive Circuits

$$I_3 = \frac{V_{BE} - V_{CE}}{15}, \quad I_4 = \frac{V_{CE}}{20},$$

$$I_5 = \frac{V_{CE} - V_{DE}}{10} = \frac{V_{CE} - (-80)}{10}$$

$$\text{or, } I_5 = \frac{V_{CE} + 80}{10}$$

$$V_{DE} = -80$$

putting values of I_3 , I_4 & I_5 in eqn (i) we get

$$\frac{V_{BE} - V_{CE}}{15} - \frac{V_{CE}}{20} - \frac{V_{CE} + 80}{10} = 0$$

$$\Rightarrow V_{BE} \left(\frac{1}{15} \right) - V_{CE} \left(\frac{1}{15} + \frac{1}{20} + \frac{1}{10} \right) = \frac{+80}{10} = 8$$

$$\Rightarrow \frac{2V_{BE}}{30} - \frac{3V_{CE}}{30} = 8$$

Mesh and Nodal Analysis in Passive Circuits

$$\Rightarrow V_{BE} + 4V_{CE} = 120 \quad \text{--- (iv)}$$

Subtracting eqn. (iv) from (iii) we get.

$$13V_{BE} - 4V_{CE} = 300$$

$$-V_{BE} + 4V_{CE} = -120$$

$$12V_{BE} = 180$$

$$V_{BE} = \frac{180}{12} = 15 \text{ V} = V_B$$

$$V_{CE} = V_C = -26.25 \text{ V}$$

$$I_1 = \frac{100 - V_B}{20} = \frac{100 - 15}{20} = 4.25 \text{ A}$$

$$\text{Lastly } I_2 = \frac{V_{BE}}{10} = \frac{V_{BE}}{10} = 1.5 \text{ A}$$

Mesh and Nodal Analysis in Passive Circuits


$$I_3 = 2.75 \text{ A}$$

$$I_4 = -2.625 \text{ A}$$

$$I_5 = 5.375 \text{ A}$$


Assignment

1)

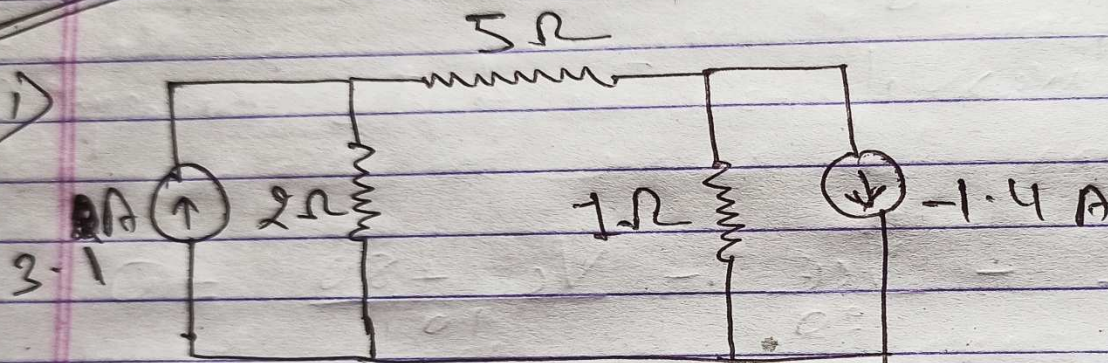

Find the current in 1Ω resistor

2)

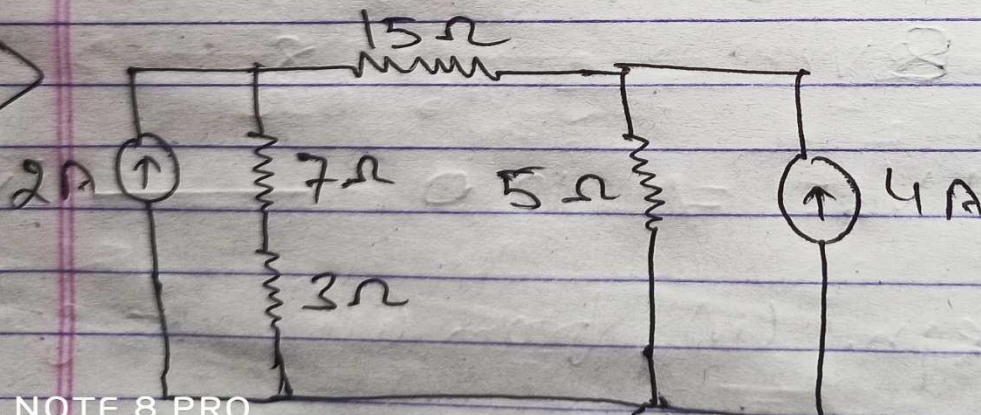

Determine the current flowing left to right through the 15Ω resistor.

Mesh and Nodal Analysis in Passive Circuits

For any query contact- 9771474020

Thank You