

**Paper 1, TDC Part-1**  
**Chapter– 4, Circuit Theorems**  
**Lecture – 5 Superposition Theorem**

**By:**

**Mayank Mausam**

**Assistant Professor (Guest Faculty)**

**Department of Electronics**


**L.S. College, BRA Bihar University,**

**Muzaffarpur, Bihar**

# Circuit Theorem – Superposition Theorem

Solutions of problem discussed

Q1)

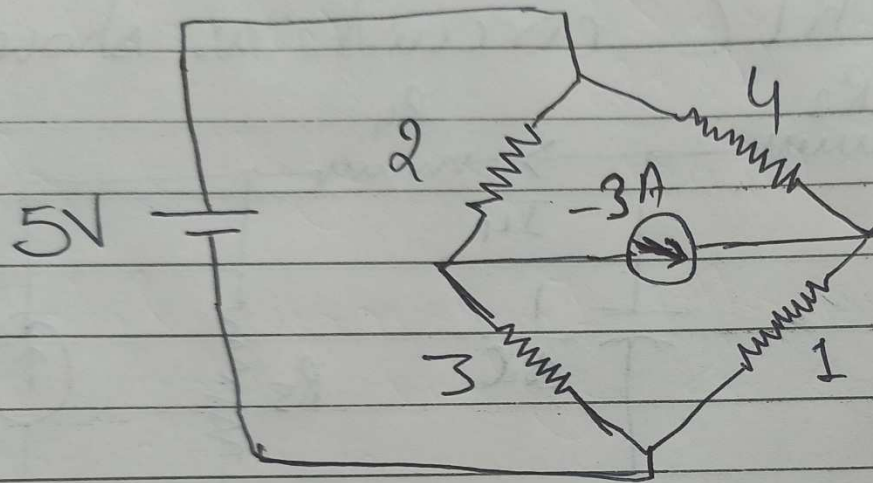

Find the current & voltage in  $3\Omega$  Resistor using superposition theorem.

figure 1(a)

Sol: As per superposition theorem while solving the n/w we will consider one source at a time and removing remaining other sources with their internal resistance.

So let us consider  $5V$  voltage source 1st, so removing  $-3A$  current source with its

# Circuit Theorem – Superposition Theorem

So let us consider 5V voltage source 1st, so removing -3A current source with it's equivalent internal resistance. So the ckt is

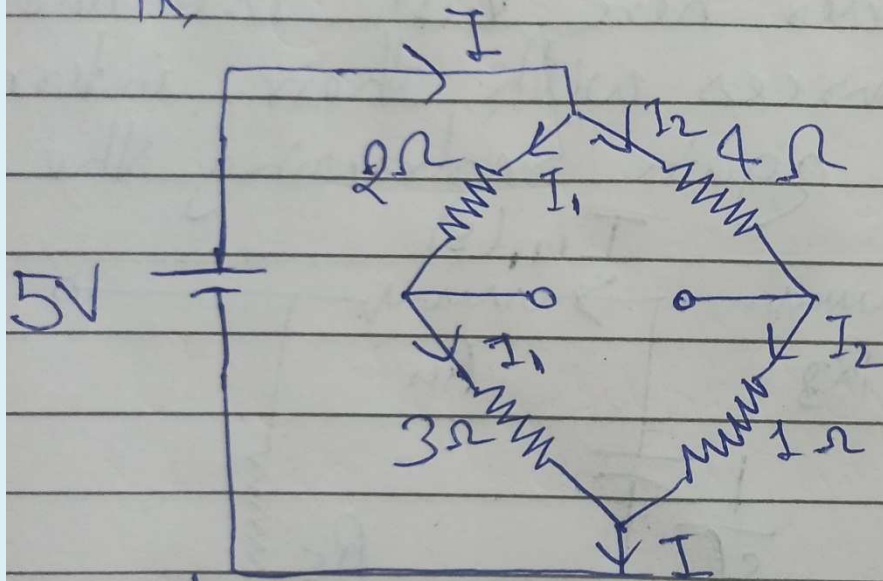



figure 1(b)

For the ckt. shown in figure 1(b)

We have 2Ω & 3Ω resistors are in series & on other side 4Ω & 1Ω resistors are in series

So the ckt. can be considered as shown in figure 1(c).
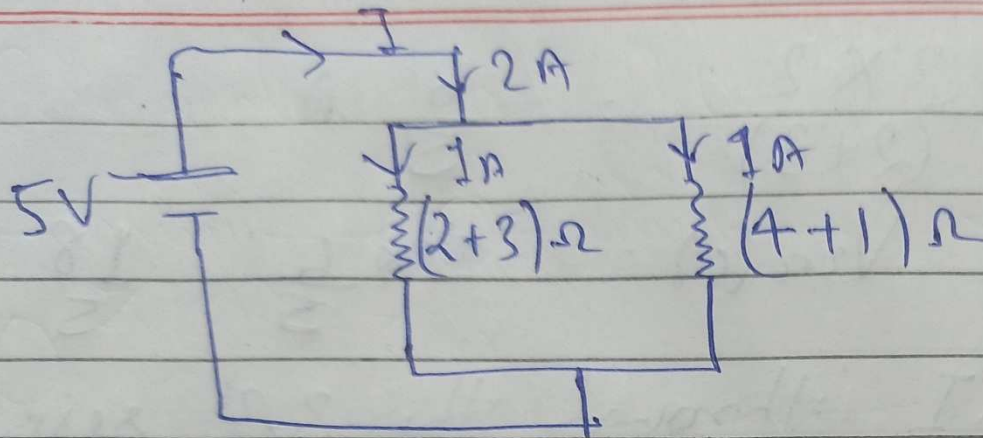
# Circuit Theorem – Superposition Theorem



So current  $I =$   

$$= \frac{5V}{5\Omega \parallel 5\Omega} = \frac{5V}{2.5\Omega}$$

$$= 2A.$$

fig 1(c)

So the current through through  $3\Omega$  resistor due to  $5V$  voltage source is  $1A$  and voltage across the  $3\Omega$  resistor is  $3V$ .

Now let us take current source & remove voltage source by its equivalent internal resistance. So the ckt. redrawn in fig 1(d)

# Circuit Theorem – Superposition Theorem


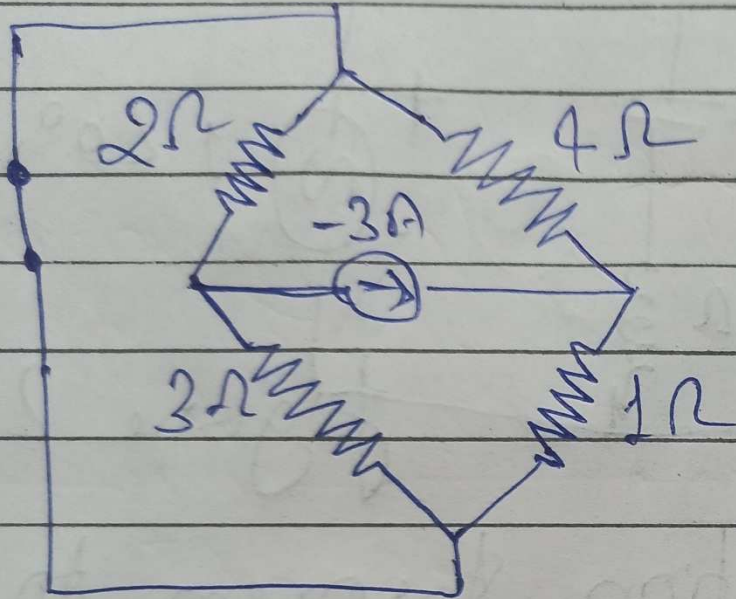
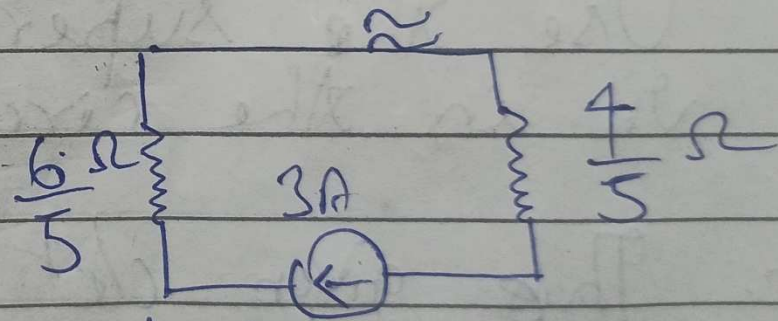


Fig 1(d)

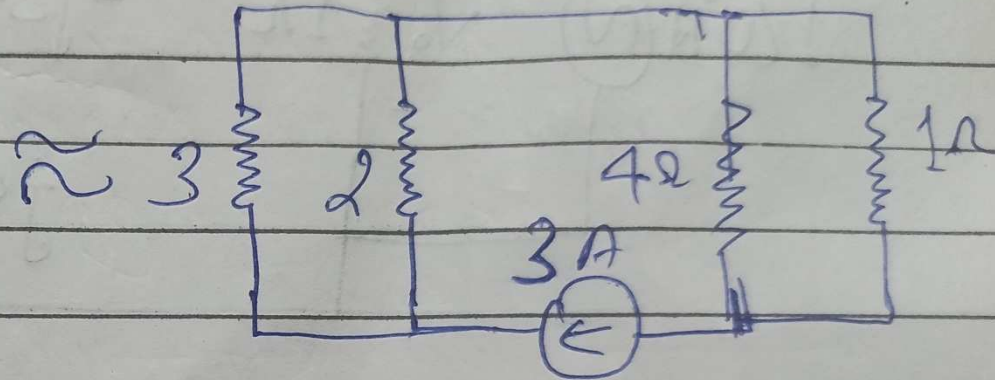

From above ckt we can find  
 Current through  $3\Omega$  resistor due to  $3A$  current  
 source is

# Circuit Theorem – Superposition Theorem

$$I_{3R}(a) = \frac{3 \times 2}{(2+3)} = \frac{6}{5} \text{ A}$$

So, Voltage is  $V_{3R}(c) = 3 \times \frac{6}{5} = \frac{18}{5} \text{ V}$


Total current  $I$  through the  $3R$  resistor due to both voltage & current sources connected in ckt. is,

$$I_{3R} = \left( \frac{6}{5} + 1 \right) \text{ A} = \left( \frac{11}{5} \right) \text{ A} = 2.2 \text{ A}$$

and So <sup>total</sup> voltage across  $3R$  resistor is given by

$$= (2.2 \times 3) \text{ V}$$
$$= 6.6 \text{ V}$$
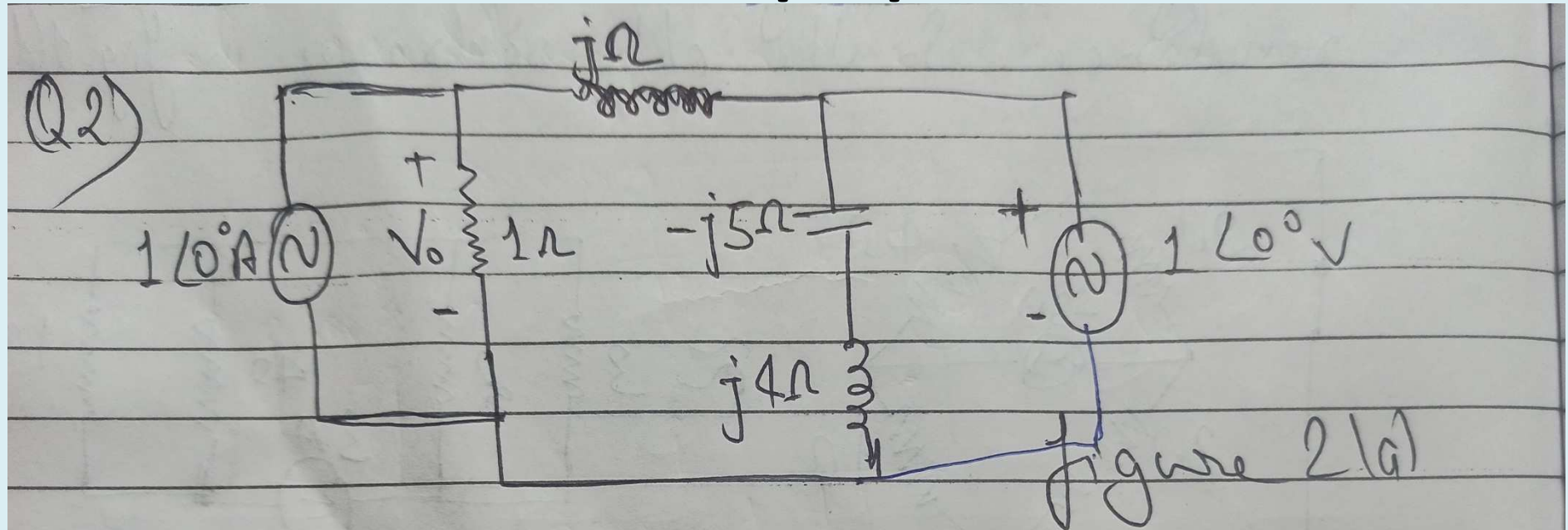
# Circuit Theorem – Superposition Theorem




Use the superposition theorem to find  $V_0$  in the circuit given ~~below~~ in figure 2(a).

soln. This given ckt. also consist of energy storage element or in other word it is a RLC ckt. The ckt can also be solved
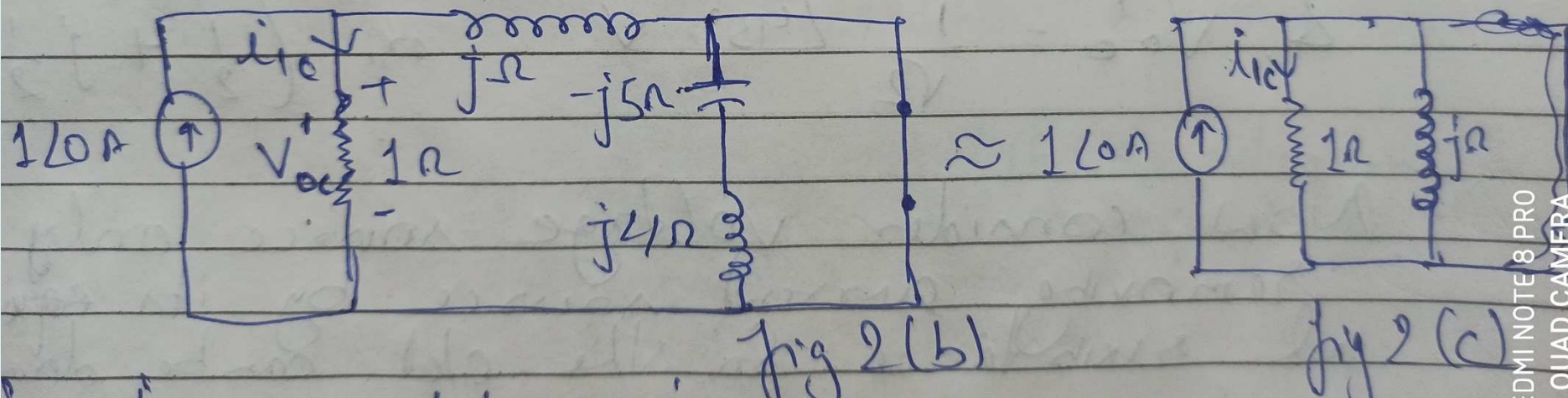
# Circuit Theorem – Superposition Theorem

using superposition theorem in the same way as discussed earlier problems on superposition theorem.

So first consider current source connected in left of the ckt, and removing voltage source by its equivalent (internal) resistance



# Circuit Theorem – Superposition Theorem

$$\text{So, } \hat{I}_{1c} = 1 \angle 0^\circ \times \frac{j}{1+j\Omega}$$

angle

$$\text{Phase of } j = \tan^{-1}\left(\frac{1}{0}\right) = \tan^{-1}(\infty) = 90^\circ$$

$$\text{Magnitude of } j = \sqrt{0^2 + 1^2} = \sqrt{1} = 1$$

$$j = 1 \angle 90^\circ$$

Also,  $1+j\Omega$  in polar form written as,

$$= \sqrt{1^2 + 1^2} \tan^{-1}\left(\frac{1}{1}\right) = \sqrt{2} \tan^{-1} 1 = \sqrt{2} \angle 45^\circ$$

# Circuit Theorem – Superposition Theorem

$$\text{So, } i_{1c} = \frac{1 \angle 0^\circ \times 1 \angle 90^\circ}{\sqrt{2} \angle 45^\circ} = \frac{1 \angle 90^\circ - 45^\circ}{\sqrt{2}} \\ = \frac{1 \angle 45^\circ}{\sqrt{2}} \text{ A}$$

$$\text{In cartesian form, } i_{1c} = \frac{1}{\sqrt{2}} \cos 45^\circ + j \frac{1}{\sqrt{2}} \sin 45^\circ \\ = \left( \frac{1}{2} + j \frac{1}{2} \right) \text{ A}$$

$$\Delta, V_{0c} = \frac{1 \angle 45^\circ}{\sqrt{2}} \text{ V} \quad \text{or} \quad \left( \frac{1}{2} + j \frac{1}{2} \right) \text{ V}$$

Now consider voltage source only removing current source by its equivalent resistance. So the ckt can be drawn

# Circuit Theorem – Superposition Theorem

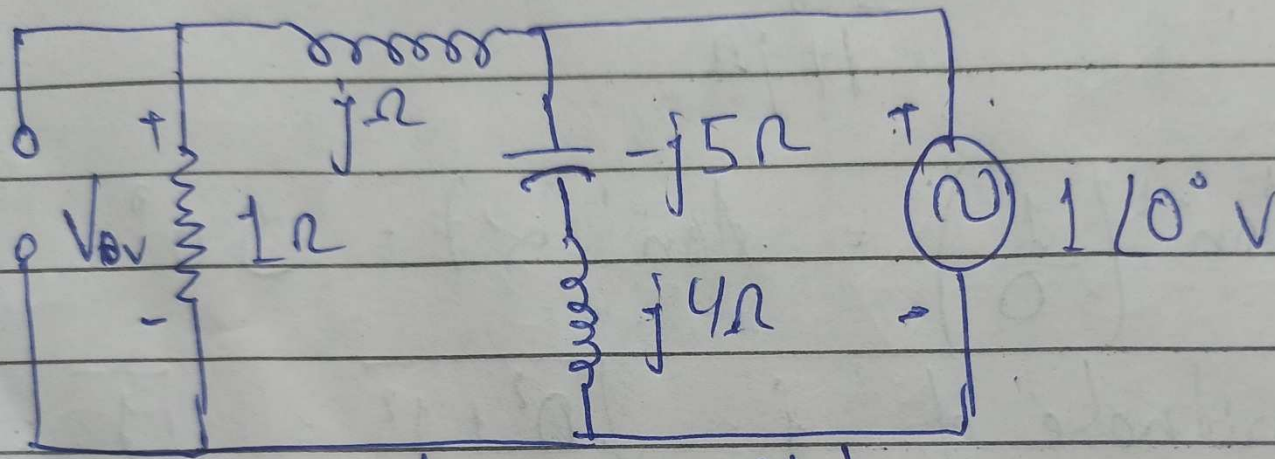


Figure 1 (d)

$$\begin{aligned} \text{So, } V_{ov} &= \frac{1 \angle 0^\circ \times 1}{(1 + j)} = \frac{1 \angle 0^\circ}{\sqrt{2} \angle 45^\circ} = \frac{1}{\sqrt{2}} \angle -45^\circ \\ &= \frac{1}{\sqrt{2}} \angle -45^\circ \text{ V} \end{aligned}$$

# Circuit Theorem – Superposition Theorem

$$V_{ov} = \frac{1}{\sqrt{2}} \angle -45^\circ \approx \frac{1}{\sqrt{2}} \cos(-45^\circ) + j \frac{\sin(-45^\circ)}{\sqrt{2}}$$

$$= \frac{1}{\sqrt{2}} \times \frac{1}{\sqrt{2}} - j \frac{1}{\sqrt{2}} \times \frac{1}{\sqrt{2}} = \frac{1}{2} - j \frac{1}{2}$$

So total Voltage across  $2\Omega$  resistor is.

$$V_o' = \left( \frac{1}{2} + j \frac{1}{2} \right) + \left( \frac{1}{2} - j \frac{1}{2} \right)$$

$$= 1 \text{ V}$$

Q Find current through  $j4\Omega$  inductor ~~resistor~~ in the ckt. shown below using superposition theorem

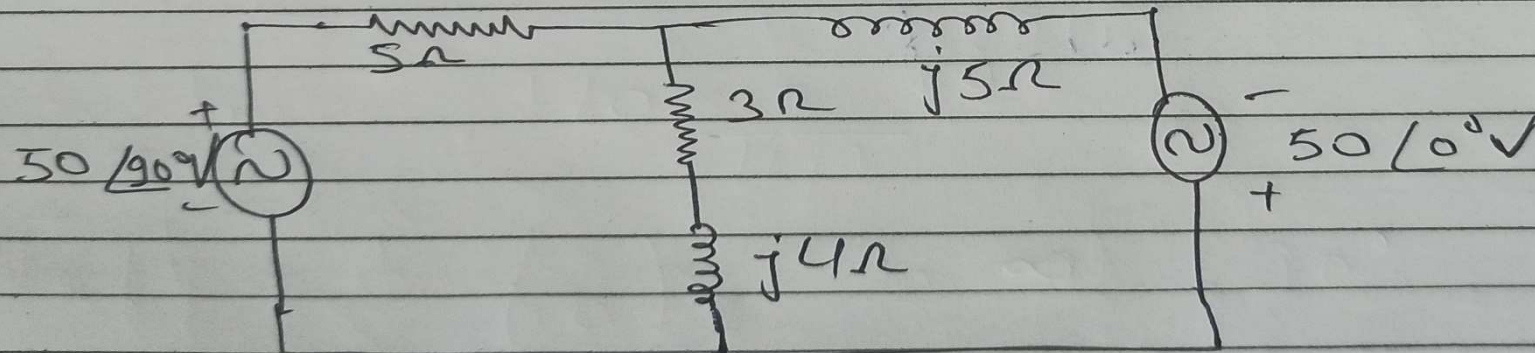


Figure 3(a)

# **Circuit Theorem – Superposition Theorem**

For any query contact at “9771474020”.

*Thank You*