

Paper 1, TDC Part-1
Chapter– 4, Circuit Theorems
Lecture – 2 Superposition Theorem

By:

Mayank Mausam

Assistant Professor (Guest Faculty)

Department of Electronics

L.S. College, BRA Bihar University,

Muzaffarpur, Bihar

Circuit Theorem – Superposition Theorem

- In previous lecture we have discussed “Superposition Theorem” and did one example. Today we will solve few more problems on superposition theorem.

09/07/2020

Ex → 2 Obtain the current in the branch containing 10Ω resistor of the network shown in fig B using superposition theorem.


fig. (B)

Soln: →

The network consist of two active voltage sources of $20V$ and $8V$. As per superposition theorem we will take one source first then take the other source, so here we take $20V$ source first.

Circuit Theorem – Superposition Theorem

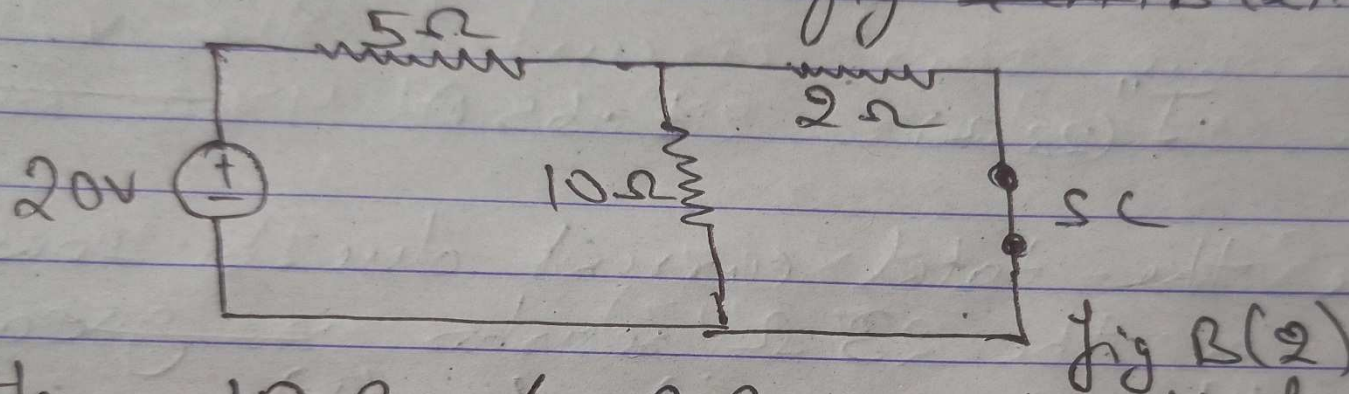So the 8V source will be short circuited as it is a voltage source. The fig of the new is drawn in fig. 2(A) B(2).



Here 10Ω & 2Ω are in \parallel now so

$$R'_{\text{all}} = \frac{5 \times 10 \times 2}{3 + 2 \times 6} \Omega = \frac{5}{3} \Omega =$$

Now 5Ω is in series with $\frac{5}{3} \Omega$ so.

$$R_{\text{eq}} = \left(5 + \frac{5}{3} \right) \Omega = \frac{20}{3} \Omega$$

Circuit Theorem – Superposition Theorem

$$I_T = \frac{20 \times 3}{20} = 3 \text{ A}$$

$$I_{10\Omega} = \frac{3 \times 2}{10 + 2} = 0.5 \text{ A} \quad \text{--- (i)}$$

Now considering 8V source so 20V source will be short circuit, so redrawing n/w. as shown in figure B(3)

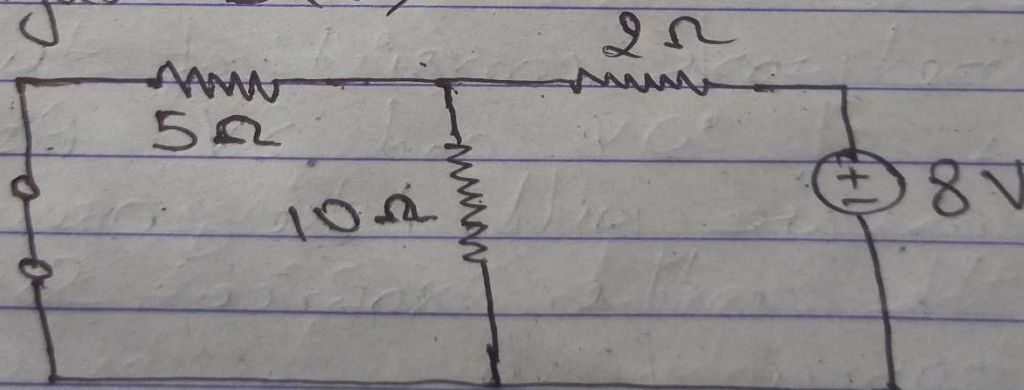


Fig B(3)

Circuit Theorem – Superposition Theorem

REDMI NOTE 8 PRO
AI QUAD CAMERA

Here $10\ \Omega$ & $5\ \Omega$ are in parallel, so
 $R''_{\text{all}} = \frac{10 \times 5}{10 + 5}\ \Omega = \frac{10}{3}\ \Omega$

Now this $\frac{10}{3}\ \Omega$ is in series with $2\ \Omega$

$$\text{So, } R_{\text{eq}} = \left(\frac{10}{3} + 2\right)\ \Omega = \frac{16}{3}\ \Omega$$

Total current deliver by 8V in the n/w is.

$$I''_T = \frac{8 \times 3}{16} \text{ A} \Rightarrow \frac{3}{2} \text{ A}$$

Current deliver to $10\ \Omega$ resistor through 8V source is

$$I''_{10\ \Omega} = \frac{8 \times 5}{2 \times (10 + 5)} = 0.5 \text{ A.} \quad \text{--- (ii)}$$


Hence total current in $10\ \Omega$ resistor due to both sources 90V & 8V voltage sources can be obtained by adding eqn. (i) & (ii)

$$\begin{aligned} I_{10\ \Omega} &= I'_{10\ \Omega} + I''_{10\ \Omega} \\ &= (0.5 + 0.5) \text{ A} \\ &= 1.0 \text{ A.} \end{aligned}$$

Circuit Theorem – Superposition Theorem

- Now let us see third example.

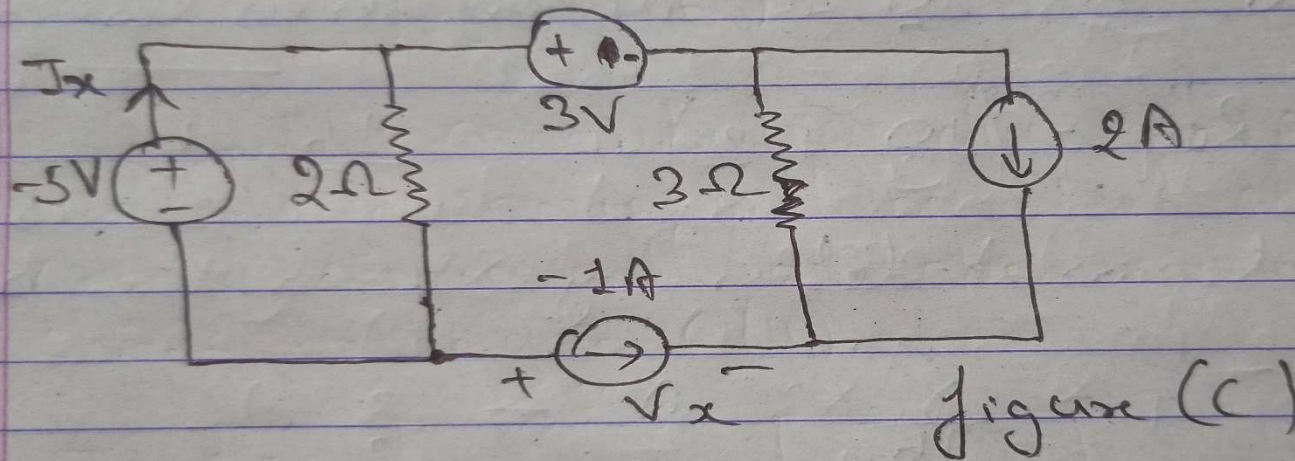
Q Determine V_x & I_x using the superposition theorem for the below circuit shown in figure (c).



Q. Contribution due to $-5V$ voltage source
Both current sources will be open circuited
remaining 1 voltage source will be short ck
So the ckt is drawn in figure (c1)

Circuit Theorem – Superposition Theorem

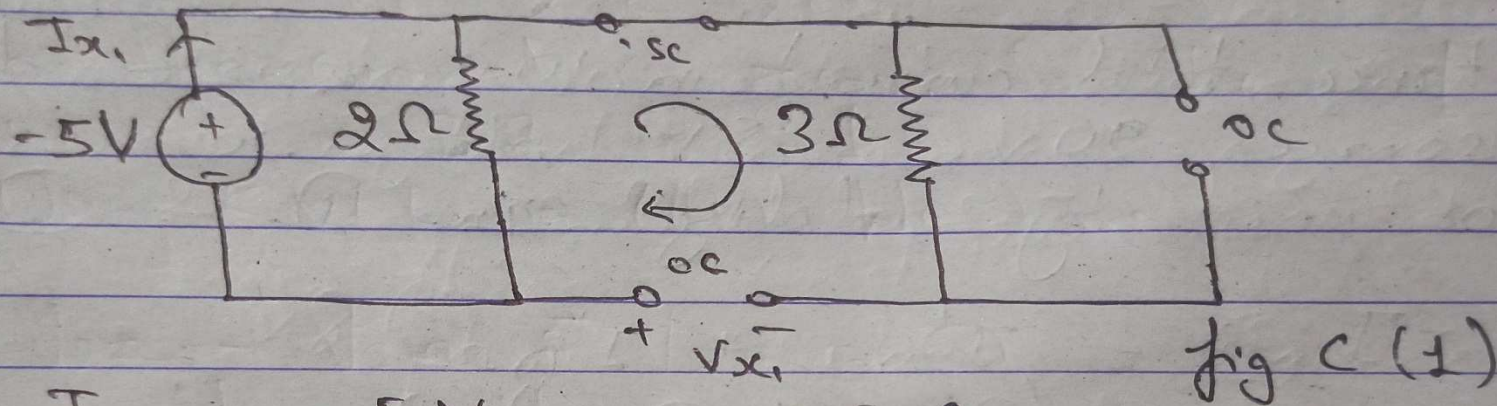remaining 1 voltage source will be short ckt.
So the ckt is drawn in figure (1)



$$I_{x_1} = \frac{-5V}{2\Omega} = -2.5A$$

Current through 3Ω resistor is zero.
Now using KVL in second loop we have


$$-(2\Omega \times -2.5A) + (3\Omega \times 0A) - V_{x_1} = 0$$

$$5V + 0V - V_{x_1} = 0$$

$$V_{x_1} = 5V$$

Circuit Theorem – Superposition Theorem

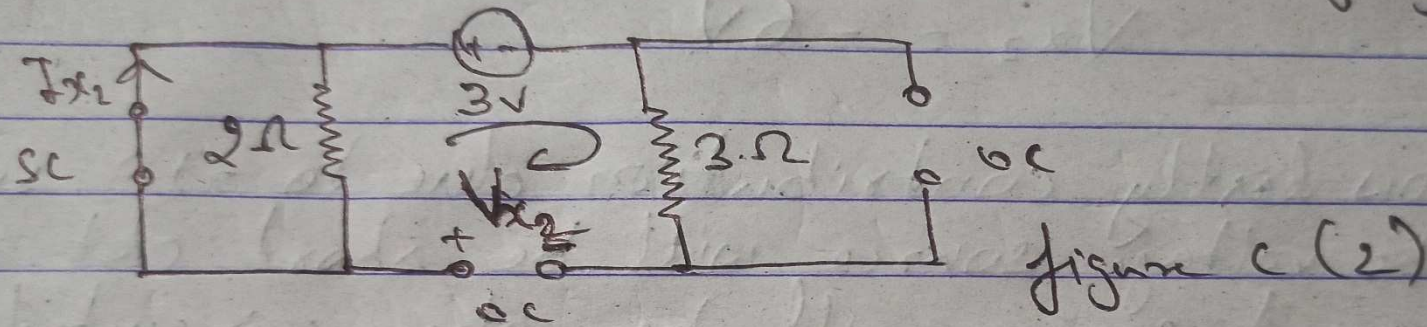Now contribution due to 3V voltage source. Again both current is open circuited & 1 voltage source is ~~sc~~ short circuited, as shown in figure (2)



The current through 2Ω resistor is zero, ~~so the~~
 ~~I_{x2} as it is~~ as there is short circuit ~~to I_{x2}~~

So $I_{x2} = 0\text{ A}$.

Current through 3Ω is also zero.


Now applying KVL in loop of fig. (2)

$$-3V + V_{3\Omega} + V_{x2} + V_{2\Omega} = 0$$

Circuit Theorem – Superposition Theorem

$$\begin{aligned} -3V + V_{3\Omega} + V_{2\Omega} &= 0 \\ -3V + 0V + V_{3\Omega} + 0V &= 0 \\ V_{3\Omega} &= 3V \end{aligned}$$

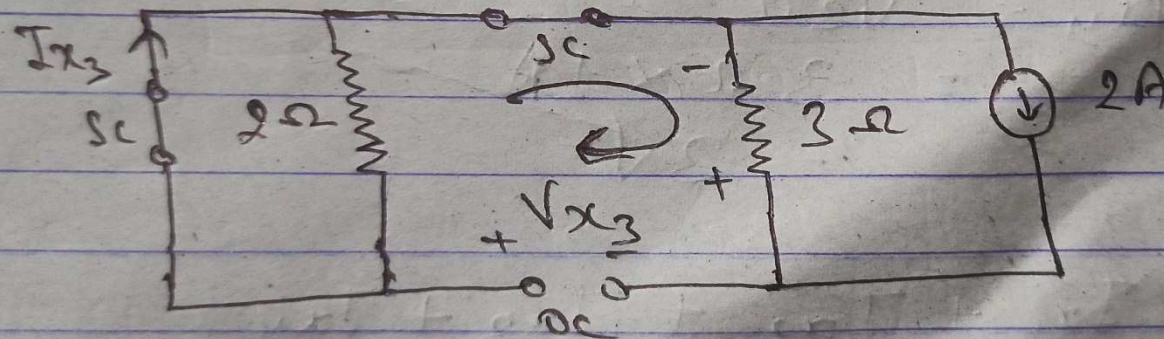Now contribution due to 2A current source, both voltage source will be short ckt. and 2 current source open ckt. as shown in figure (3).



Again, the 2Ω resistor is short circuited so current through it is zero, so $I_{x3} = 0A$.
 $I_{3\Omega} = 2A$.

Circuit Theorem – Superposition Theorem

Using KVL


$$V_{2\Omega} - V_{3\Omega} - V_{x_3} = 0$$

$$0 - 3 \times 2 \text{ V} - V_{x_3} = 0$$

$$V_{x_3} = -6 \text{ V}$$


Now lastly contribution due to -1 A source.

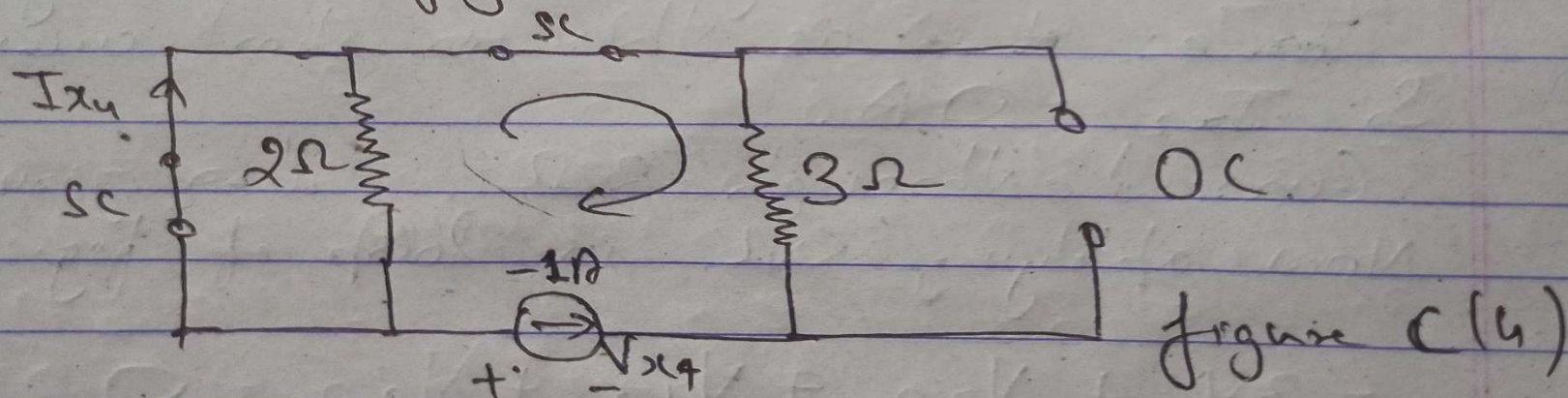The voltage source will be short ckt and one current source will be open circuited, as shown in figure (4).



Again the 2Ω resistor is short circuited.

Circuit Theorem – Superposition Theorem

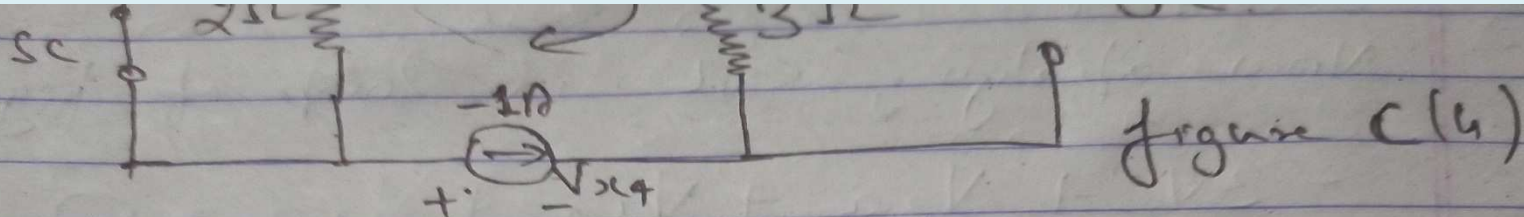

Again, the 2Ω resistor is short circuited so the current is zero, so, $I_{x4} = 1A$. The current in 3Ω is $-1A$.

Using KVL in (4). We have

$$V_{2\Omega} + V_{3\Omega} + V_{x4} = 0$$

$$V_{x4} = -V_{3\Omega}$$

$$= -3\Omega \times 1A$$

$$= -3V$$

So,

$$I_x = I_{x1} + I_{x2} + I_{x3} + I_{x4}$$

$$= -2.5A + 0 + 0 + 1A = -1.5A$$

$$\text{And } V_x = V_{x1} + V_{x2} + V_{x3} + V_{x4}$$

$$= 3V + 3V + -6V + 3V = 3V$$

Circuit Theorem – Superposition Theorem

For any query contact at “9771474020”.

Thank You