

**Paper 7, TDC Part-3**  
**Chapter– 4, Combinational Logic Design**  
**Lecture - 8**

**By:**

**Mayank Mausam**

**Assistant Professor (Guest Faculty)**

**Department of Electronics**

**L.S. College, BRA Bihar University,**

**Muzaffarpur, Bihar**

# Combinational Logic Design

## Grouping Eight Adjacent Ones


Eight cells from a group of 8 adjacent ones or zeros if three of the literals associated with the minterms/maxterms are not same and the other literals are same.

for a 2-Variable K-map we have maximum of 4 cells so ~~we~~ there is no possibility of grouping of 8 cells.

In case of 3-variable K-map, there is only one possibility of eight ones or zeros
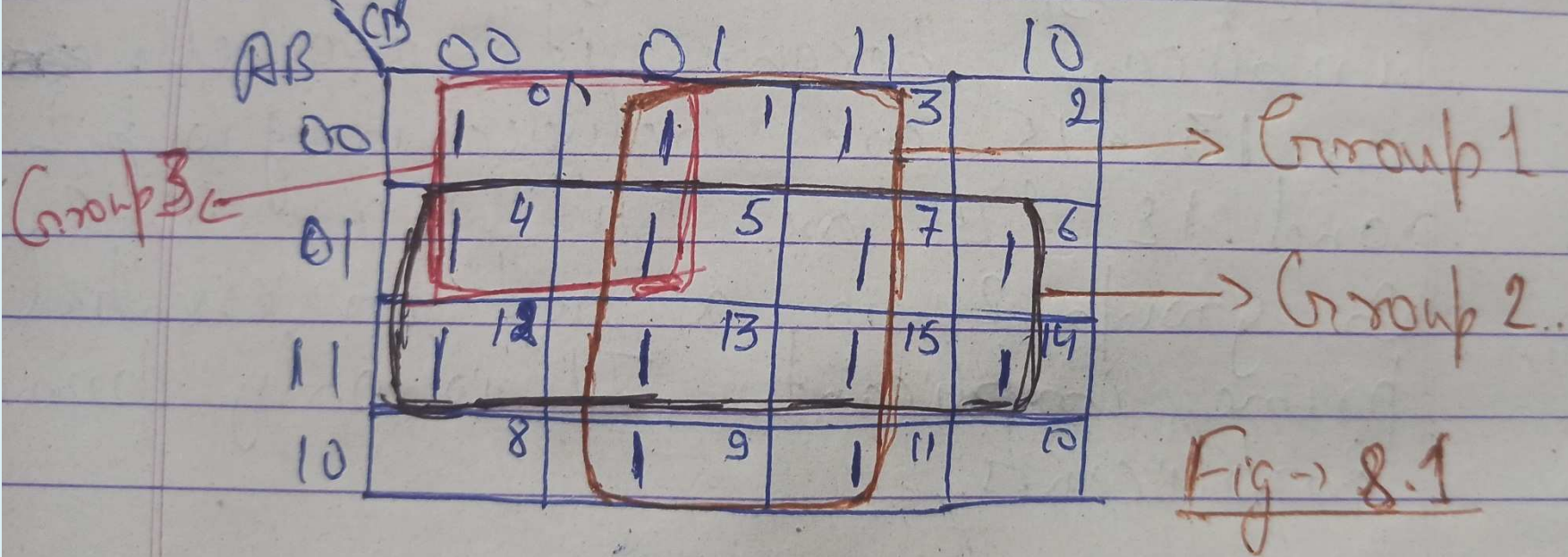
# Combinational Logic Design

appearing in the K-map and this corresponds to output equal to 1, irrespective of the values of the input variables. Figure below ~~gives~~ all shows the grouping of eight adjacent ones in a 4-variable K-map.



# Combinational Logic Design

The above K-map have 2 groups of eight adjacent ones.

Group 1 involves cells with decimal value  $\rightarrow 1, 3, 5, 7, 9, 11, 13$  &  $15$  while Group 2 involves cells with decimal value  $\rightarrow 4, 5, 6, 7, 12, 13, 14$  &  $15$ . Table below gives all possible groups of Eight adjacent ones in a 4-variable K-map.

# Combinational Logic Design

Table 5.7 *Groups of Eight Adjacent Ones  
in 4-variable K-map*

**Decimal numbers of cells forming groups  
of adjacent eights in a 4-variable K-map**

0, 4, 12, 8, 1, 5, 13, 9,

0, 4, 12, 8, 2, 6, 14, 10

0, 1, 3, 2, 4, 5, 7, 6

0, 1, 3, 2, 8, 9, 11, 10

1, 5, 13, 9, 3, 7, 15, 11

4, 5, 7, 6, 12, 13, 15, 14

12, 13, 15, 14, 8, 9, 11, 10

3, 7, 15, 11, 2, 6, 14, 10

# Combinational Logic Design

Grouping 8 adjacent cells reduce (eliminate) 3 literals than the number of literals in the original minterms.

As in the K-map of Fig 8.1, we have 2 groups.

Group 1 have cells with decimal value 1  $\Rightarrow \bar{A}\bar{B}\bar{C}D$   
1 only for ~~3~~  $\rightarrow \bar{A}\bar{B}CD$ , 5  $\rightarrow \bar{A}B\bar{C}D$ , 7  $\rightarrow \bar{A}BCD$   
9  $\rightarrow A\bar{B}\bar{C}D$ , 11  $\rightarrow A\bar{B}CD$ , 13  $\rightarrow AB\bar{C}D$   
& 15  $\rightarrow ABCD$ .

# Combinational Logic Design

So in all these minterms we find that literal 'D' is present (same) in all terms while the other literals are not common in all terms. So the resulting value of group 1 is 'D'.

Similarly for group 2 we find out that literal 'B' is present (same) in all terms while other literals are not common in all terms so for group 2 resulting value is group 2 is 'B'.

If we solve for the function  $Y$  of the K-map of fig 8.1, we have ~~three~~ groups. 2-groups of adjacent 8 cells & 1-group of adjacent 4-cells was shown in fig 8.1.

# Combinational Logic Design

$$\text{As, } Y = \sum m(0, 1, 3, 4, 5, 7, 6, 9, 11, 12, 13, 14, 15)$$

or in simplified form,

$$Y = D + B + \bar{A}\bar{C}$$

As per grouping of  $m_0, m_1, m_4$  &  $m_5$

As per grouping of  $m_1, m_3, m_5, m_7$

$m_{13}, m_{15}, m_9$  &  $m_{11}$

As per grouping of

$m_4, m_5, m_6, m_7, m_{12}$

$m_{13}, m_{14}$  &  $m_{15}$

# Combinational Logic Design

## Grouping of 2, 4 and 8 Adjacent Zeros

When we want to write the logic function in terms of Maxterms we need to group adjacent zeros in the K-map.

The procedure of grouping 0's is similar to the grouping of 1's in the K-map. But grouping of 0's help in the writing of logic function in POS form.

Grouping of 0's result as below,

- 1.) Group of 2 adjacent zeros result in a term with one literal less than the number of variables. The literal which is not same in the 2 maxterms gets eliminated.

## Combinational Logic Design

2.) Group of 4 adjacent zeros result in a term with 2 literals less than the number of variables. The two literals which are not same in all the 4 maxterms get eliminated.

3.) Group of eight adjacent zeros result in a term with 3 literals less than the number of variables. The 3 literals which are not same in all the 8 maxterms get eliminated.

## Combinational Logic Design

As of now we have seen groups of 2, 4 and 8 adjacent ones and zeros. The same logic can be extended to 16, 32 and 64 adjacent ones and zeros which occur in K-maps with more than 4, 5 variables.

# Combinational Logic Design

Refer book- Modern Digital Electronics by RP Jain.

**Thank You**